

EECE 2322: Fundamentals of Digital Design and Computer Organization


Lecture 4_2: Sequential Circuit and ALU

Xiaolin Xu

Department of ECE
Northeastern University


DRAM (Dynamic Random Access Memory)

- ❖ Bits stored as charges on node capacitance (non-restorative)
 - ❖ bit cell loses charge when read
 - ❖ bit cell loses charge over time
- ❖ Read Sequence
 - ❖ 1~3 same as SRAM
 - ❖ 4. a “flip-flopping” sense amp amplifies and regenerates the bitline, data bit is mux’ed out
 - ❖ 5. precharge all bitlines
- ❖ **Refresh:** A DRAM controller must periodically read each row within the allowed refresh time (10s of ms) such that charge is restored

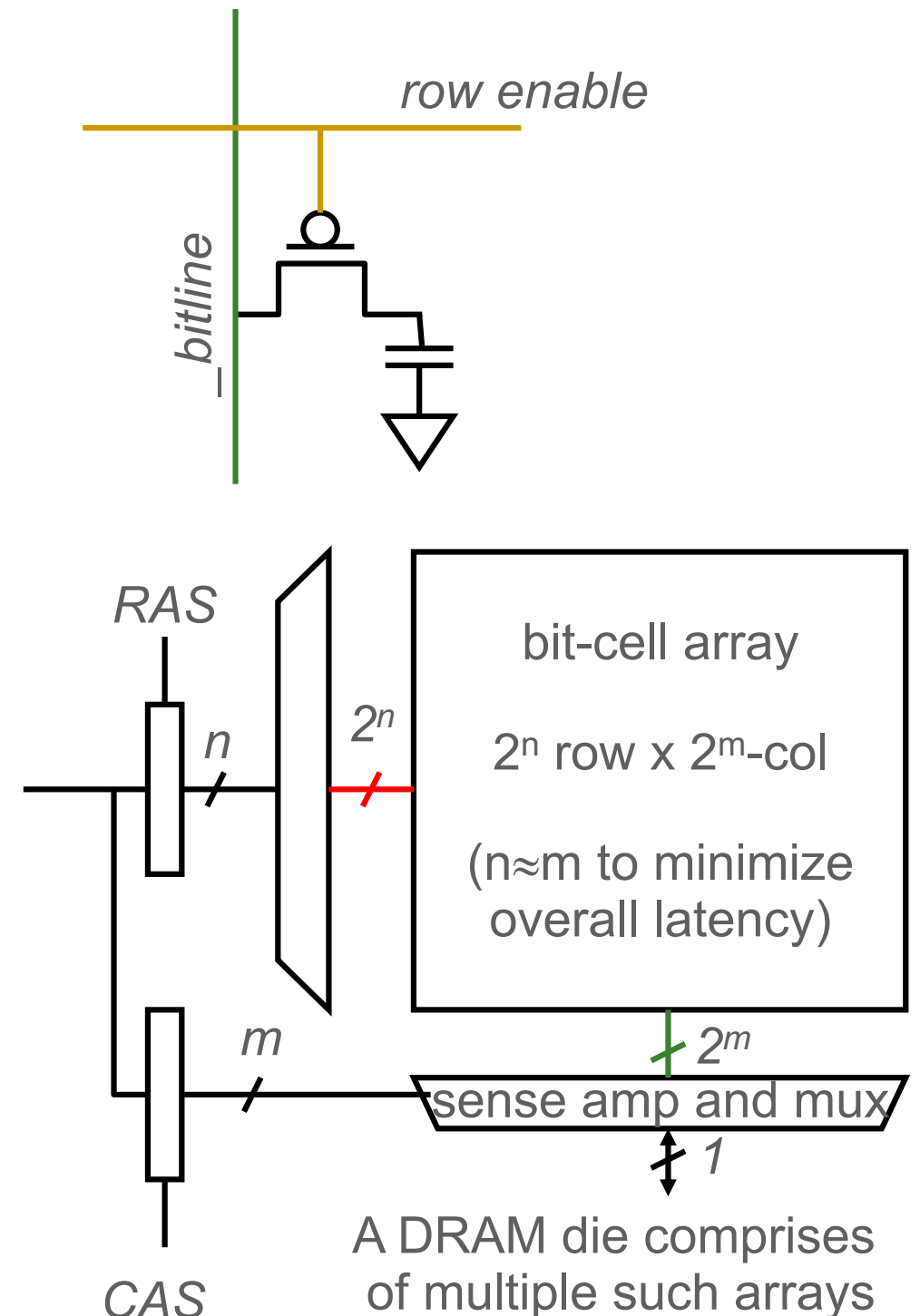

Sequential Logic (2): SR Latch

 
- ❖ SR latch
 - ❖ Cross-coupled NOR gates
 - ❖ S: Set
 - ❖ R: Reset




SR latch symbol

Sequential Logic (2): SR Latch

 - ❖ SR latch
 - ❖ Cross-coupled NOR gates
 - ❖ S: Set
 - ❖ R: Reset



SR latch symbol

 

Sequential Logic (2): SR Latch


- ❖ SR latch

- ❖ S: Set

- ❖ R: Reset


- ❖ Truth table of SR latch

R	S	Q	$\sim Q$
1	0		
0	1		
1	1		
0	0		

 

Sequential Logic (2): SR Latch

 - ❖ SR latch
 - ❖ S: Set
 - ❖ R: Reset
- ❖ Truth table of SR latch



R	S	Q	$\sim Q$
1	0		
0	1		
1	1		
0	0		

Sequential Logic (2): SR Latch

- ❖ SR latch

- ❖ S: Set

- ❖ R: Reset

- ❖ Truth table of SR latch

Case	S	R	Q	\bar{Q}
IV	0	0	Q_{prev}	\bar{Q}_{prev}
I	0	1	0	1
II	1	0	1	0
III	1	1	0	0

R	S	Q	$\sim Q$
1	0		
0	1		
1	1		
0	0		

Sequential Logic (2): SR Latch

- ❖ SR latch

- ❖ S: Set

- ❖ R: Reset

- ❖ Truth table of SR latch


Case	S	R	Q	\bar{Q}
IV	0	0	Q_{prev}	\bar{Q}_{prev}
I	0	1	0	1
II	1	0	1	0
III	1	1	0	0

- ❖ Asserting both S and R simultaneously doesn't make sense, i.e., the latch should be set and reset at the same time, which is impossible

R	S	Q	\bar{Q}
1	0		
0	1		
1	1		
0	0		

 
Problem with SR Latch

- ❖ *SR latch behaves strangely when both S and R are simultaneously asserted*
- ❖ How to solve this issue?
 - ❖ Two complementary inputs forever!
 - ❖ How?
 - ❖ Using an inverter



 Problem with SR Latch

- ❖ *SR latch behaves strangely when both S and R are simultaneously asserted*
- ❖ How to solve this issue?
 - ❖ Two complementary inputs forever!
 - ❖ How?
 - ❖ Using an inverter
- ❖ Truth table



Problem with SR Latch

- ❖ *SR latch behaves strangely when both S and R are simultaneously asserted*

- ❖ How to solve this issue?


- ❖ Two complementary inputs forever!

- ❖ How?


- ❖ Using an inverter

- ❖ Truth table

D	Q	$\sim Q$
0		
1		

 


SR Latch in Verilog

 

```
module sr_latch(  
    input wire S, R,  
    output wire Q, Q_not);  
  
    assign Q      = ~(R | Q_not);  
    assign Q_not = ~(S | Q);  
endmodule
```


Sequential Logic (2): D Latch

 - ❖ *The current design CANNOT latch the D value*
- ❖ How to solve this issue?
 - ❖ Adding an *Enable*



Sequential Logic (2): D Latch

 
- ❖ *The current design CANNOT latch the D value*
- ❖ How to solve this issue?
 - ❖ Adding an *Enable*
- ❖ Truth table



Sequential Logic (2): D Latch



- ❖ *The current design CANNOT latch the D value*
- ❖ How to solve this issue?
 - ❖ Adding an *Enable*
- ❖ Truth table

E	D	Q	$\sim Q$
1	0		
0	1		
0	1		
0	0		

 



Sequential Logic (2): D Latch

  - ❖ Replacing Enable with **CLK** (clock)



Sequential Logic (2): D Latch

  - ❖ Replacing Enable with **CLK** (clock)



CLK	D	\bar{D}	S	R	Q	\bar{Q}
0	X	\bar{X}	0	0	Q_{prev}	\bar{Q}_{prev}
1	0	1	0	1	0	1
1	1	0	1	0	1	0

Level-Sensitive and Edge-Sensitive

- ❖ Left: will block until there is a change in the value of a or b
- ❖ Right: will block until clk transitions from 0 to 1.

```
always   @ (a or b or sel)
begin
    y = 0;
    if (sel == 0) begin
        y = a;
    end else begin
        y = b;
    end
end
```

```
always   @ (posedge clk )
if (reset == 0) begin
    y <= 0;
end else if (sel == 0) begin
    y <= a;
end else begin
    y <= b;
end
```

D Latch in Verilog

- ❖ `module dlatchmod(e, d, q);`
 - ❖ `input e;`
 - ❖ `input d;`
 - ❖ `output q;`
 - ❖ `reg q;`
 - ❖ `always @(e or d)`
 - ❖ `begin`
 - ❖ `if (e)`
 - ❖ `q<=d;`
 - ❖ `end`
- ❖ `endmodule`

Sequential Logic (3): D Flip-flop


❖ Sequential circuit is edge-sensitive!

❖ Truth table

❖ CLK = 0, first transparent

❖ CLK = 1, second transparent

CLK	D	N1	Q	$\sim Q$
0				
1				
0				
1				

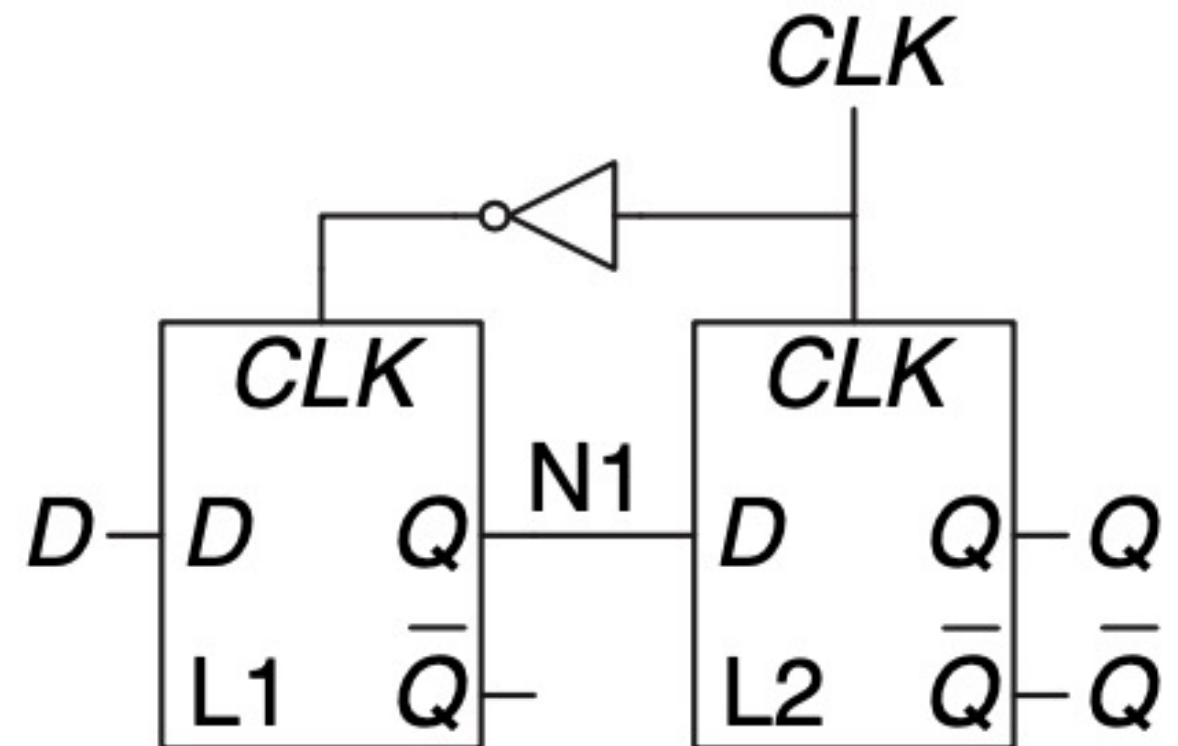

Sequential Logic (3): D Flip-flop


❖ Sequential circuit is edge-sensitive!

❖ Truth table

❖ CLK = 0, first transparent

❖ CLK = 1, second transparent

CLK	D	N1	Q	$\sim Q$
0				
1				
0				
1				

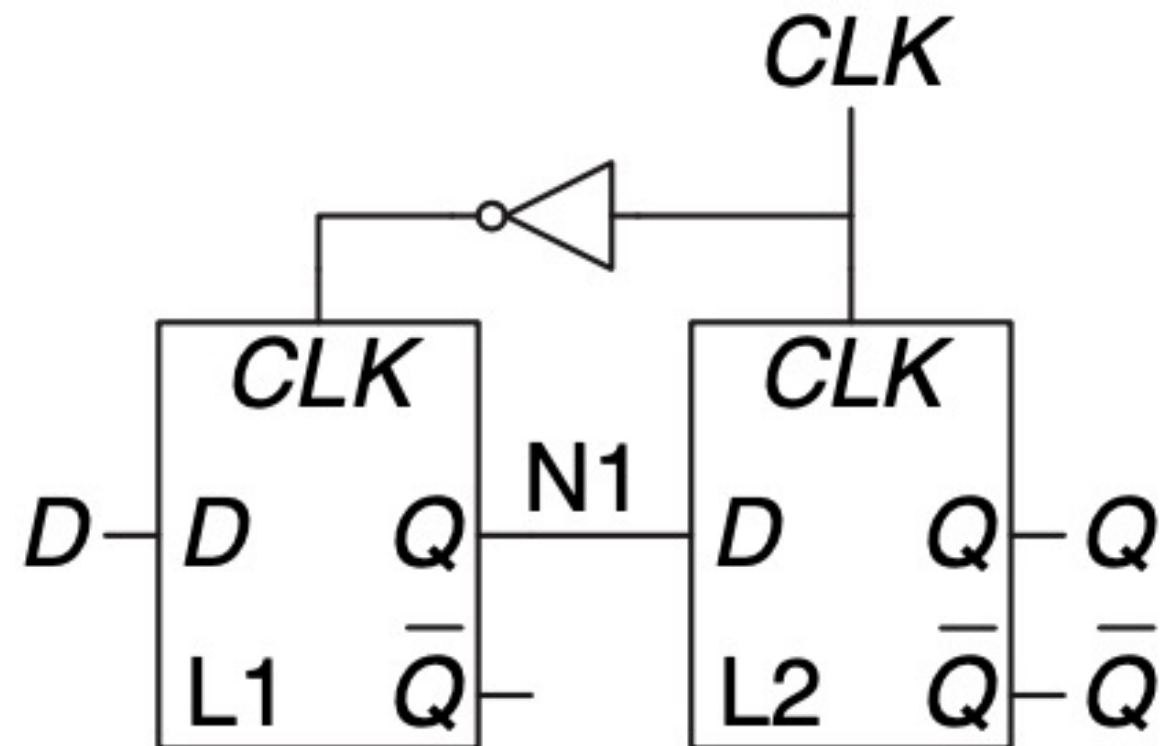


A D flip-flop copies D to Q on the rising edge of the clock, and remembers its state at all other times

D Flip-flop in Verilog

```
module RisingEdge_DFlipFlop(D,clk,Q);  
input D; // Data input  
input clk; // clock input  
output Q; // output Q  
always @(posedge clk)  
begin  
    Q <= D;  
end  
endmodule
```



Sequential Logic (4): Enabled Flip-flop

 - ❖ How to implement?
- ❖ Lets analyze what we want
 - ❖ EN is true, ordinary D Flip-flop
 - ❖ EN is false, value retained





Sequential Logic (4): Enabled Flip-flop

  - ❖ How to implement?
- ❖ Lets analyze what we want
 - ❖ EN is true, ordinary D Flip-flop
 - ❖ EN is false, value retained




Sequential Logic (4): Enabled Flip-flop

  - ❖ How to implement?
- ❖ Lets analyze what we want
 - ❖ EN is true, ordinary D Flip-flop
 - ❖ EN is false, value retained




Sequential Logic (5): Resettable Flip-flop

- ❖ Active-low reset signal

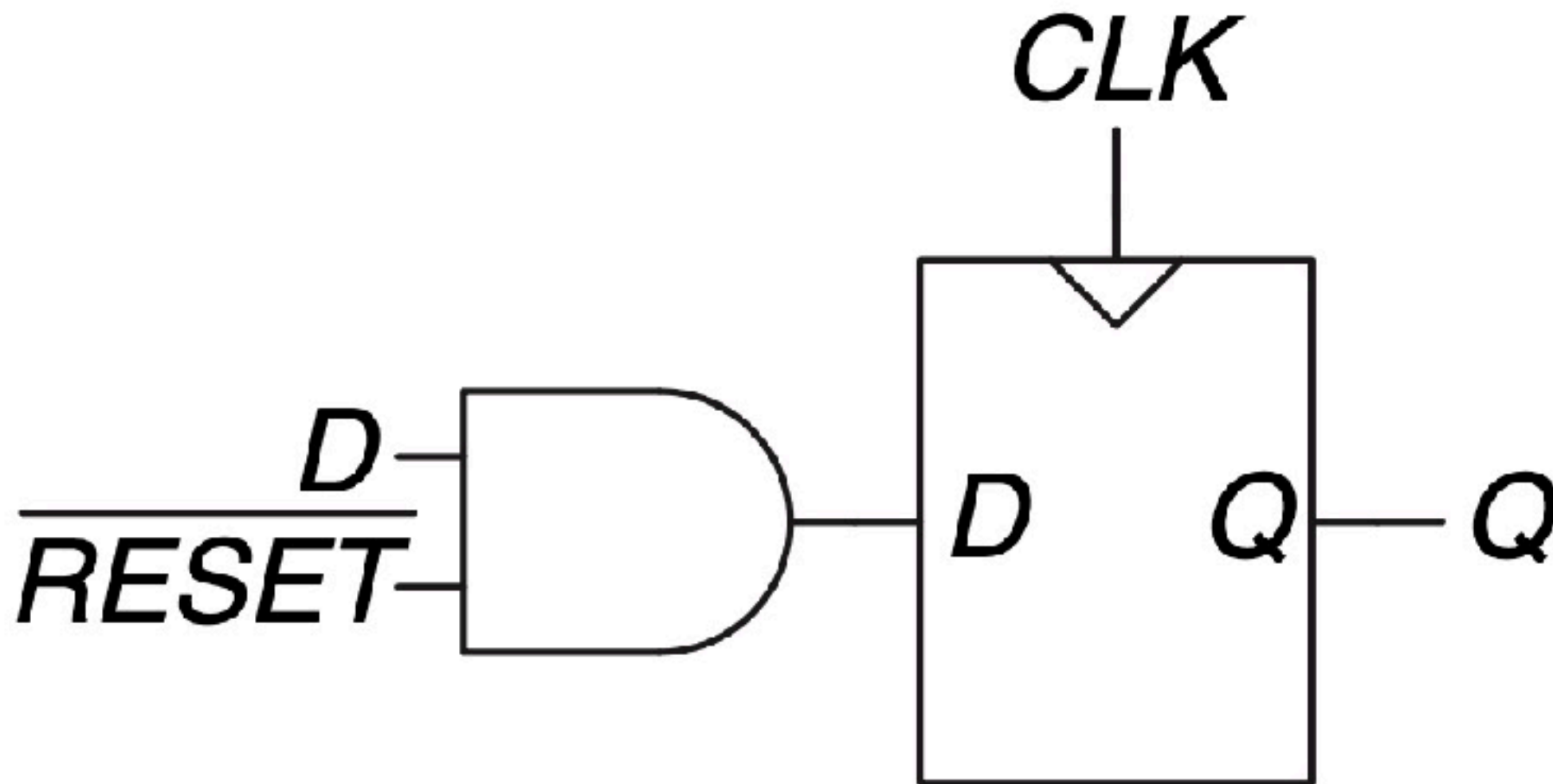

Sequential Logic (6): Register

 - ❖ Consists of N flip-flops
- ❖ Share a common CLK
 - ❖ All inputs updated at the same time
- ❖ 4-bit example



Register in Verilog

- ❖ *// positive edge-triggered 4-bit register*
- ❖ `module reg4 (CLK,Q,D,RST);`
- ❖ `input [3:0] D;`
- ❖ `input CLK, RST;`
- ❖ `output [3:0] Q;`
- ❖ `reg [3:0] Q;`
- ❖ `always @ (RST, posedge CLK)`
- ❖ `if (RST) Q <= 0; else Q <= D;`
- ❖ `endmodule // reg4`