

# EECE 2322: Fundamentals of Digital Design and Computer Organization


## Lecture 12\_3: Timing of Digital Systems

Xiaolin Xu

Department of ECE  
Northeastern University

 
# Synchronizers

- **Asynchronous inputs are inevitable** (user interfaces, systems with different clocks interacting, etc.)
- **Synchronizer goal:** make the probability of failure (the output  $Q$  still being metastable) low
- Synchronizer cannot make the probability of failure 0



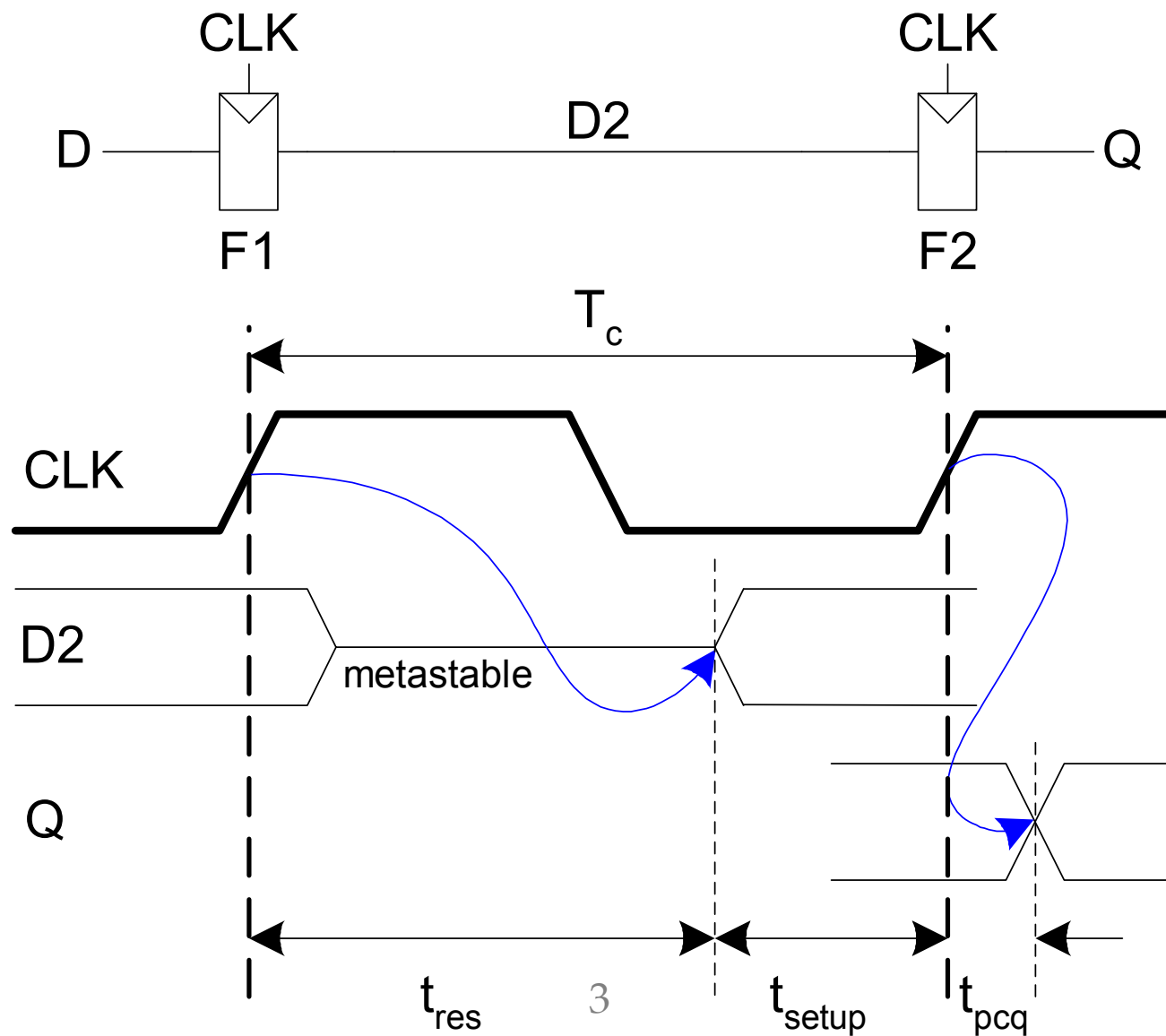
# Synchronizer Internals

- Synchronizer: built with two back-to-back flip-flops
- Suppose D is transitioning when sampled by F1
- Internal signal D2 has  $(T_c - t_{\text{setup}})$  time to resolve to 1 or 0




# Synchronizer Probability of Failure

 
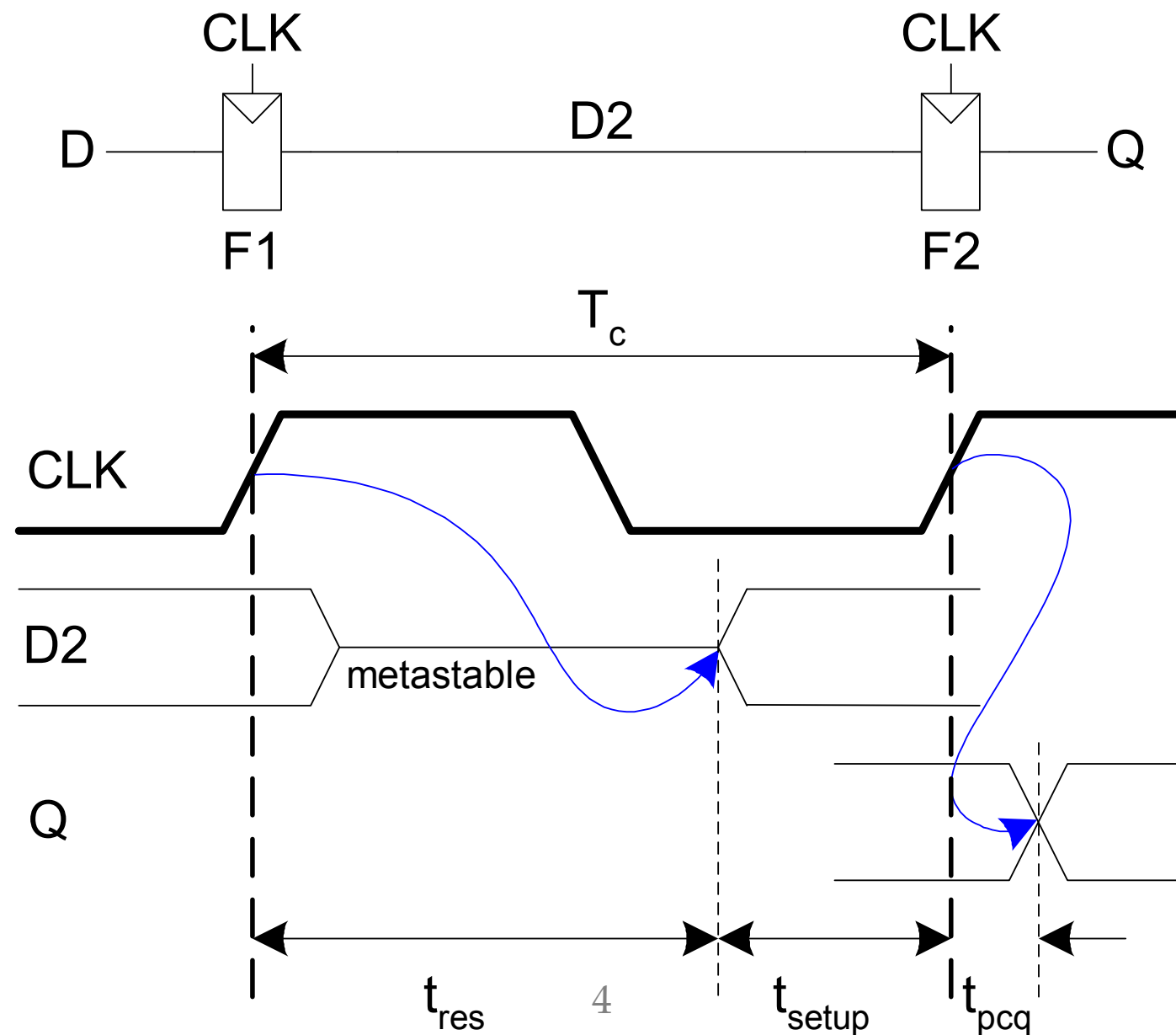
# Synchronizer Probability of Failure

$$P(t_{\text{res}} > t) = (T_0 / T_c) e^{-t/\tau}$$




# Synchronizer Probability of Failure

$$P(t_{\text{res}} > t) = (T_0 / T_c) e^{-t/\tau}$$

For each sample, probability of failure is:
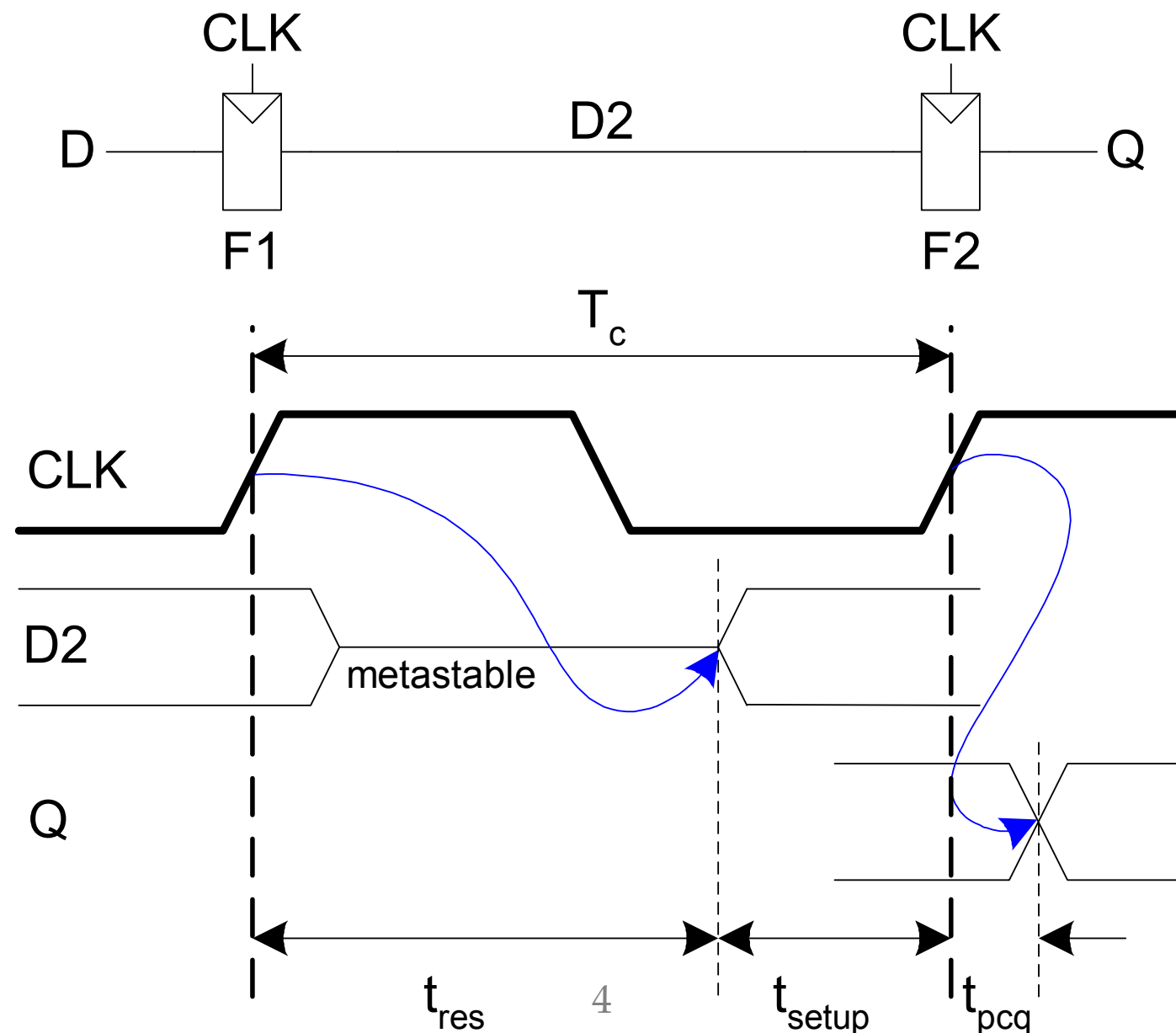
$$P(\text{failure}) = (T_0 / T_c) e^{-(T_c - t_{\text{setup}})/\tau}$$



# Synchronizer Mean Time Between Failures

- If asynchronous input changes once per second, probability of failure per second is  $P(\text{failure})$ .
- If input changes  $N$  times per second, probability of failure per second is:


$$P(\text{failure})/\text{second} = (NT_0/T_c) e^{-(T_c - t_{\text{setup}})/\tau}$$

- Synchronizer fails, on average,  $1/[P(\text{failure})/\text{second}]$
- Called *mean time between failures*, MTBF:

$$\text{MTBF} = 1/[P(\text{failure})/\text{second}] = (T_c/NT_0) e^{(T_c - t_{\text{setup}})/\tau}$$
 
# Example Synchronizer

- Suppose:  $T_c = 1/500 \text{ MHz} = 2 \text{ ns}$      $\tau = 200 \text{ ps}$   
 $T_0 = 150 \text{ ps}$      $t_{\text{setup}} = 100 \text{ ps}$   
 $N = 1 \text{ events per second}$
- What is the probability of failure? MTBF?






# Example Synchronizer

- Suppose:  $T_c = 1/500 \text{ MHz} = 2 \text{ ns}$      $\tau = 200 \text{ ps}$   
 $T_0 = 150 \text{ ps}$      $t_{\text{setup}} = 100 \text{ ps}$   
 $N = 1 \text{ events per second}$
- What is the probability of failure? MTBF?

Synchronizer fails, on average,  $1 / [P(\text{failure}) / \text{second}]$   
Called *mean time between failures*, MTBF:
 
$$\text{MTBF} = 1 / [P(\text{failure}) / \text{second}] = (T_c / NT_0) e^{(T_c - t_{\text{setup}}) / \tau}$$



# Example Synchronizer

- Suppose:  $T_c = 1/500 \text{ MHz} = 2 \text{ ns}$      $\tau = 200 \text{ ps}$

$$T_0 = 150 \text{ ps} \quad t_{\text{setup}} = 100 \text{ ps}$$


$$N = 1 \text{ events per second}$$

- What is the probability of failure? MTBF?

$$\begin{aligned} P(\text{failure}) &= (150 \text{ ps} / 2 \text{ ns}) e^{-(1.9 \text{ ns}) / 200 \text{ ps}} \\ &= \mathbf{5.6 \times 10^{-6}} \end{aligned}$$

$$\begin{aligned} P(\text{failure})/\text{second} &= 10 \times (5.6 \times 10^{-6}) \\ &= 5.6 \times 10^{-5} / \text{second} \end{aligned}$$
 
$$\text{MTBF} = 1/[P(\text{failure})/\text{second}] \approx \mathbf{5 \text{ hours}}$$



# EECE 2322: Fundamentals of Digital Design and Computer Organization


## Lecture 12\_3: Microarchitecture

Xiaolin Xu

Department of ECE  
Northeastern University
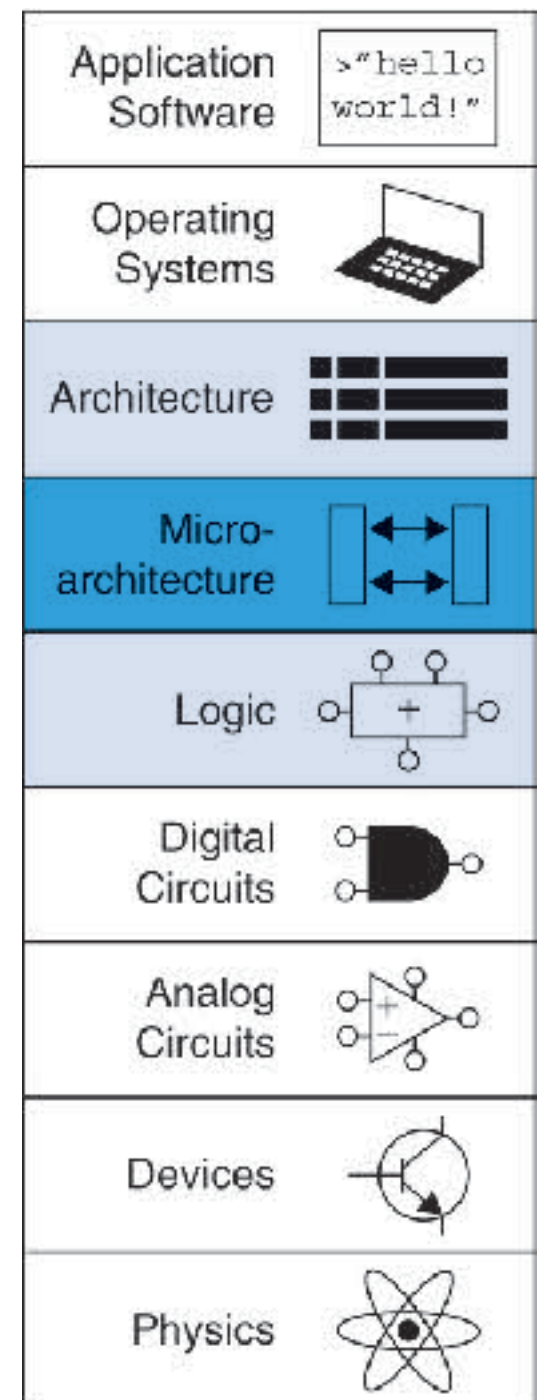
# Microarchitecture Topics

- ❖ Introduction
- ❖ Performance Analysis
- ❖ Single-Cycle Processor
- ❖ Multicycle Processor
- ❖ Pipelined Processor
- ❖ Exceptions
- ❖ Advanced Microarchitecture



# Microarchitecture

❖ **Microarchitecture:** how to implement an Instruction-Set Architecture (ISA) in hardware

❖ **Processor:**

❖ **Datapath:** functional blocks

❖ **Control:** control signals

Application Software	programs
Operating Systems	device drivers
Architecture	instructions registers
Micro-architecture	datapaths controllers
Logic	adders memories
Digital Circuits	AND gates NOT gates
Analog Circuits	amplifiers filters
Devices	transistors diodes
Physics	electrons

---

# Microarchitecture

---

- ❖ Multiple implementations for a single architecture:
  - ❖ **Single-cycle:** Each instruction executes in a single cycle
  - ❖ **Multicycle:** Each instruction is broken into series of shorter steps
  - ❖ **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once

---

# Processor Performance

---

- ❖ Program execution time

**Execution Time = (#instructions)(cycles/instruction)(seconds/cycle)**

- ❖ Definitions:

- ❖ CPI: Cycles / instruction
- ❖ clock period: seconds / cycle
- ❖ IPC: instructions / cycle = IPC

- ❖ Challenge is to satisfy constraints of:

- ❖ Cost
- ❖ Power
- ❖ Performance

---

# MIPS Processor

---

- ❖ Consider subset of MIPS instructions:
  - ❖ R-type instructions: and, or, add, sub, slt
  - ❖ Memory instructions: lw, sw
  - ❖ Branch instructions: beq



---

# Architectural State

---


- ❖ What determine everything about a processor:
  - ❖ PC
  - ❖ 32 registers
  - ❖ Memory

---
 
# MIPS State Elements

---

- ❖ PC: program counter —> the next instruction




---

# MIPS State Elements

---


- ❖ Instruction memory:

 

- ❖ Read (RD) port
  - ❖ 32-bit addr as input
  - ❖ 32-bit instruction as output

# MIPS State Elements


- ❖ Register file

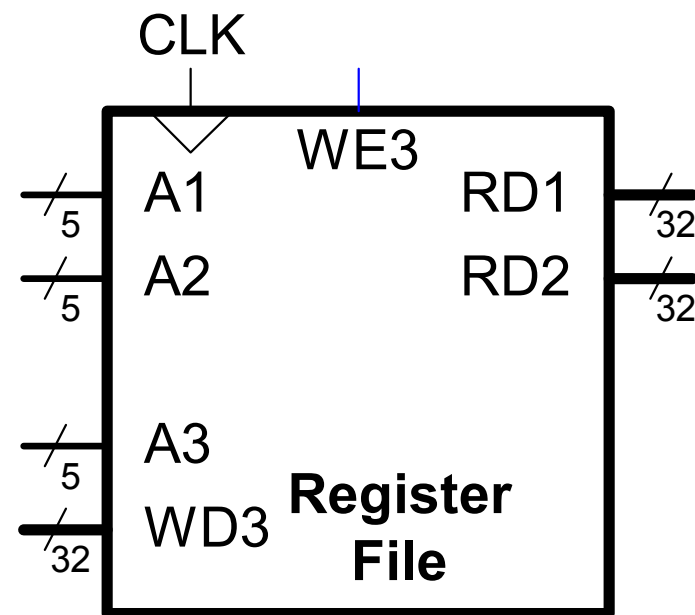

- ❖ Two read ports — RD1 / RD2
  - ❖ 5-bit address inputs A1 / A2 — selecting registers as source operands
- ❖ One write port — WD3, with enable signal WE3 (1 active)
  - ❖ 5-bit address input A3 —


# MIPS State Elements

- ❖ Data memory

 

- ❖ 32-bit address (A) as input, 32-bit write-in data (WD) input, with enable signal WE (1 active)
- ❖  $WE = 0$  — reading the data predicted by address A

# MIPS State Elements

 

- ❖ Instruction memory, register file, and data memory, are being **read** as combinational circuit, i.e., data change follows address change, while the writing follows clock-edge
- ❖ **Benefits:** all elements are synchronized, while MIPS processor is a FSM!

---

# Single-Cycle MIPS Processor

---

- ❖ Datapath
- ❖ Control

# Overview: Single-Cycle Control

## R-Type


op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

## I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

## J-Type

op	addr
6 bits	26 bits

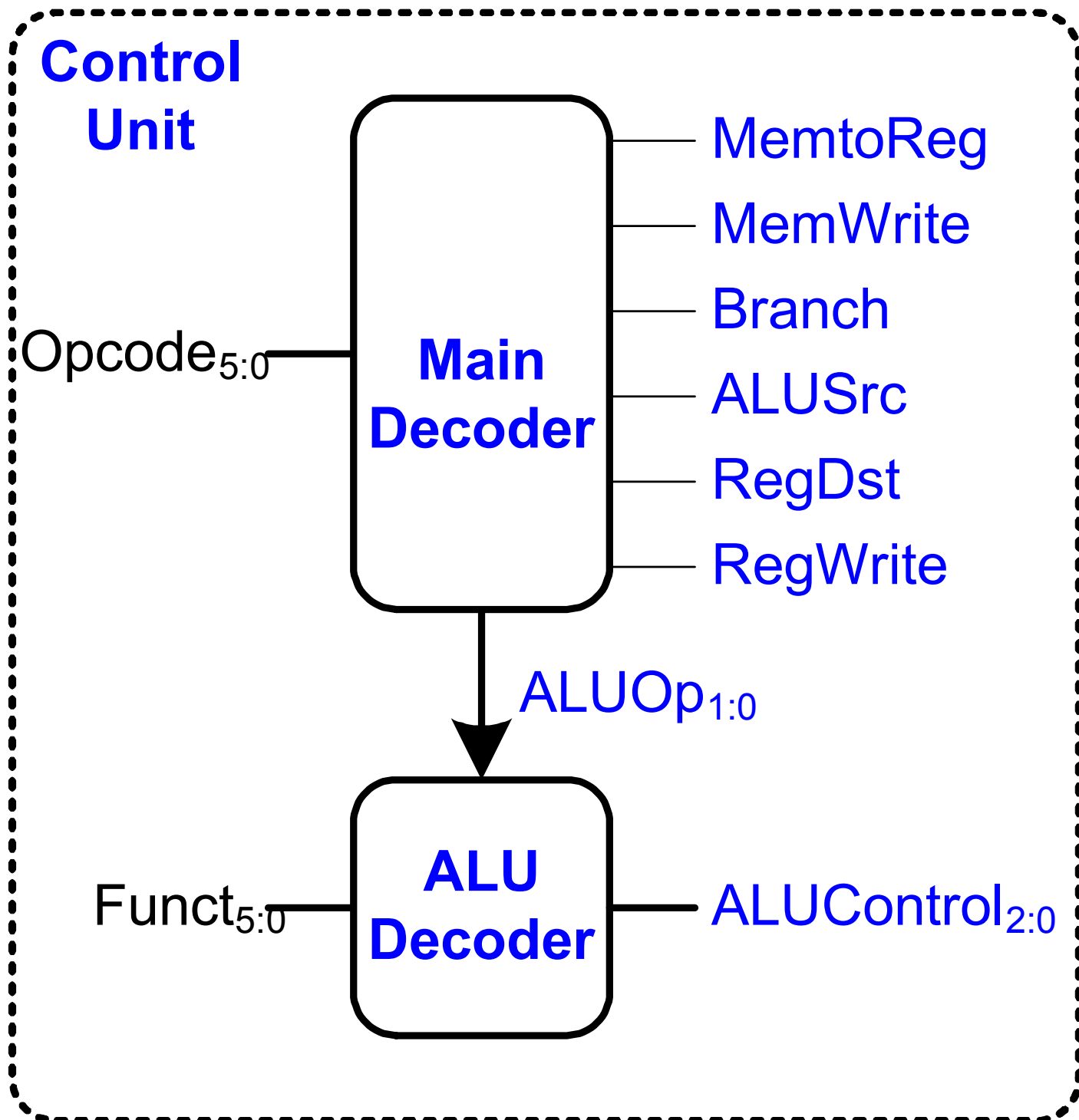



---

# Single-Cycle Datapath Example: lw fetch

---


# Revisit: Practice of I-type

`lw $s3, -24($s4)`


`lw` has opcode of 35

Name	Number
\$0	0
\$at	1
\$v0-\$v1	2-3
\$a0-\$a3	4-7
\$t0-\$t7	8-15
\$s0-\$s7	16-23
\$t8-\$t9	24-25
\$k0-\$k1	26-27
\$gp	28
\$sp	29
\$fp	30
\$ra	31

## Field Values

 

## Machine Code

 

# Revisit: Practice of I-type

`lw $s3, -24($s4)`


`lw` has opcode of 35

Name	Number
\$0	0
\$at	1
\$v0-\$v1	2-3
\$a0-\$a3	4-7
\$t0-\$t7	8-15
\$s0-\$s7	16-23
\$t8-\$t9	24-25
\$k0-\$k1	26-27
\$gp	28
\$sp	29
\$fp	30
\$ra	31

## Field Values

op	rs	rt	imm
35	20	19	-24
6 bits	5 bits	5 bits	16 bits

## Machine Code

 

# Revisit: Practice of I-type

lw \$s3, -24(\$s4)

lw has opcode of 35

Name	Number
\$0	0
\$at	1
\$v0-\$v1	2-3
\$a0-\$a3	4-7
\$t0-\$t7	8-15
\$s0-\$s7	16-23
\$t8-\$t9	24-25
\$k0-\$k1	26-27
\$gp	28
\$sp	29
\$fp	30
\$ra	31

## Field Values

op	rs	rt	imm
35	20	19	-24
6 bits	5 bits	5 bits	16 bits

## Machine Code


op	rs	rt	imm	
100011	10100	10011	1111 1111 1110 1000	(0x8E93FFE8)
8	E	9	3	F F E 8

# Single-Cycle Datapath Example: lw fetch


## STEP 1: Fetch instruction

lw \$s3, -24(\$s4)

lw has opcode of 35

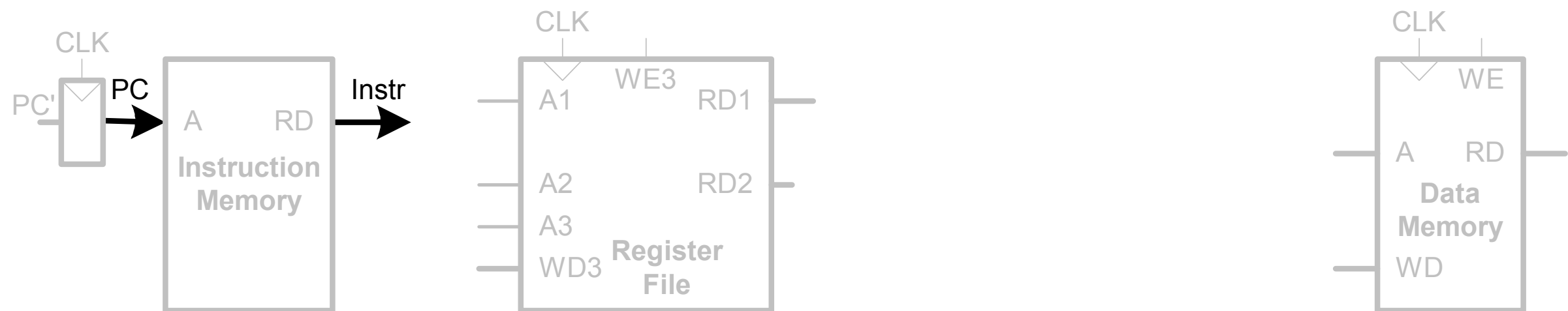

## Field Values

 


# Single-Cycle Datapath Example: lw fetch

## STEP 1: Fetch instruction

lw \$s3, -24(\$s4)

lw has opcode of 35

 

## Field Values


op	rs	rt	imm
35	20	19	-24
6 bits	5 bits	5 bits	16 bits

# Single-Cycle Datapath Example: lw fetch

## STEP 1: Fetch instruction

lw \$s3, -24(\$s4)

lw has opcode of 35

 

The offset is stored in the immediate field of the instruction, Instr<sub>15:0</sub>


### Field Values

op	rs	rt	imm
35	20	19	-24
6 bits	5 bits	5 bits	16 bits


# Single-Cycle Datapath: lw Register Read

## STEP 2: Read source operands from RF

`lw $s3, -24($s4)`

 

### Field Values

 




# Single-Cycle Datapath: lw Register Read

## STEP 2: Read source operands from RF

`lw $s3, -24($s4)`

 


### Field Values

op	rs	rt	imm
35	20	19	-24
6 bits	5 bits	5 bits	16 bits

# Single-Cycle Datapath: lw Immediate

## STEP 3: Sign-extend the immediate


`lw $s3, -24($s4)`

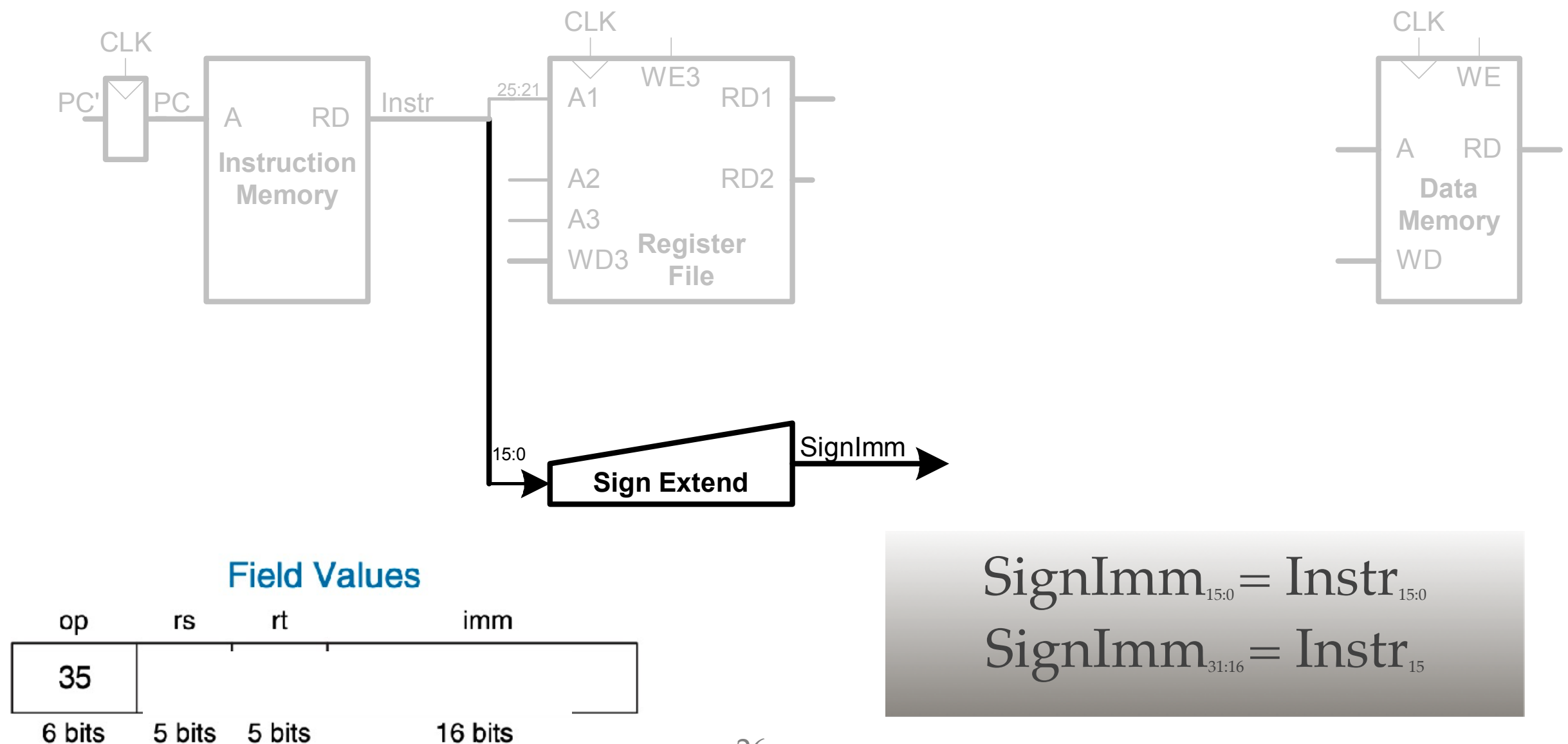

# Single-Cycle Datapath: lw address

## STEP 4: Compute the memory address

lw \$s3, -24(\$s4)

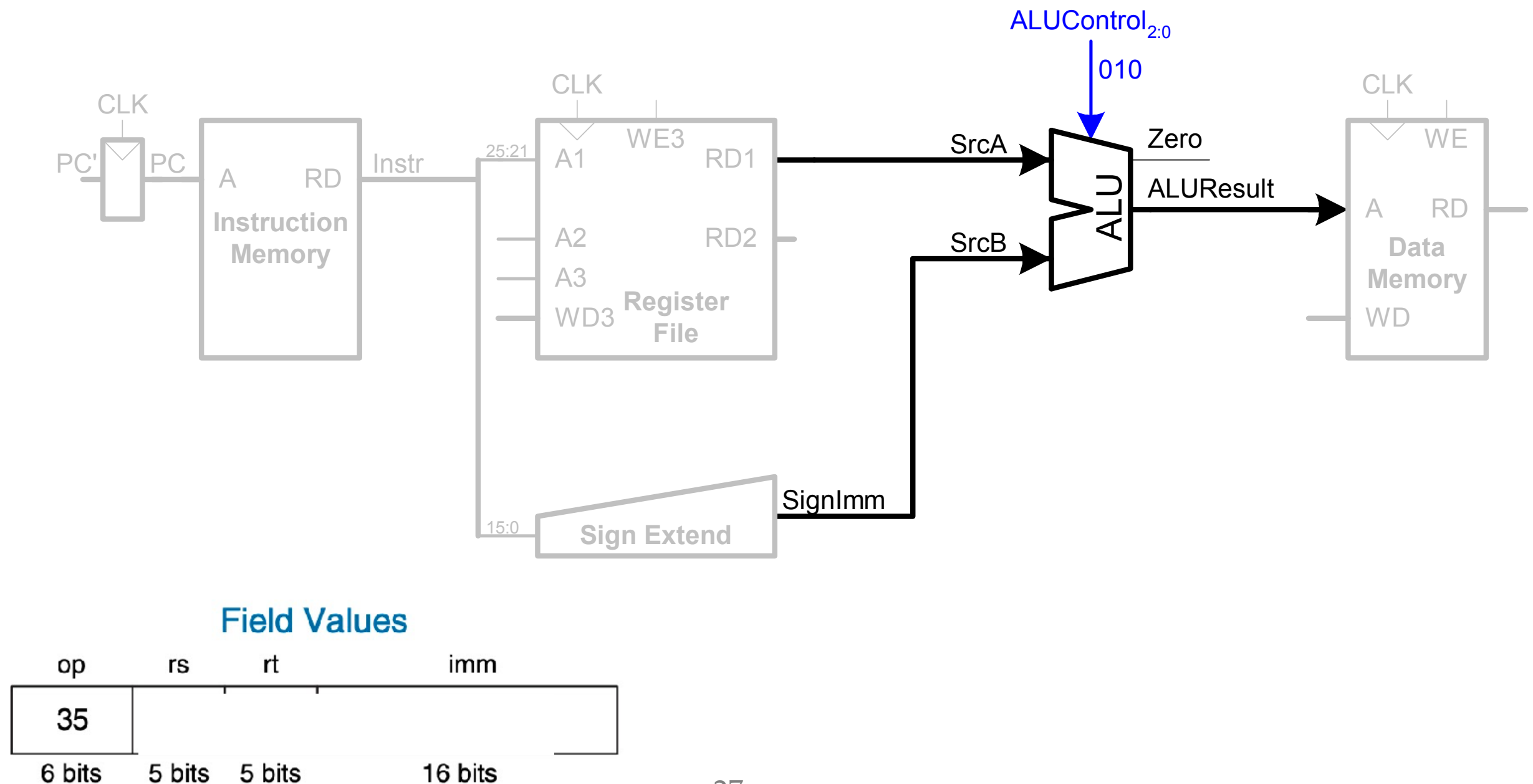


# Single-Cycle Datapath: lw address
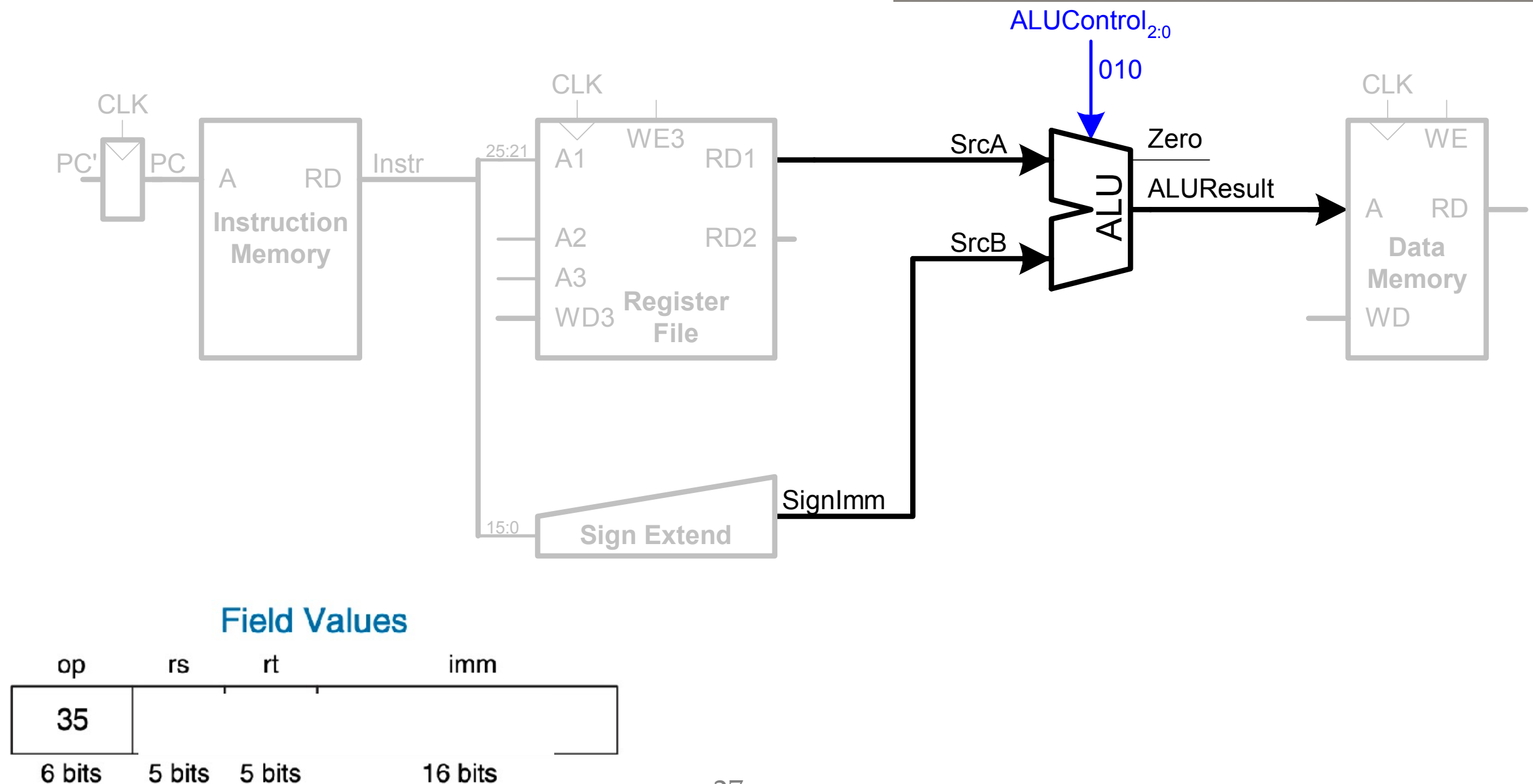
## STEP 4: Compute the memory address

lw \$s3, -24(\$s4)

add the base address to the offset to find the address to read from memory




# Single-Cycle Datapath: lw address
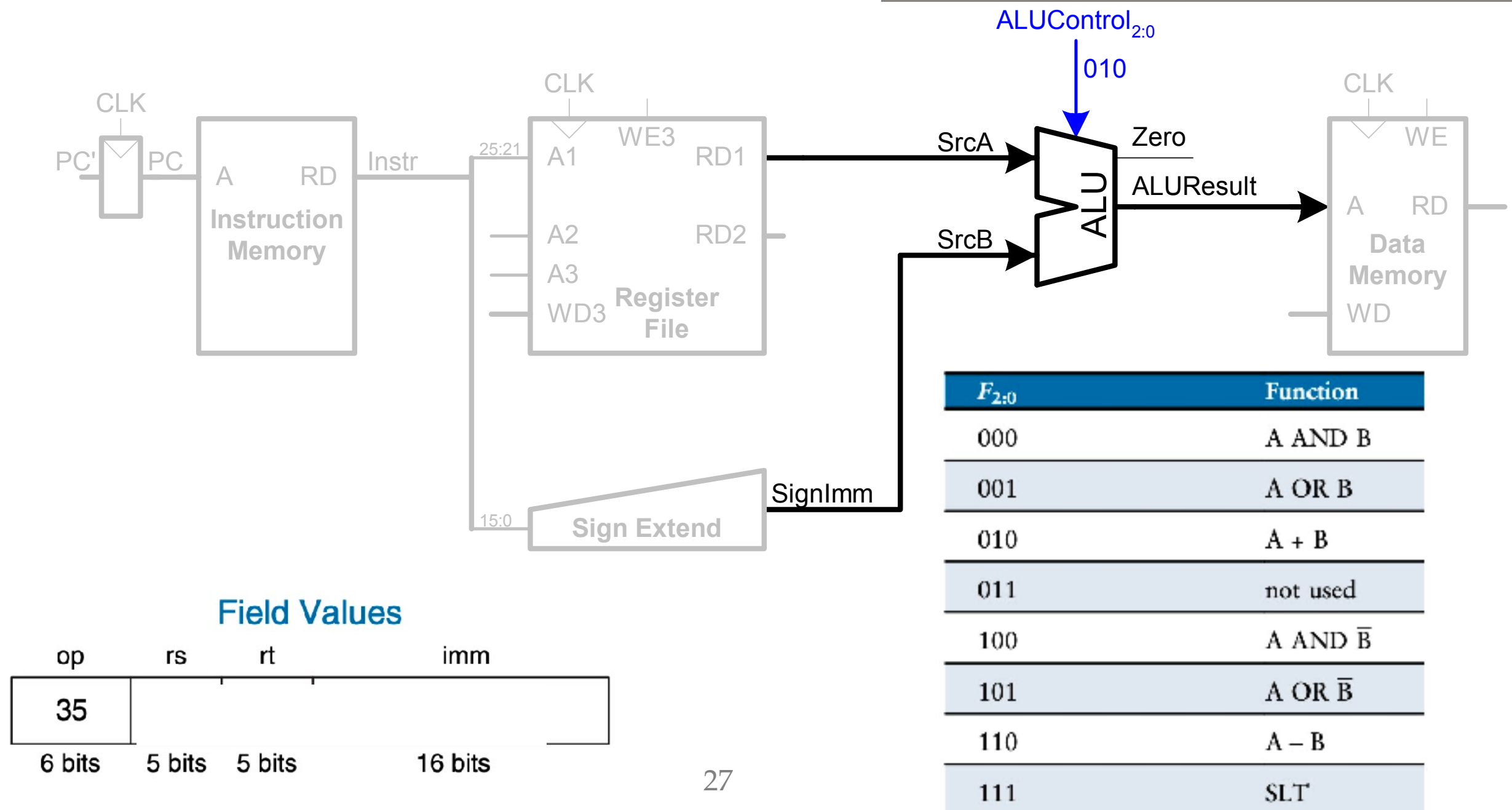
## STEP 4: Compute the memory address

lw \$s3, -24(\$s4)

add the base address to the offset to find the address to read from memory



# Single-Cycle Datapath: lw Memory Read

- ❖ **STEP 5:** Read data from memory and write it back to register file

