



EECE 2322: Fundamentals of Digital Design and Computer Organization

Lecture 10_3: Finite State Machine

Xiaolin Xu
Department of ECE
Northeastern University

Sequential Logic

  - Sequential circuits: all circuits that aren't combinational
- A problematic circuit:




- No inputs and 1-3 outputs
- Un-stable circuit, always oscillating
- Period depends on the number of inverters and their delay
- It has a *cyclic path*: output fed back to input

Synchronous Sequential Logic Design

- Breaks cyclic paths by **inserting registers**
- Registers contain **state** of the system
- State changes at clock edge: system **synchronized** to the clock
- **Rules** of synchronous sequential circuit composition:
 - Every circuit element is either a register or a combinational circuit
 - At least one circuit element is a register
 - All registers receive the same clock signal
 - Every cyclic path contains at least one register
- Two common synchronous sequential circuits
 - Finite State Machines (FSMs)
 - Pipelines

Finite State Machine (FSM)

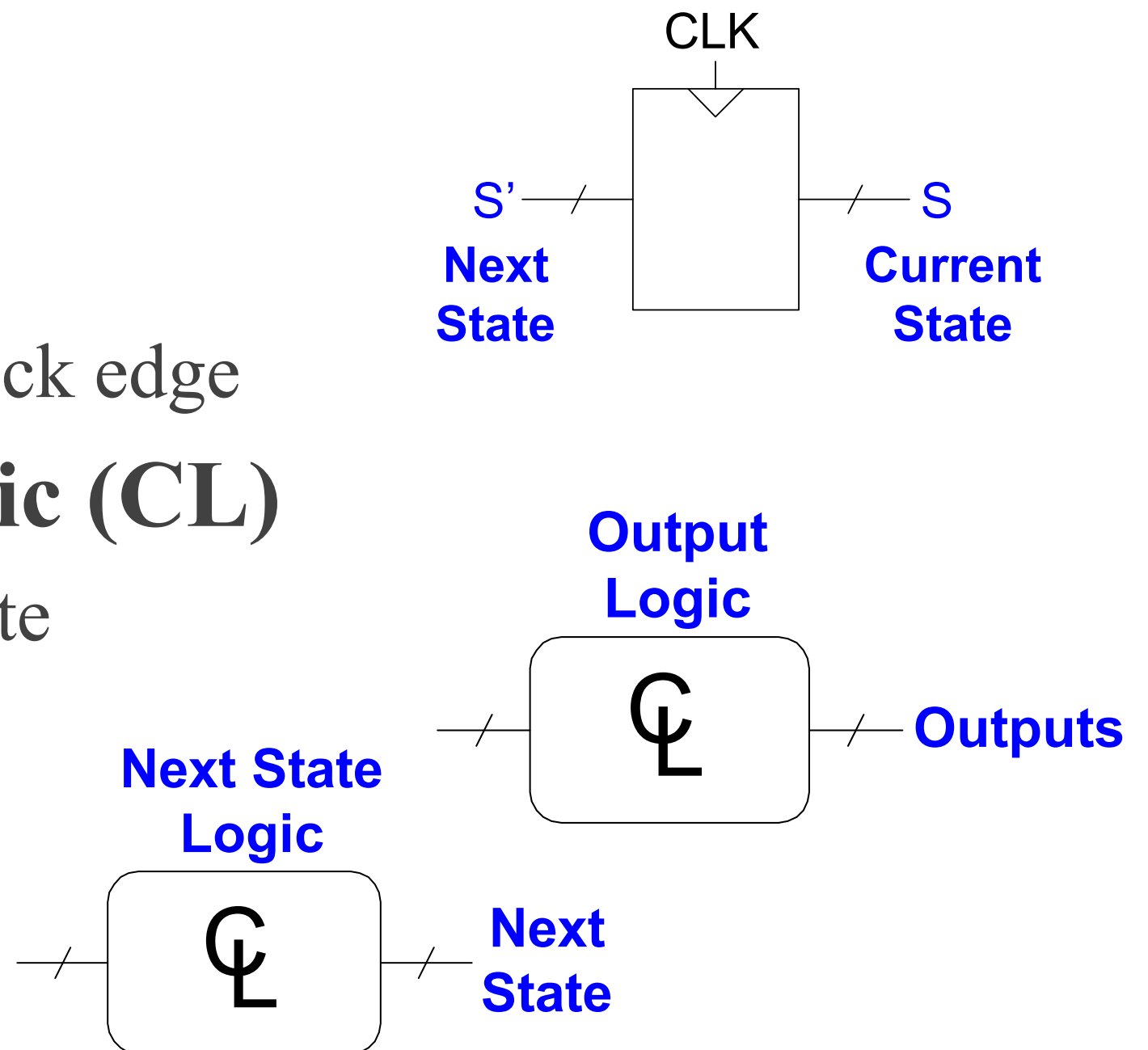
- Consists of:
 - **State register**
 - Stores current state
 - Loads next state at clock edge
 - **Combinational logic (CL)**
 - Computes the next state
 - Computes the outputs




Finite State Machines (FSMs)

- Next state determined by current state and inputs
- Two types of finite state machines differ in output logic:
 - **Moore FSM:** outputs depend **only on** current state
 - **Mealy FSM:** outputs depend on **current state *and* inputs**

Moore FSM

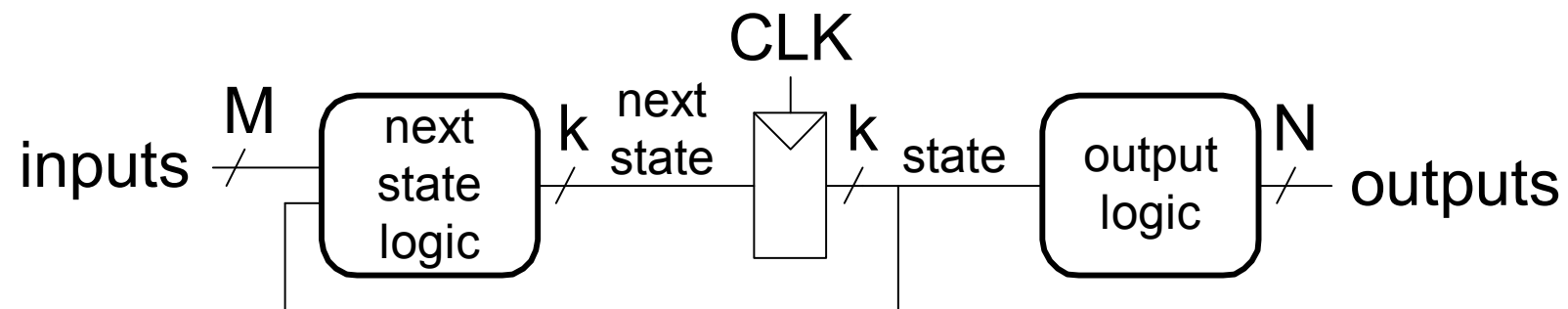


Mealy FSM

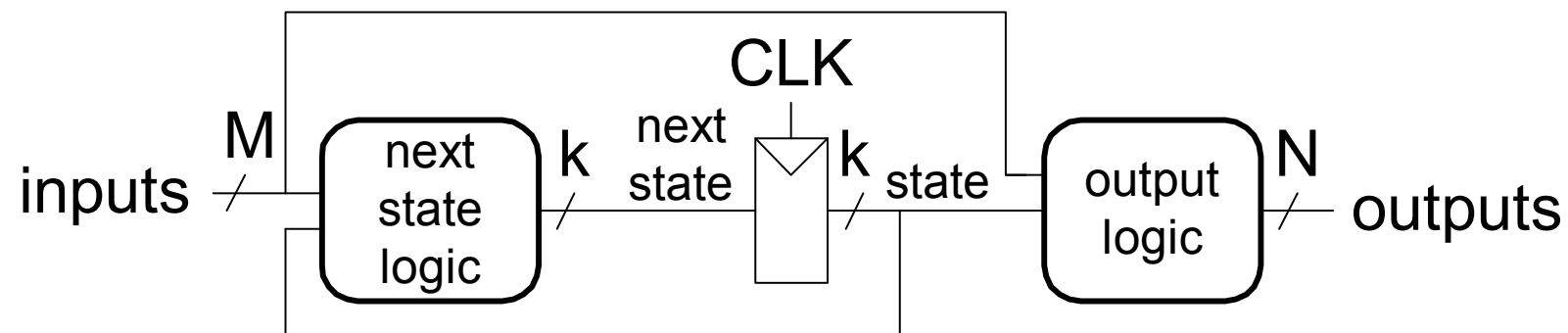


Moore State Machine

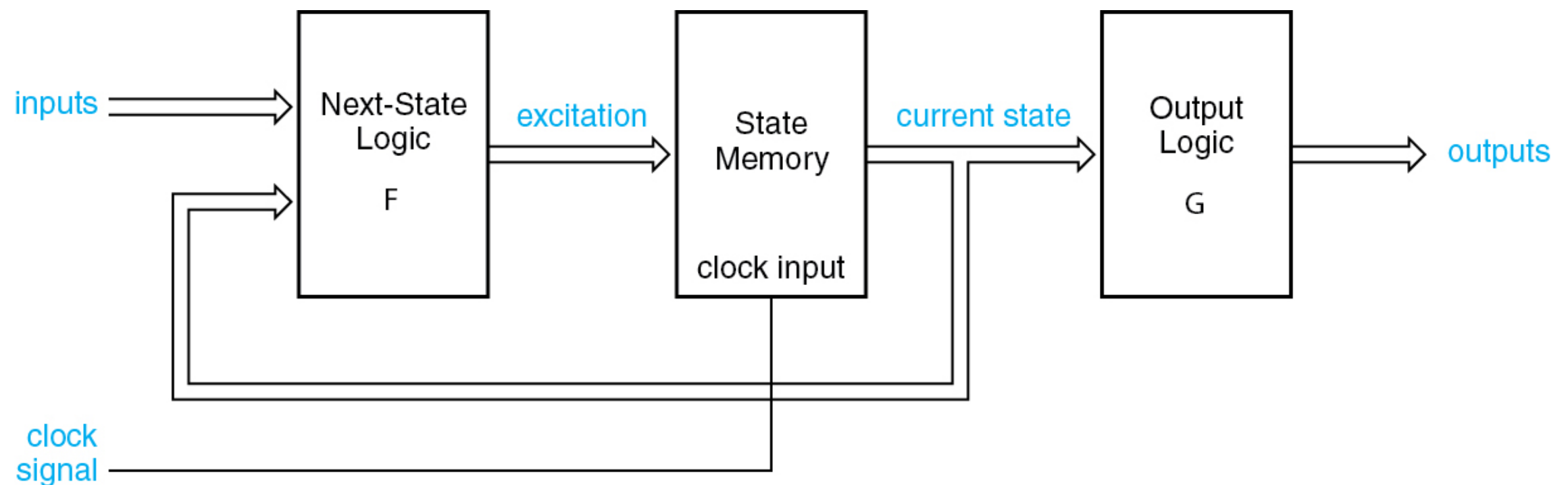❖ $\text{output} = G(\text{current state})$




Mealy State Machine

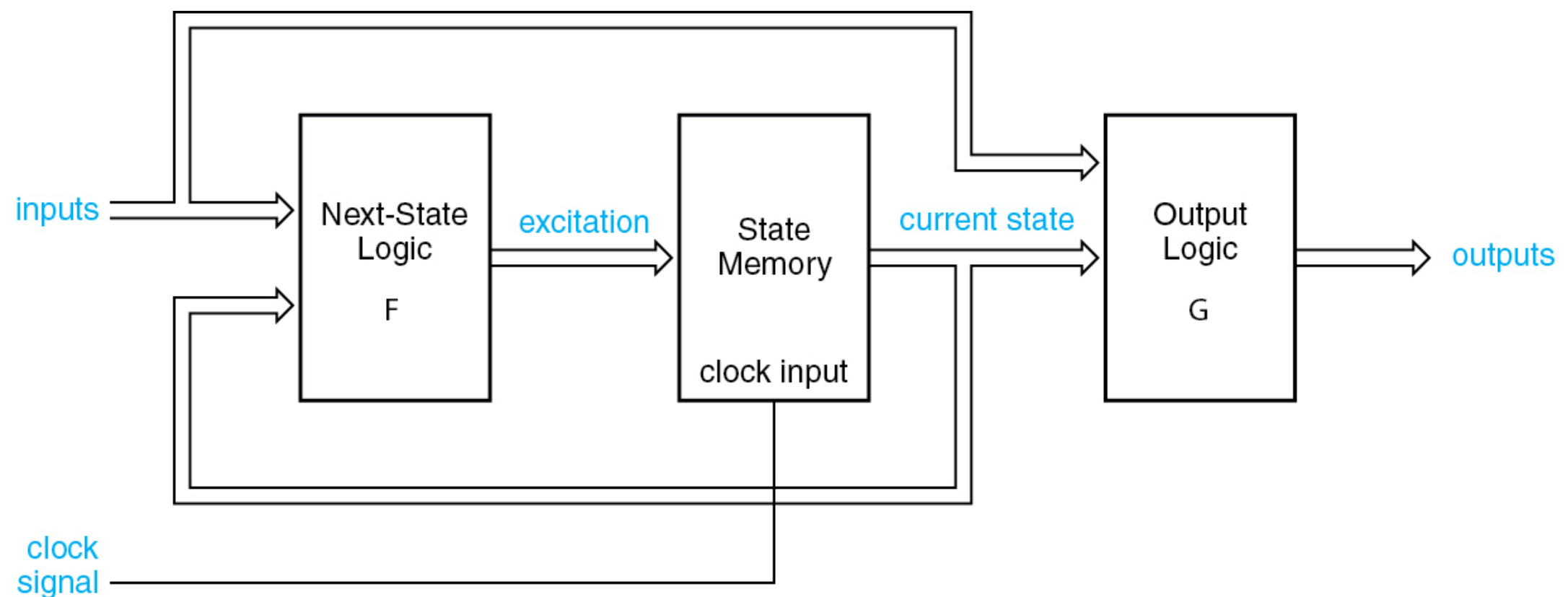- ❖ next state = $F(\text{input}, \text{current state})$
- ❖ output = $G(\text{input}, \text{current state})$




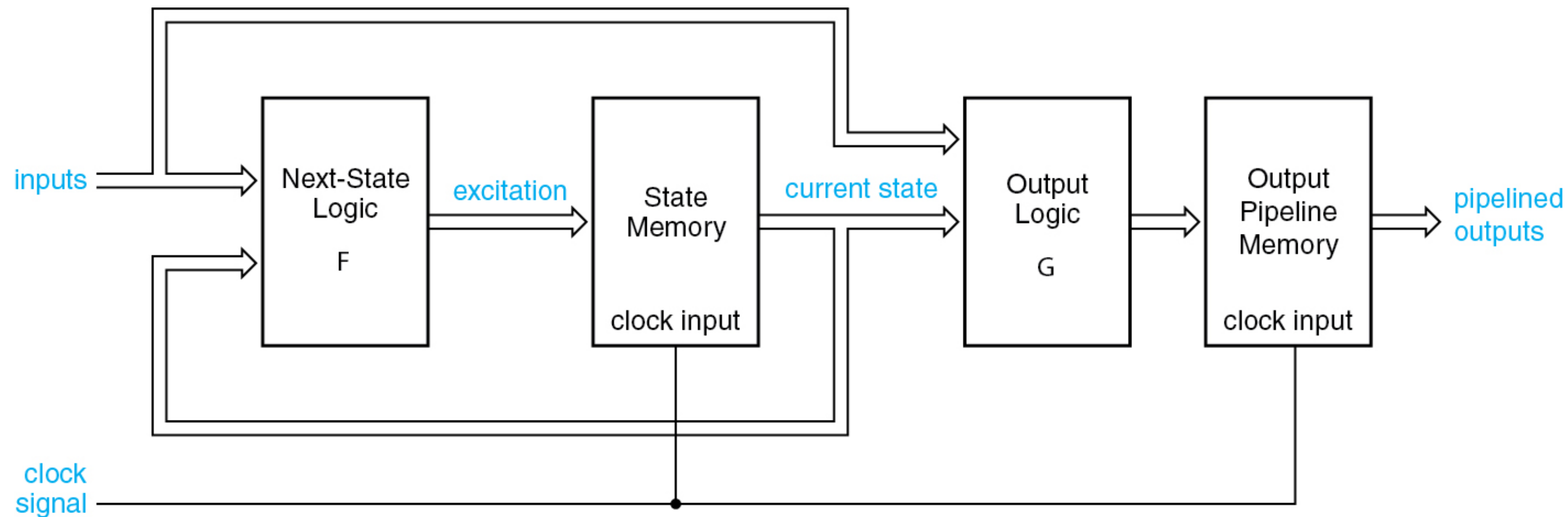Mealy State Machine with Pipelined Outputs




Revisiting an FSM Example

 - Traffic light controller
 - Traffic sensors: T_A , T_B (TRUE when there's traffic)
 - Lights: L_A , L_B




FSM Black Box

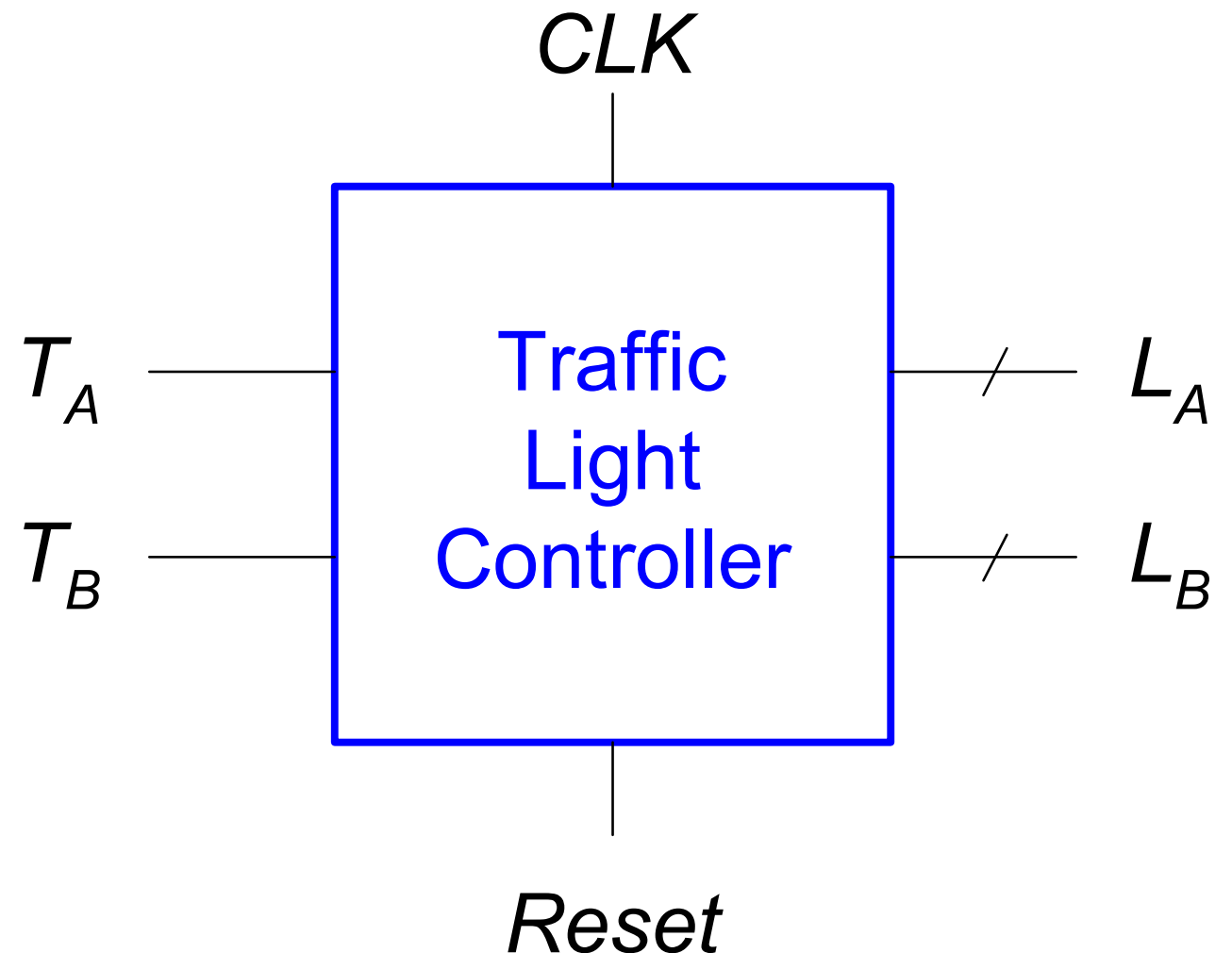- Inputs: CLK , $Reset$, T_A , T_B
- Outputs: L_A , L_B




FSM State Transition Diagram

 - **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs




FSM State Transition Diagram

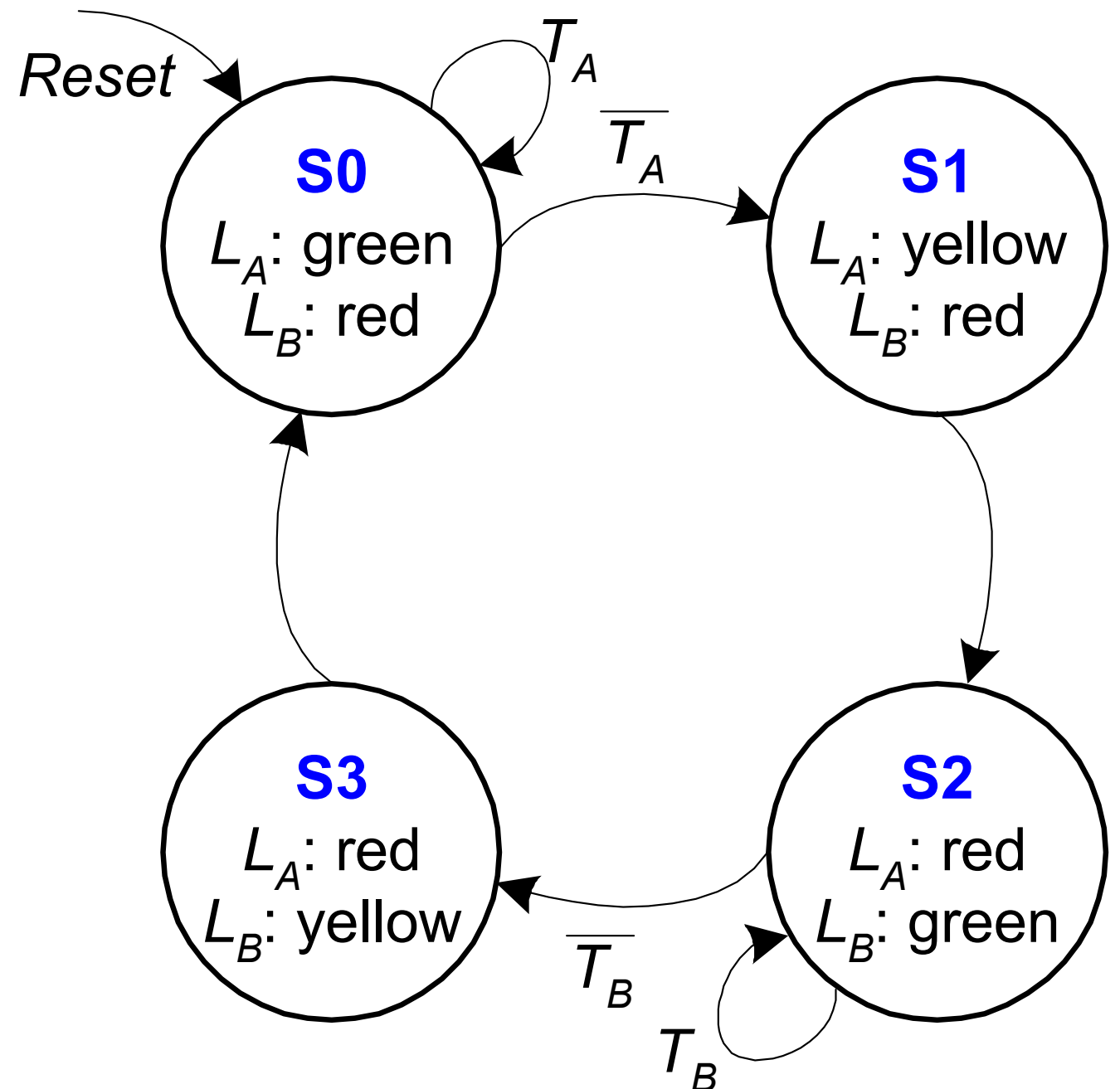- **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs




State Transition Table

 

Current State S	Inputs T_A T_B		Next State S'
S0	0	X	
S0	1	X	
S1	X	X	
S2	X	0	
S2	X	1	
S3	X	X	

FSM State Transition Table

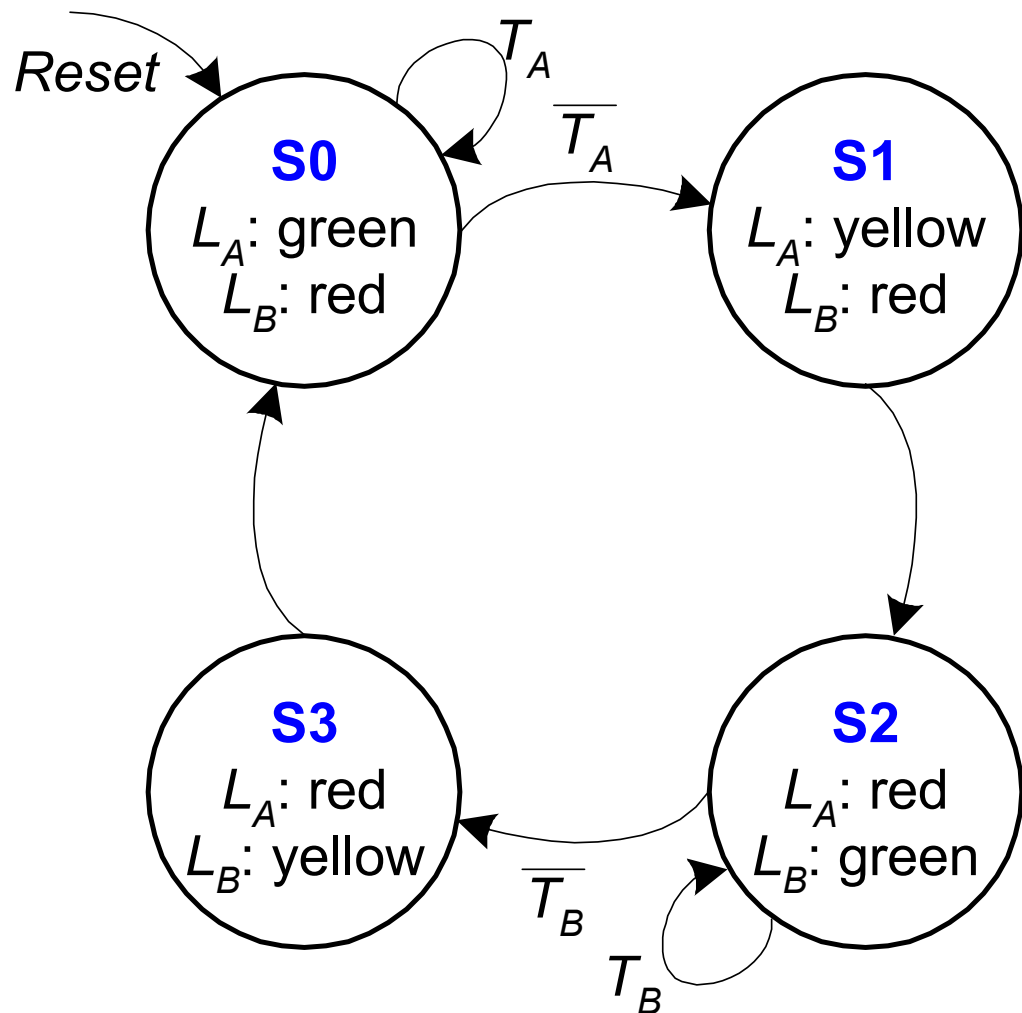

Current State S	Inputs T_A T_B		Next State S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

FSM Encoded State Transition Table

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X		
0	0	1	X		
0	1	X	X		
1	0	X	0		
1	0	X	1		
1	1	X	X		

State	Encoding
S0	00
S1	01
S2	10
S3	11

FSM Encoded State Transition Table

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

$$S'_1 = ?$$

$$S'_0 = ?$$

State	Encoding
S0	00
S1	01
S2	10
S3	11

FSM Encoded State Transition Table

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1} \overline{S_0} T_A + S_1 \overline{S_0} T_B$$

FSM Output Table

Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0				
0	1				
1	0				
1	1				

Output	Encoding
green	00
yellow	01
red	10

FSM Output Table


$$L_{A1} = S_1$$

$$L_{A0} = \overline{S_1}S_0$$

$$L_{B1} = \overline{S_1}$$

$$L_{B0} = S_1S_0$$


Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

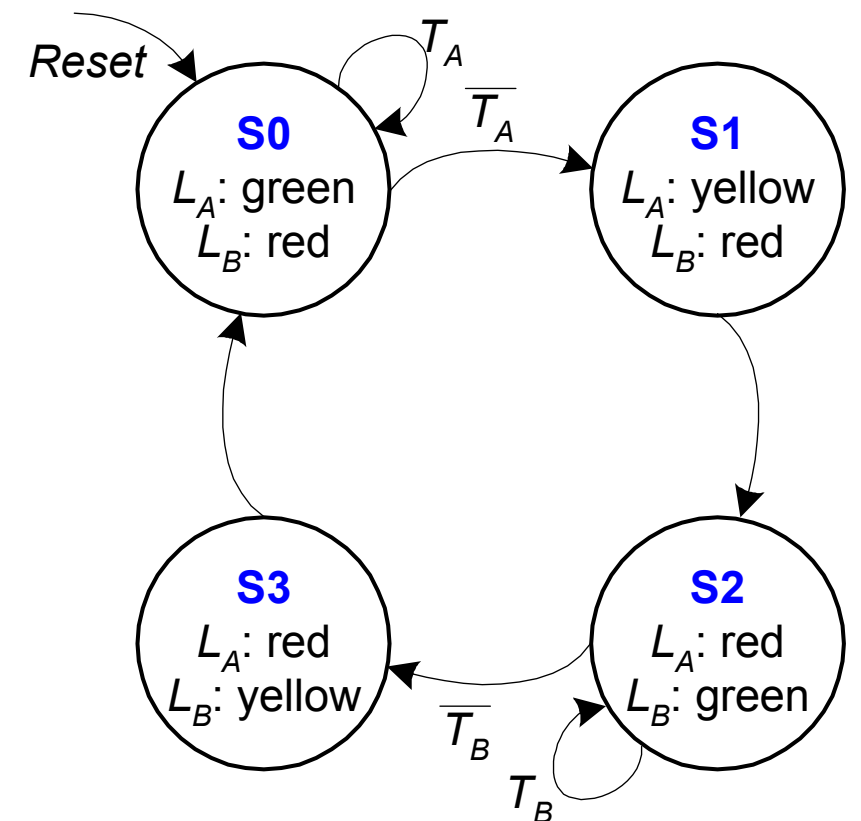

Output	Encoding
green	00
yellow	01
red	10

FSM Schematic: State Register
 
$$S'_1 = S_1 \oplus S_0$$
$$S'_0 = \overline{S_1} \overline{S_0} \overline{T_A} + S_1 \overline{S_0} \overline{T_B}$$




state register

FSM Schematic: Next State Logic


$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = S_1 S_0 T_A + S_1 S_0 T_B$$

 


$$\begin{aligned} L_{A1} &= S_1 \\ L_{A0} &= \overline{S_1} S_0 \\ L_{B1} &= \overline{S_1} \\ L_{B0} &= S_1 S_0 \end{aligned}$$



FSM Schematic: Output Logic

 

FSM Timing Diagram

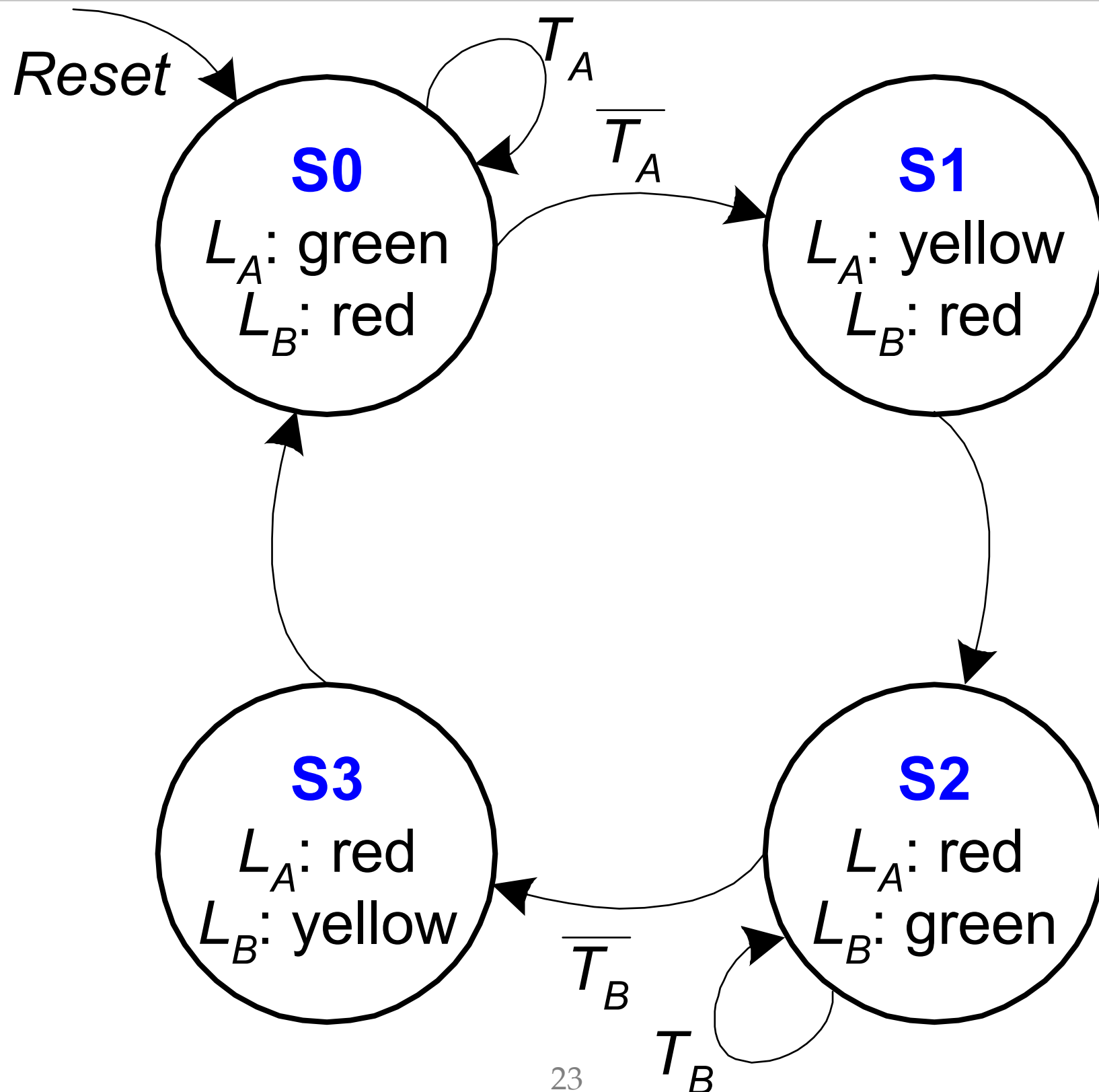

FSM Timing Diagram

  

FSM State Encoding Methods

- **Binary encoding:**
 - i.e., for four states, 00, 01, 10, 11
- **One-hot encoding**
 - One state bit per state
 - Only one state bit HIGH at once
 - i.e., for 4 states, 0001, 0010, 0100, 1000
 - Requires more flip-flops
 - Often next state and output logic is simpler