

# EECE 2322: Fundamentals of Digital Design and Computer Organization


## Lecture 12\_2: Timing of Digital Systems

Xiaolin Xu

Department of ECE  
Northeastern University

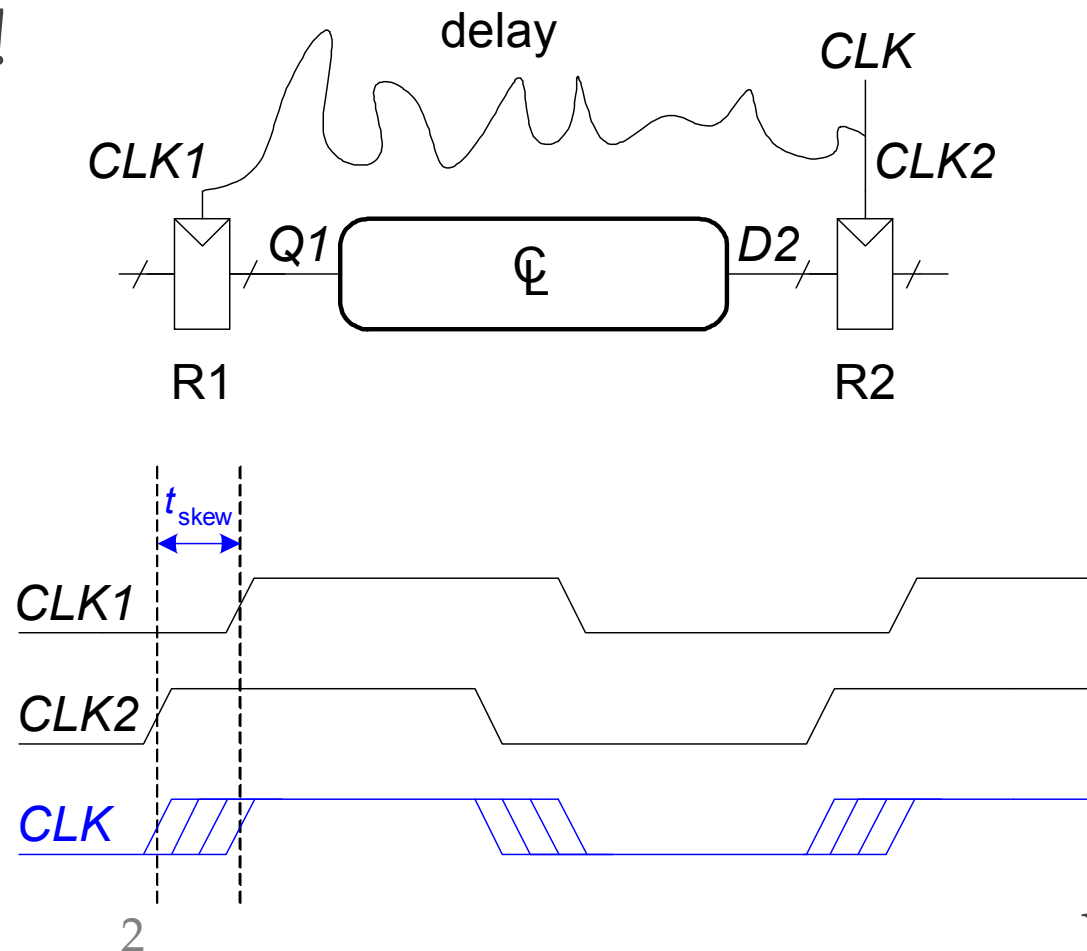
# Clock Skew

- ❖ The clock doesn't arrive at all registers at same time
- ❖ **Skew**: difference between two clock edges
- ❖ Perform **worst case analysis**
  - ❖ Guarantee dynamic discipline is not violated for any register – many registers in a system!



# Difficulties in Synchronous Design


## ❖ Clock-Skew Example

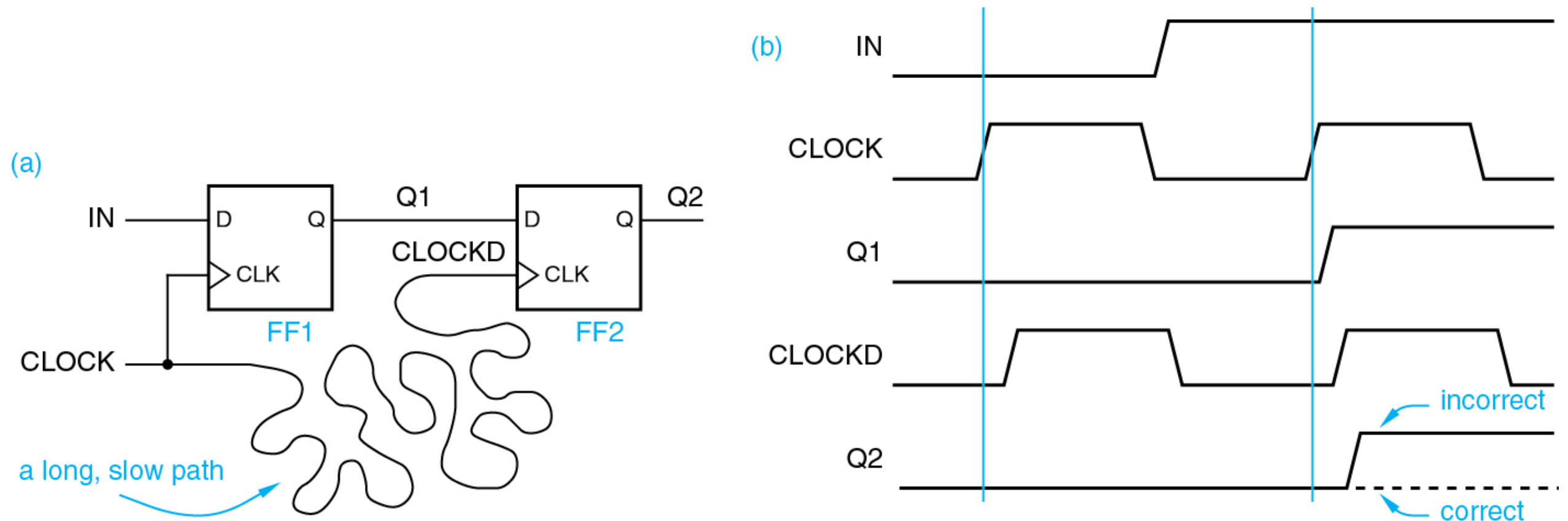

$$t_{\text{ffpd}(\text{min})} + t_{\text{comb}(\text{min})} - t_{\text{hold}} - t_{\text{skew}(\text{max})} > 0$$
 
# Setup Time Constraint with Skew

- ❖ In the worst case, CLK2 is earlier than CLK1




$$T_c \geq$$

$$T_c \geq t_{pcq} + t_{pd} + t_{setup}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{setup})$$
 
# Setup Time Constraint with Skew


- ❖ In the worst case, CLK2 is earlier than CLK1



$$T_c \geq$$
 
# Setup Time Constraint with Skew

- ❖ In the worst case, CLK2 is earlier than CLK1




$$T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$$

$$t_{pd} \leq$$

$$T_c \geq t_{pcq} + t_{pd} + t_{setup}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{setup})$$
 
# Setup Time Constraint with Skew

- ❖ In the worst case, CLK2 is earlier than CLK1




$$T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{setup} + t_{skew})$$

$$T_c \geq t_{pcq} + t_{pd} + t_{setup}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{setup})$$
 
# Hold Time Constraint with Skew

- ❖ In the worst case, CLK2 is later than CLK1




$$t_{ccq} + t_{cd} >$$


 
# Hold Time Constraint with Skew

- ❖ In the worst case, CLK2 is later than CLK1




$$t_{ccq} + t_{cd} >$$

$$t_{hold} < t_{ccq} + t_{cd}$$

$$t_{cd} > t_{hold} - t_{ccq}$$
 
# Hold Time Constraint with Skew

- ❖ In the worst case, CLK2 is later than CLK1




$$t_{ccq} + t_{cd} > t_{hold} + t_{skew}$$
$$t_{cd} >$$

$$t_{hold} < t_{ccq} + t_{cd}$$

$$t_{cd} > t_{hold} - t_{ccq}$$
 
# Hold Time Constraint with Skew

- ❖ In the worst case, CLK2 is later than CLK1




$$t_{ccq} + t_{cd} > t_{hold} + t_{skew}$$

$$t_{cd} > t_{hold} + t_{skew} - t_{ccq}$$

$$t_{hold} < t_{ccq} + t_{cd}$$


$$t_{cd} > t_{hold} - t_{ccq}$$
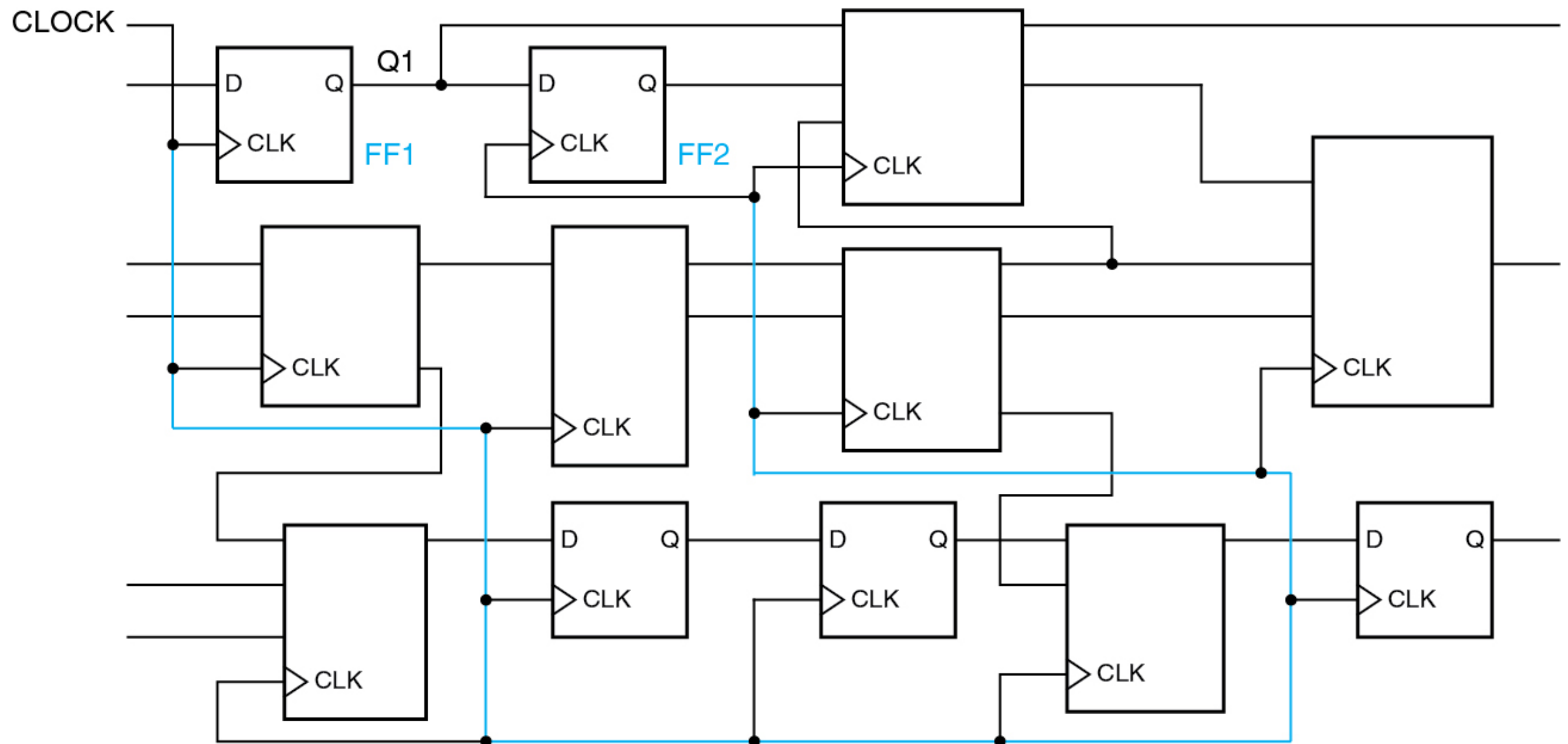
# A Clock-Signal Path Leading to Excessive Skew


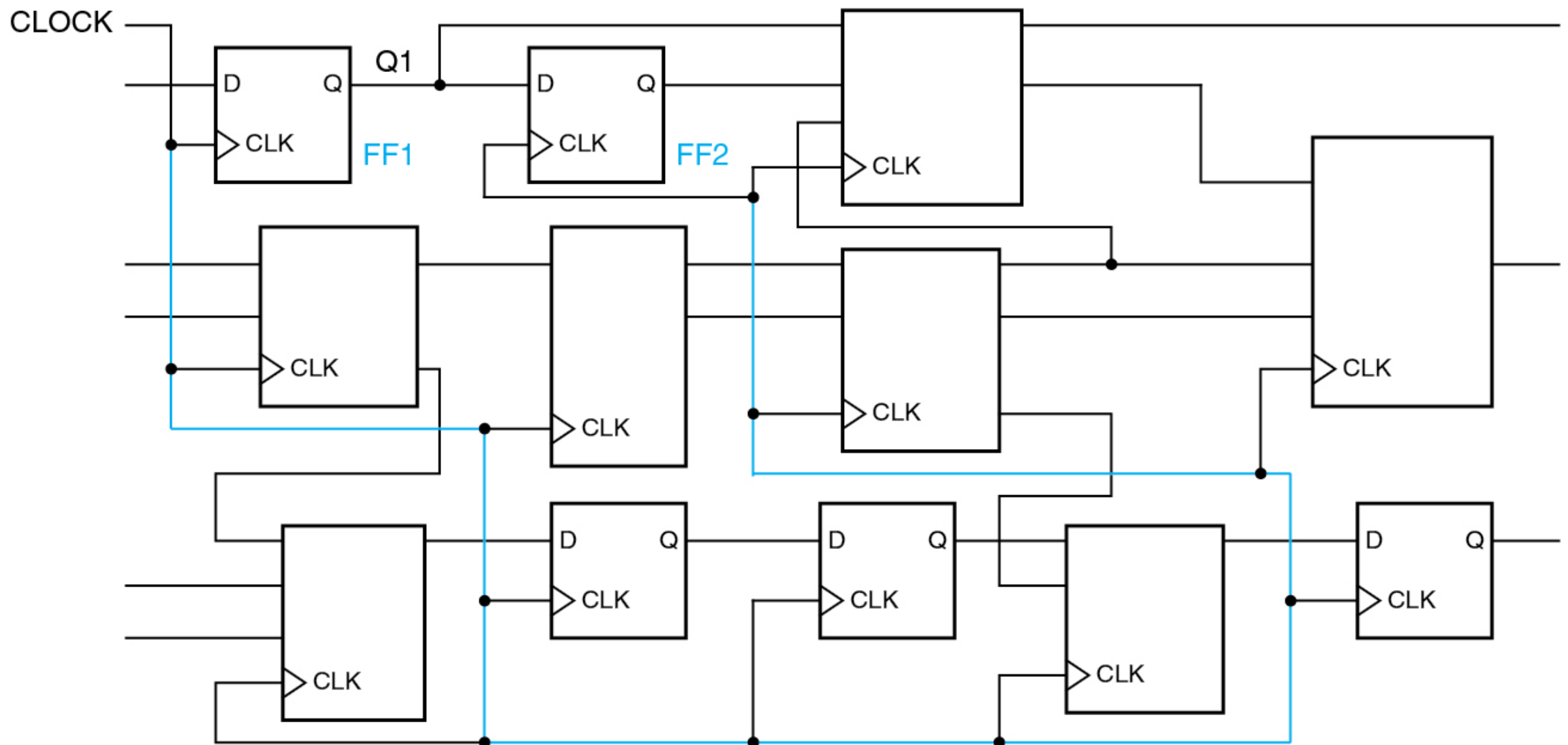
# A Clock-Signal Path Leading to Excessive Skew

- ❖ Problem: clock signal may arrive FF2 **much later!**



---


# Clock-Signal Routing to Minimize Skew

---

- ❖ Distributed, balanced, tree-like structure
- ❖ Fastest type of wire connection
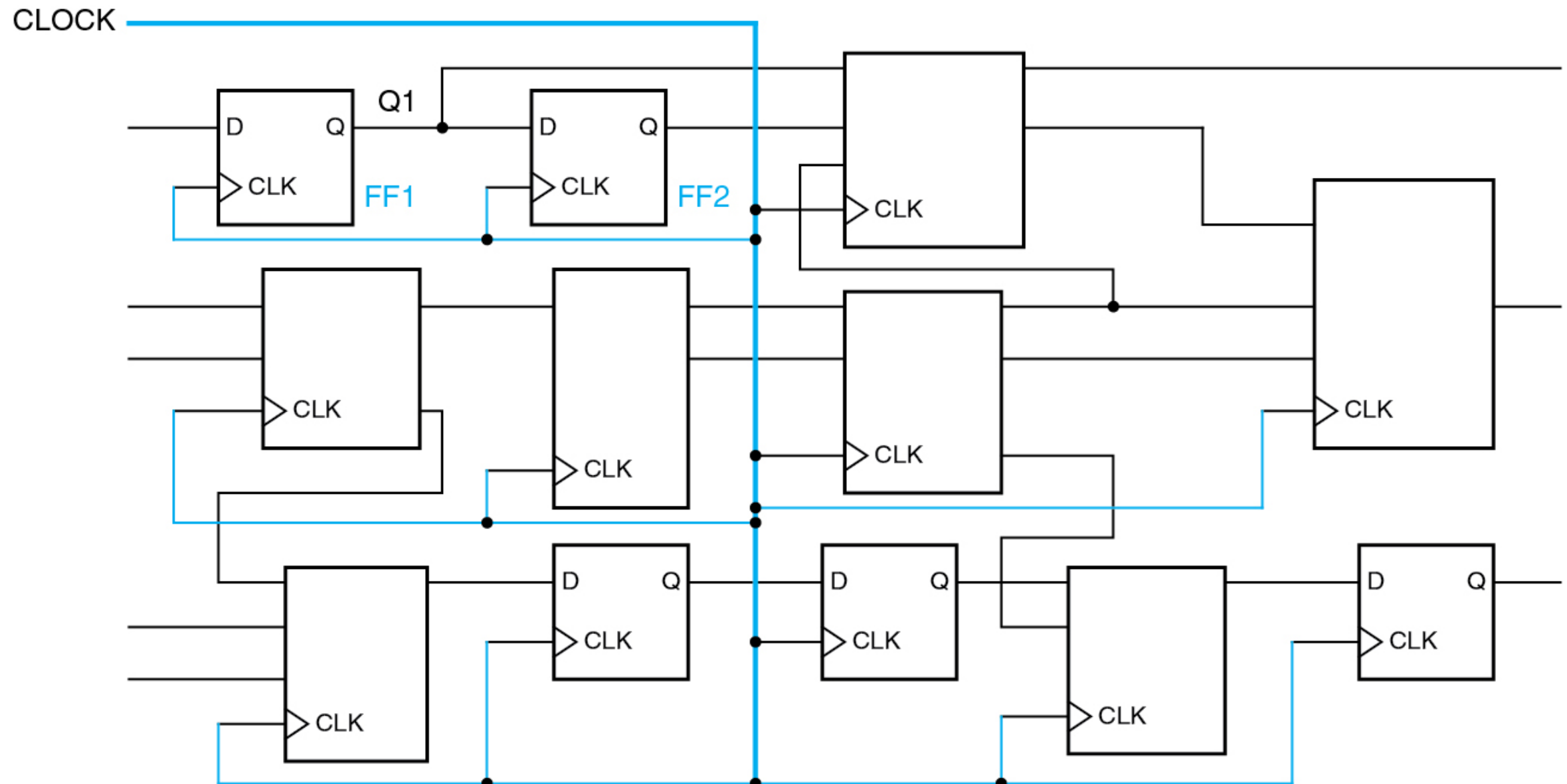
# Clock-Signal Routing to Minimize Skew

- ❖ Distributed, balanced, tree-like structure
- ❖ Fastest type of wire connection




# Clock-Signal Routing to Minimize Skew

## Clock Tree Architecture

 
### Comb

- Clock signal passed down the spine then spreads out through the branches
- Does not have equal length traces


 
### H-Tree

- All trace lengths are equal
- Minimizes clock skew





---



# Clock-Signal Routing to Minimize Skew

---

- ❖ Receivers using the same clock signal
  - ❖ Should be placed equally close, inserted in a balanced way!
- ❖ Sometimes, designer may have to route the components by hand
- ❖ Modern EDA tools —> “clock tree synthesis (CTS)” algorithm
  - ❖ Back end design, after the logic components have been placed on the chip

  
# Buffering the Clock

- ❖ (A) Excessive Clock Skew; (B) Controllable Clock Skew
- ❖ While more copies are needed?


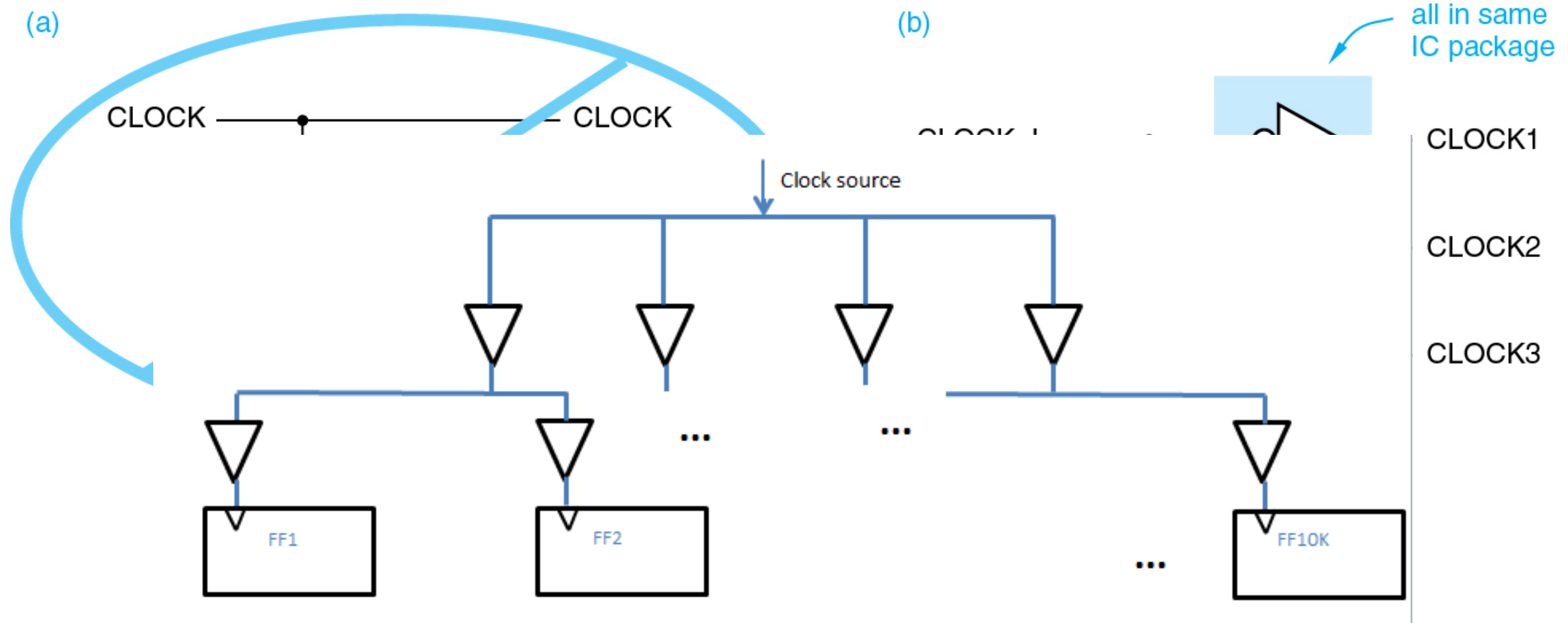
# Buffering the Clock

- ❖ (A) Excessive Clock Skew; (B) Controllable Clock Skew
- ❖ While more copies are needed?



---



# What if a Circuit DOES Violate the Timing Constraints

---

- ❖ For example, violating setup or hold time?
- ❖ Either due to circuit design
- ❖ Or
- ❖ Due to the external input!

  
# Violating the Dynamic Discipline

- Asynchronous (for example, user) inputs might violate the dynamic discipline



 
# Metastability

- **Bistable devices:** two stable states, and a metastable state between them
- **Flip-flop:** two stable states (1 and 0) and one metastable state
- If flip-flop lands in metastable state, could stay there for an undetermined amount of time



 
# Flip-Flop Internals

- Flip-flop has **feedback**: if  $Q$  is somewhere between 1 and 0, cross-coupled gates drive output to either rail (1 or 0)



- **Metastable signal**: if it hasn't resolved to 1 or 0

# Flip-Flop Internals

 

- If flip-flop input changes at random time, **probability that output  $Q$  is metastable** after waiting some time,  $t$ :

$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$

$t_{\text{res}}$  : time to resolve to 1 or 0

$T_0, \tau$  : properties of the circuit



# Metastability

$$P(t_{\text{res}} > t) = (T_0 / T_c) e^{-t/\tau}$$

$t_{\text{res}}$  : time to resolve to 1 or 0

$T_0, \tau$  : properties of the circuit

- **Intuitively:**

- $T_0/T_c$ : probability input changes at a bad time (during aperture)

$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$



- $\tau$ : time constant for how fast flip-flop moves away from metastability

$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$

- In short, if flip-flop samples metastable input, if you wait long enough ( $t$ ), the output will have resolved to 1 or 0 with high probability.
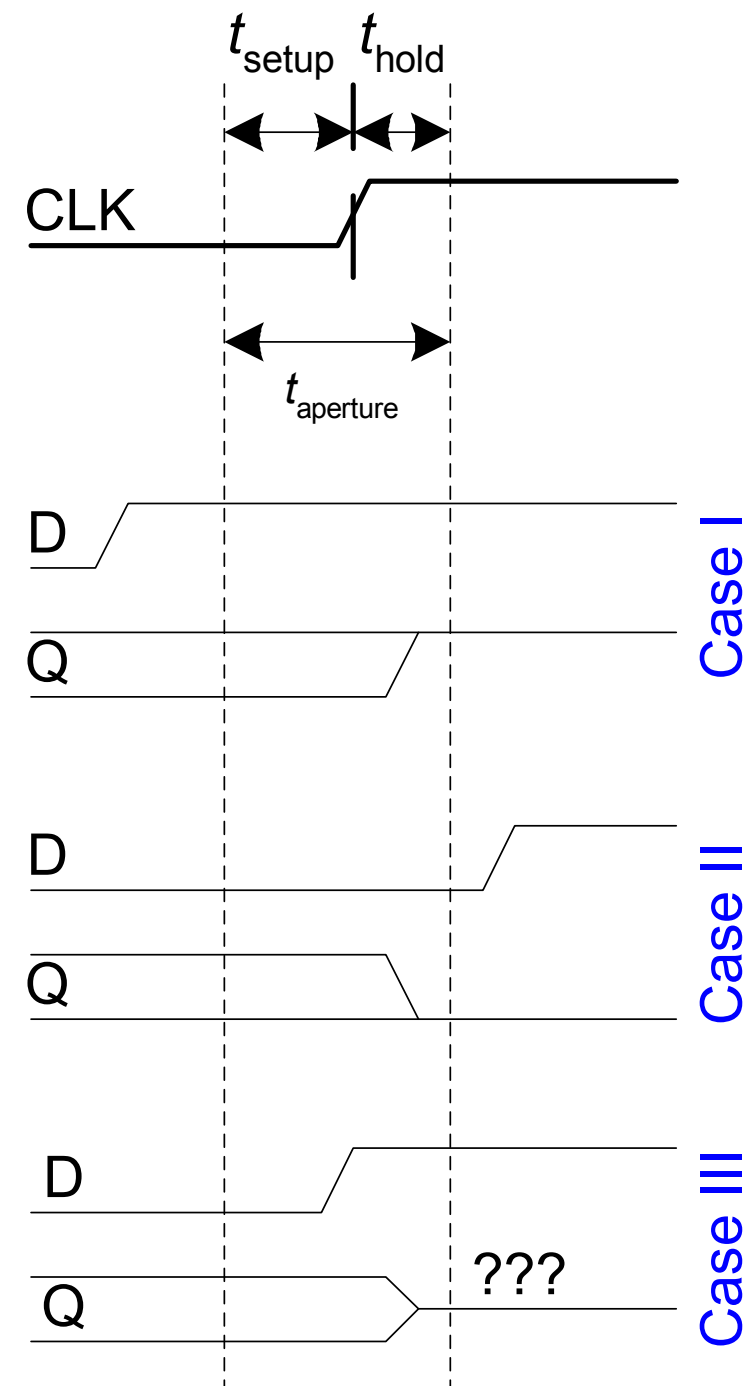 
# Violating the Dynamic Discipline

- Asynchronous (for example, user) inputs might violate the dynamic discipline



# Synchronizers

- **Asynchronous inputs are inevitable** (user interfaces, systems with different clocks interacting, etc.)
- **Synchronizer goal:** make the probability of failure (the output  $Q$  still being metastable) low
- Synchronizer cannot make the probability of failure 0

