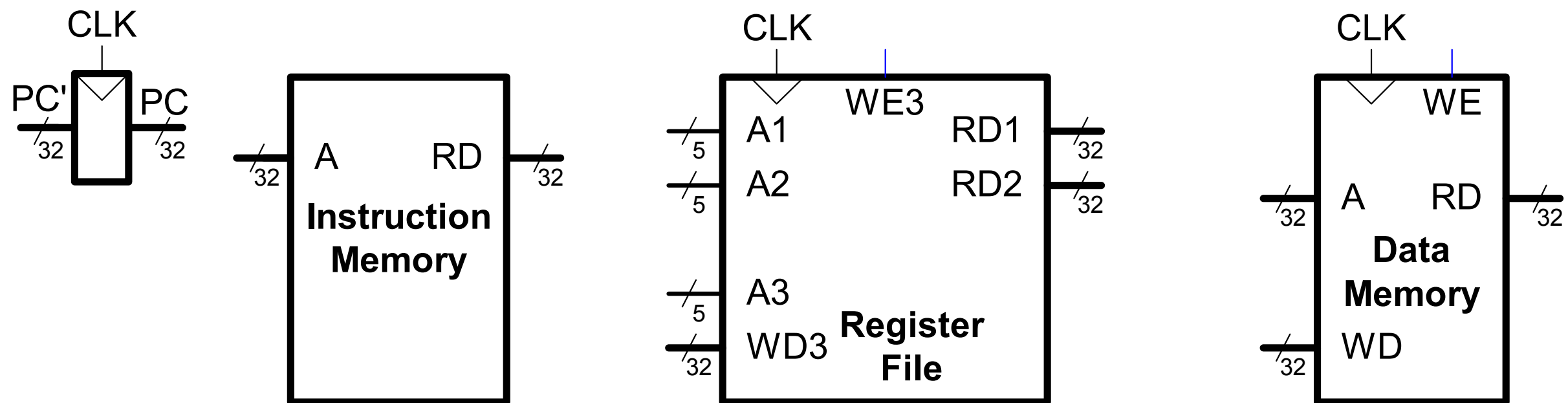


EECE 2322: Fundamentals of Digital Design and Computer Organization

Lecture 13_1: Microarchitecture

Xiaolin Xu
Department of ECE
Northeastern University

MIPS State Elements



- ❖ Instruction memory, register file, and data memory, are being **read** as combinational circuit, i.e., data change follows address change, while the writing follows clock-edge
- ❖ **Benefits:** all elements are synchronized, while MIPS processor is a FSM!

Single-Cycle MIPS Processor

- ❖ Datapath
- ❖ Control

Overview: Single-Cycle Control

R-Type


op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

J-Type

op	addr
6 bits	26 bits

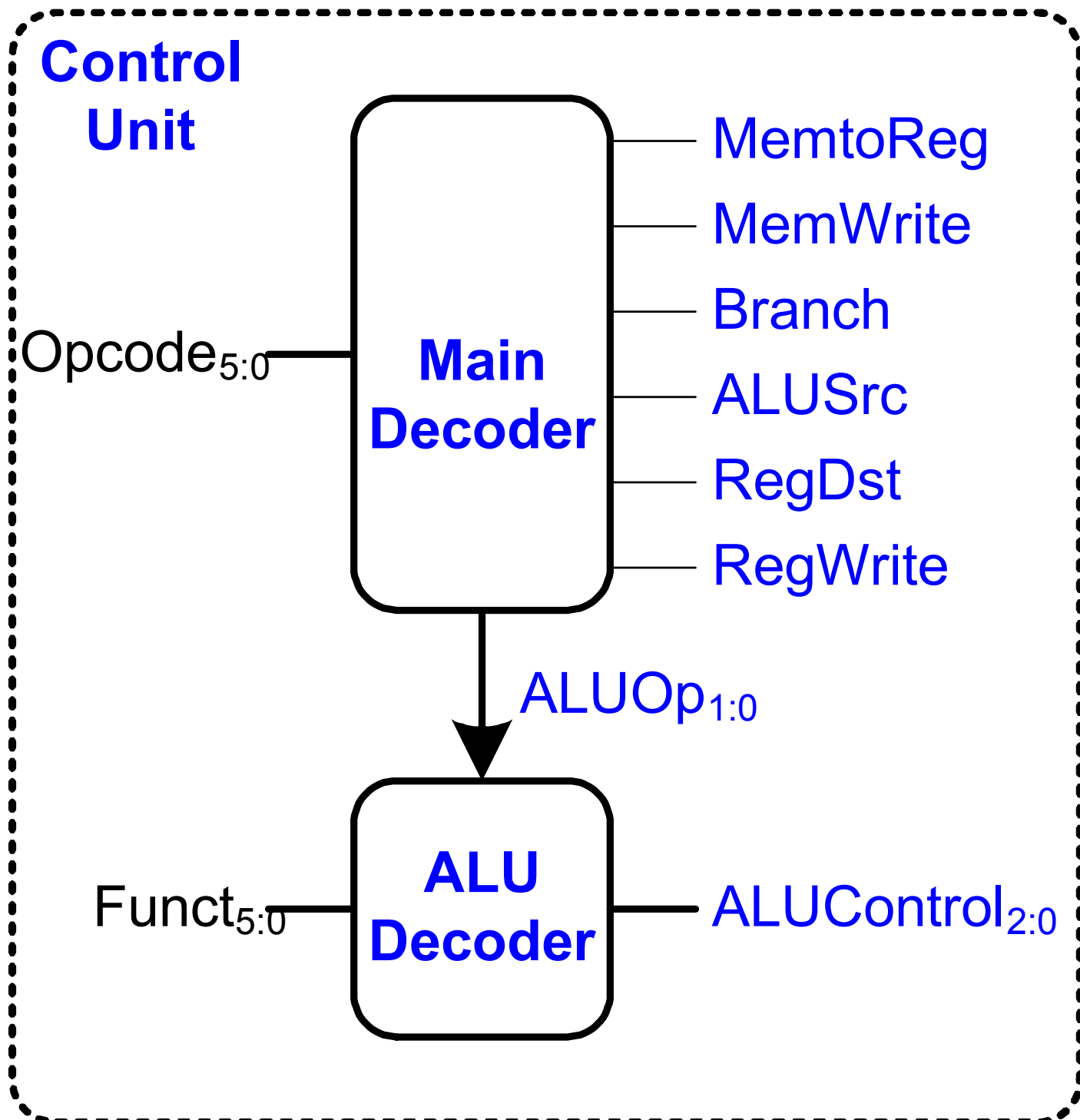

Single-Cycle Datapath Example: lw fetch


Revisit: Practice of I-type

`lw $s3, -24($s4)`


`lw` has opcode of 35

Name	Number
\$0	0
\$at	1
\$v0-\$v1	2-3
\$a0-\$a3	4-7
\$t0-\$t7	8-15
\$s0-\$s7	16-23
\$t8-\$t9	24-25
\$k0-\$k1	26-27
\$gp	28
\$sp	29
\$fp	30
\$ra	31

Field Values

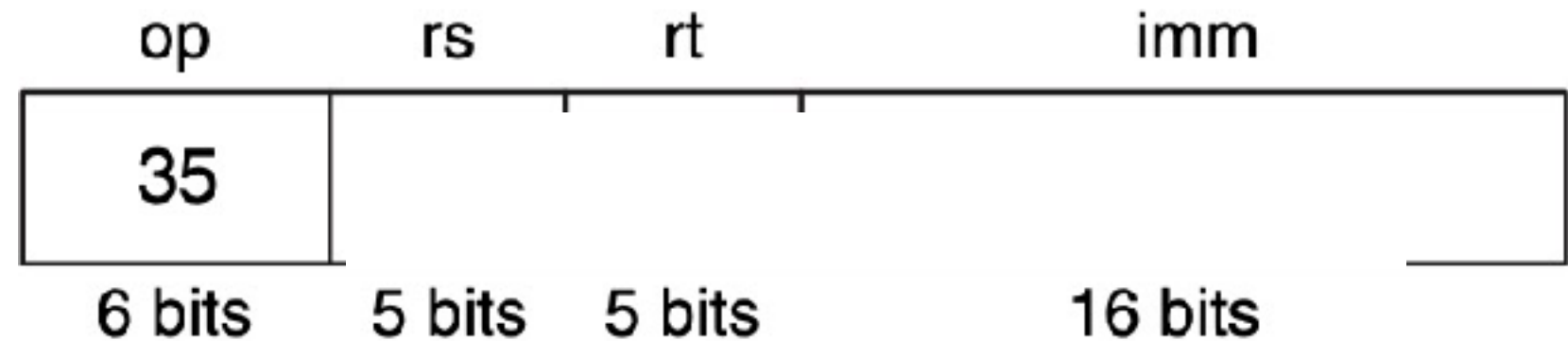

Machine Code

 

Revisit: Practice of I-type

`lw $s3, -24($s4)`


`lw` has opcode of 35

Name	Number
\$0	0
\$at	1
\$v0-\$v1	2-3
\$a0-\$a3	4-7
\$t0-\$t7	8-15
\$s0-\$s7	16-23
\$t8-\$t9	24-25
\$k0-\$k1	26-27
\$gp	28
\$sp	29
\$fp	30
\$ra	31

Field Values

op	rs	rt	imm
35	20	19	-24
6 bits	5 bits	5 bits	16 bits

Machine Code

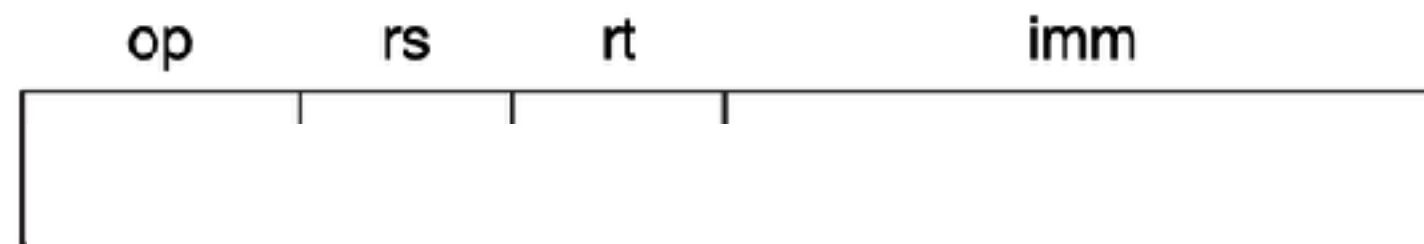

Revisit: Practice of I-type

lw \$s3, -24(\$s4)

lw has opcode of 35

Name	Number
\$0	0
\$at	1
\$v0-\$v1	2-3
\$a0-\$a3	4-7
\$t0-\$t7	8-15
\$s0-\$s7	16-23
\$t8-\$t9	24-25
\$k0-\$k1	26-27
\$gp	28
\$sp	29
\$fp	30
\$ra	31

Field Values

op	rs	rt	imm
35	20	19	-24
6 bits	5 bits	5 bits	16 bits

Machine Code


op	rs	rt	imm	
100011	10100	10011	1111 1111 1110 1000	(0x8E93FFE8)
8	E	9	3	F F E 8

Single-Cycle Datapath Example: lw fetch


STEP 1: Fetch instruction

lw \$s3, -24(\$s4)

lw has opcode of 35

 

Field Values

 


Single-Cycle Datapath Example: lw fetch

STEP 1: Fetch instruction

lw \$s3, -24(\$s4)

lw has opcode of 35

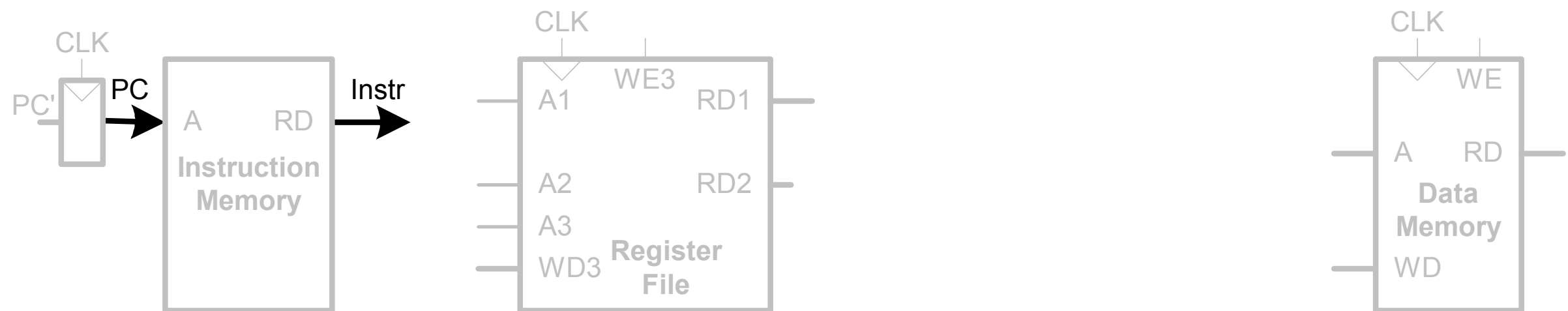

Field Values


op	rs	rt	imm
35	20	19	-24
6 bits	5 bits	5 bits	16 bits

Single-Cycle Datapath Example: lw fetch

STEP 1: Fetch instruction

lw \$s3, -24(\$s4)

lw has opcode of 35

 

The offset is stored in the immediate field of the instruction, Instr_{15:0}


Field Values

op	rs	rt	imm
35	20	19	-24
6 bits	5 bits	5 bits	16 bits


Single-Cycle Datapath: lw Register Read

STEP 2: Read source operands from RF

`lw $s3, -24($s4)`

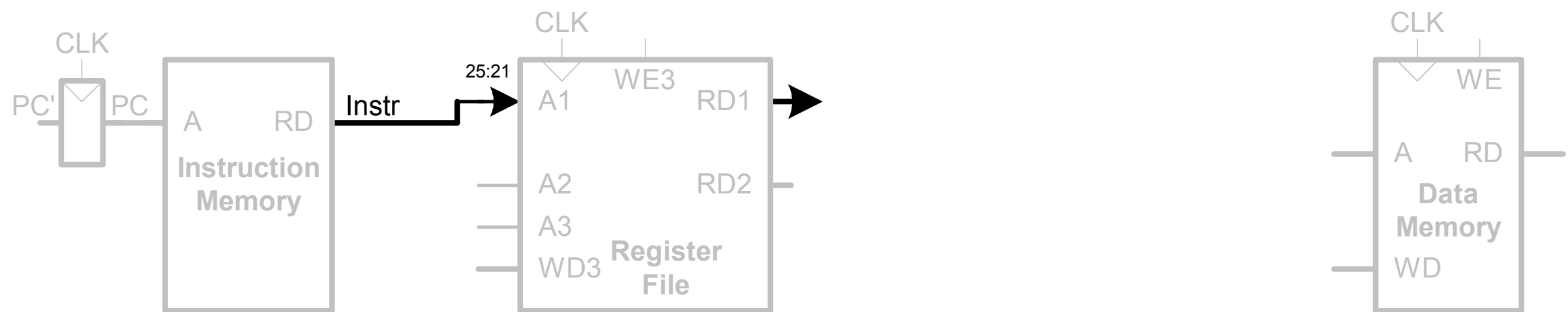


Field Values

 

Single-Cycle Datapath: lw Register Read

STEP 2: Read source operands from RF

`lw $s3, -24($s4)`

 


Field Values

op	rs	rt	imm
35	20	19	-24
6 bits	5 bits	5 bits	16 bits

Single-Cycle Datapath: lw Immediate

STEP 3: Sign-extend the immediate


`lw $s3, -24($s4)`

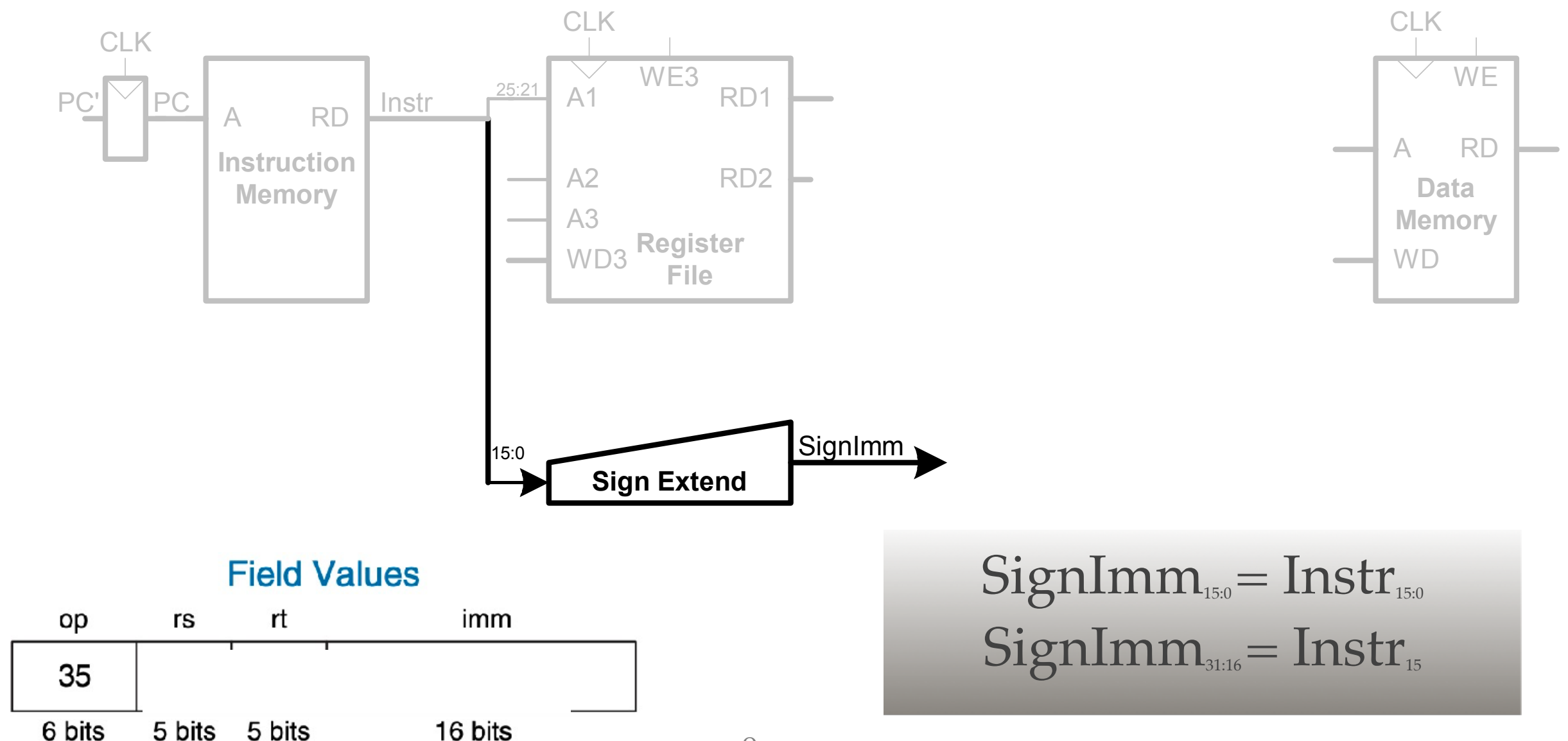

Single-Cycle Datapath: lw address

STEP 4: Compute the memory address

lw \$s3, -24(\$s4)

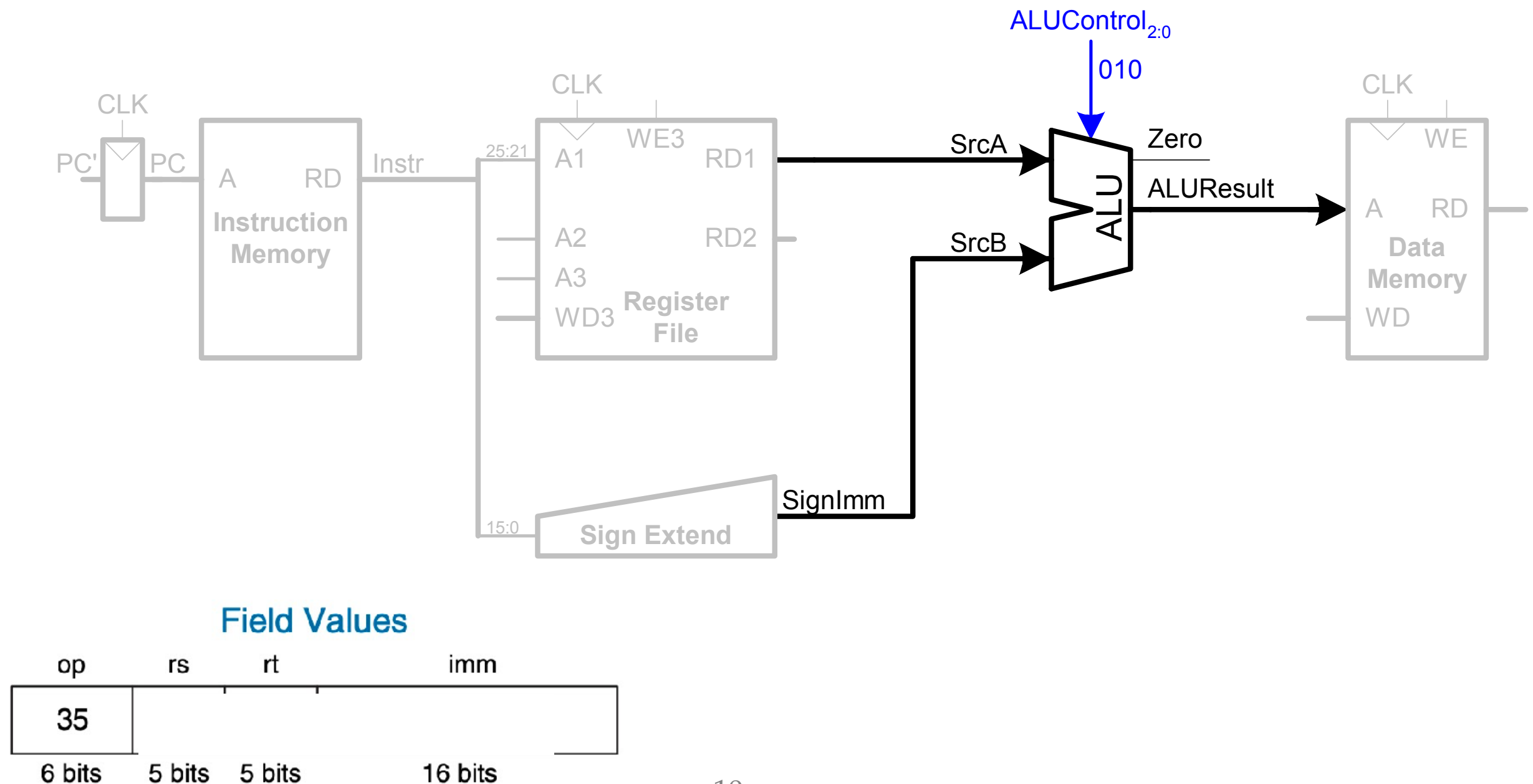


Single-Cycle Datapath: lw address

STEP 4: Compute the memory address

lw \$s3, -24(\$s4)

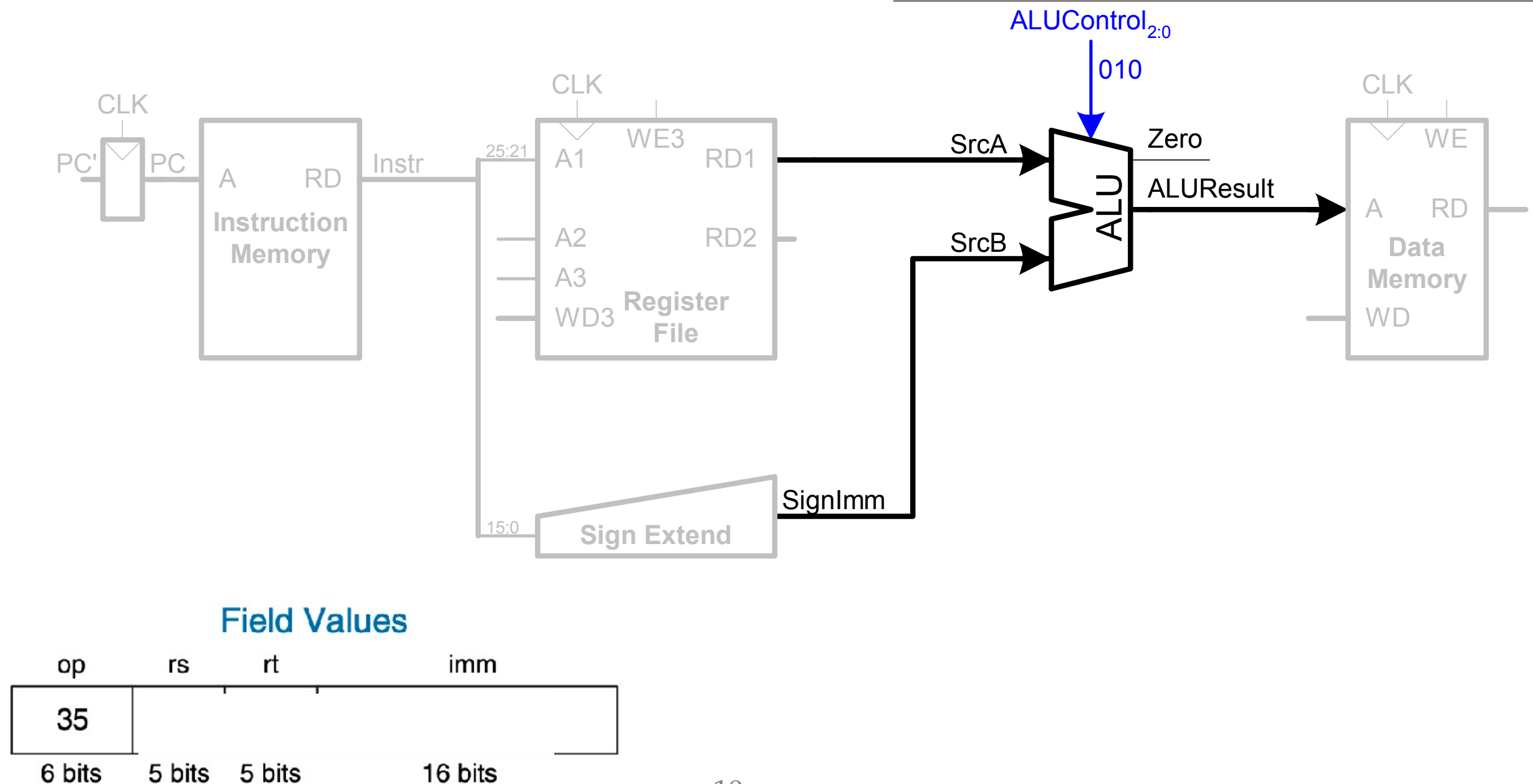add the base address to the offset to find the address to read from memory




Single-Cycle Datapath: lw address

STEP 4: Compute the memory address


lw \$s3, -24(\$s4)

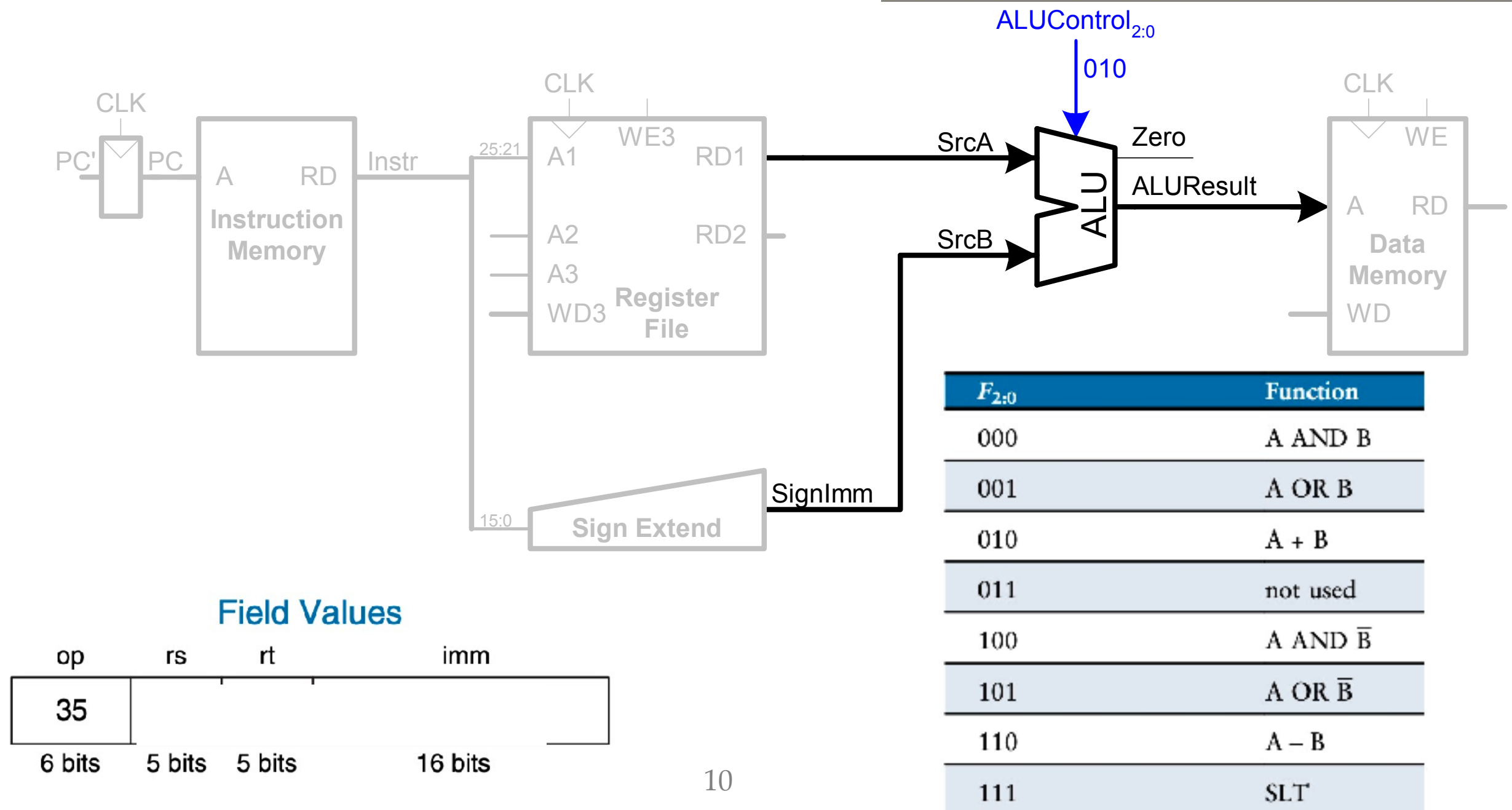add the base address to the offset to find the address to read from memory




Single-Cycle Datapath: lw Memory Read

 - ❖ **STEP 5:** Read data from memory and write it back to register file




Single-Cycle Datapath: lw Memory Read

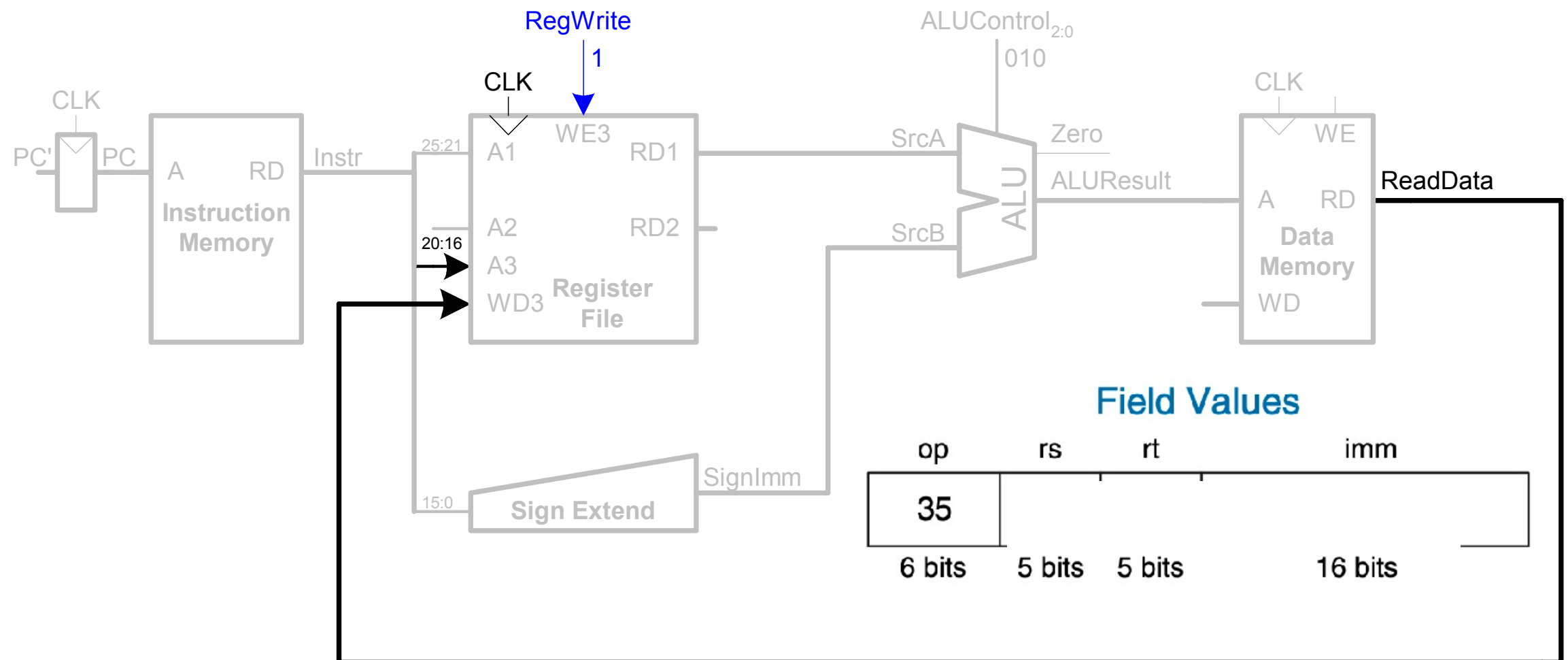- ❖ **STEP 5:** Read data from memory and write it back to register file



Single-Cycle Datapath: lw Memory Read

 
- ❖ **STEP 5:** Read data from memory and write it back to register file



The data is read from the data memory onto the `ReadData` bus, then written back to the destination register in the register file at the end of the cycle

Single-Cycle Datapath: lw PC Increment

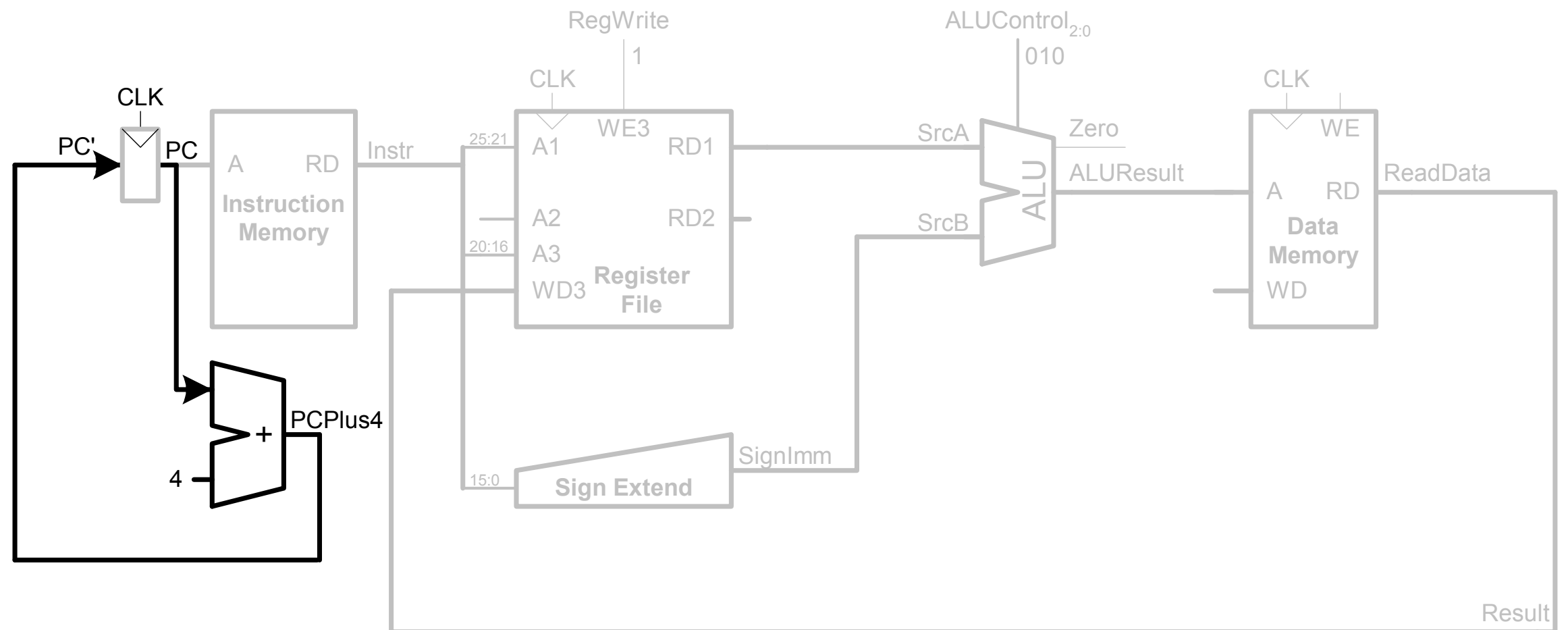STEP 6: Determine address of next instruction



Use another adder to increment the PC by 4
The new address is written into the program counter on the next rising edge of the clock. This completes the datapath for the `lw` instruction

Single-Cycle Datapath: sw

Single-Cycle Datapath: sw

Like the `lw` instruction, the `sw` instruction reads a base address from port 1 of the register file and sign-extends an immediate.

Single-Cycle Datapath: sw

Like the lw instruction, the sw instruction reads a base address from port 1 of the register file and sign-extends an immediate.

ALU adds the base address to the immediate to find the memory address

Name	Number
\$0	0
\$at	1
\$v0-\$v1	2-3
\$a0-\$a3	4-7
\$t0-\$t7	8-15
\$s0-\$s7	16-23
\$t8-\$t9	24-25
\$k0-\$k1	26-27
\$gp	28
\$sp	29
\$fp	30
\$ra	31

I-Type Examples

Assembly Code

Field Values

	op	rs	rt	imm
sw	43	9	17	4
	6 bits	5 bits	5 bits	16 bits

sw \$s1, 4(\$t1)


Machine Code

sw rt, imm(rs)

101011	01001	10001	0000 0000 0000 0100	(0xAD310004)
6 bits	5 bits	5 bits	16 bits	

Single-Cycle Datapath: sw

Write data in `rt` to memory

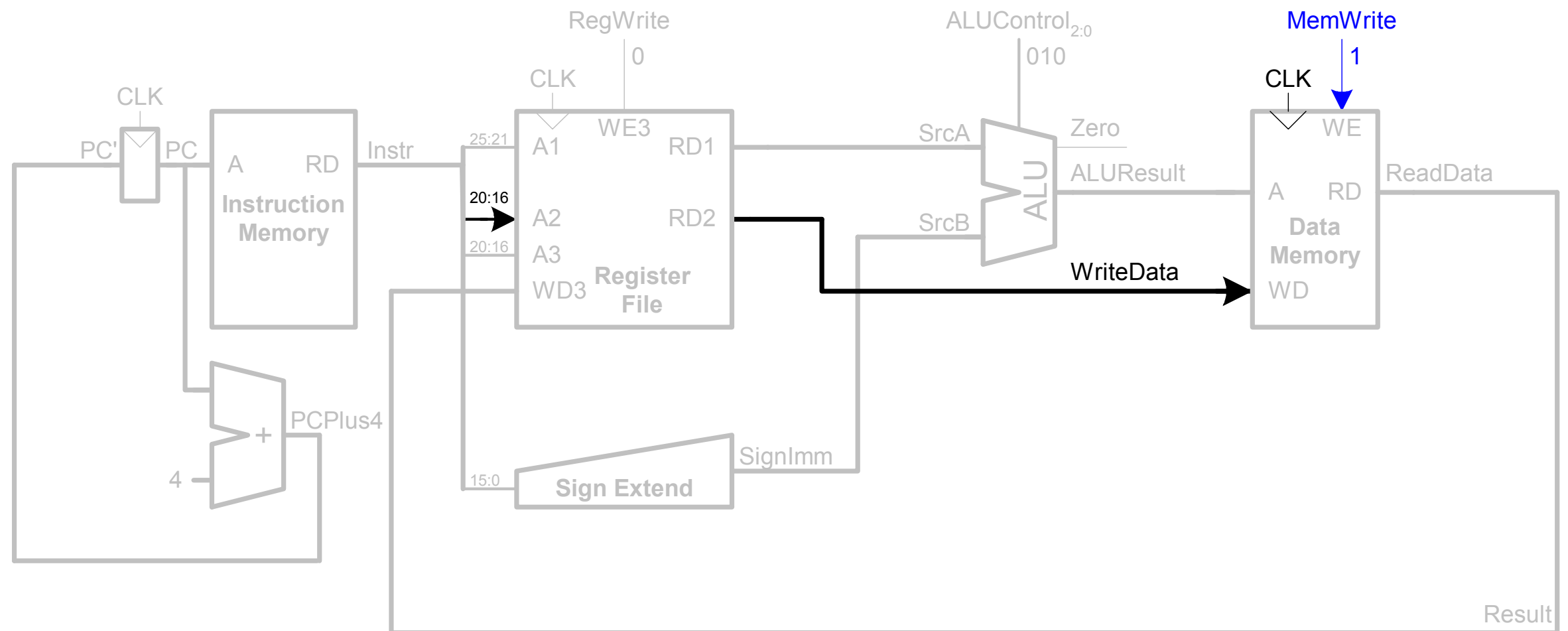

Single-Cycle Datapath: R-Type

- ❖ Read from `rs` and `rt`

R-Type

- *Register-type*
- 3 register operands:
 - rs, rt: source registers
 - rd: destination register
- Other fields:
 - op: the *operation code* or *opcode* (0 for R-type instructions)
 - funct: the *function*
 - with opcode, tells computer what operation to perform
 - shamt: the *shift amount* for shift instructions, otherwise it's 0

R-Type



Single-Cycle Datapath: R-Type

- ❖ Write *ALUResult* to register file
- ❖ Write to `rd` (instead of `rt`)


Practice of R-type

add \$t4, \$s4, \$s5


add has op code of 0 and
funct code of 32

Name	Number
\$0	0
\$at	1
\$v0-\$v1	2-3
\$a0-\$a3	4-7
\$t0-\$t7	8-15
\$s0-\$s7	16-23
\$t8-\$t9	24-25
\$k0-\$k1	26-27
\$gp	28
\$sp	29
\$fp	30
\$ra	31

Field Values

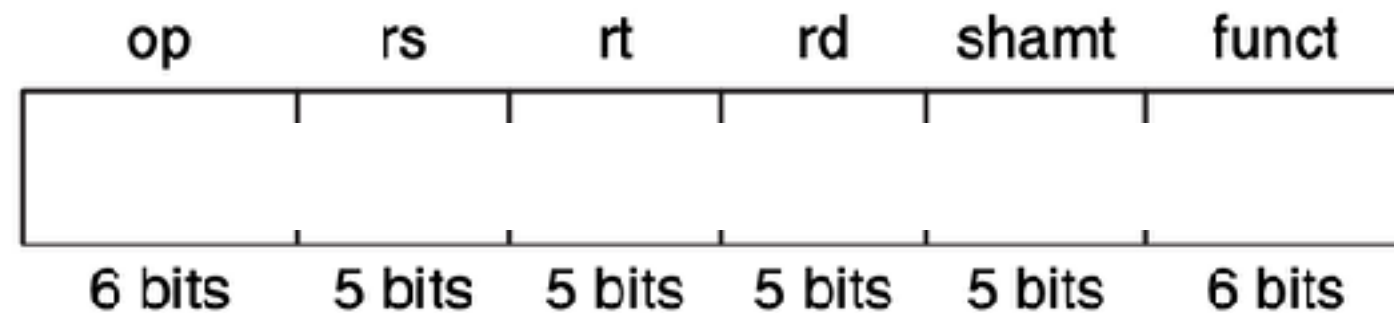

Machine Code

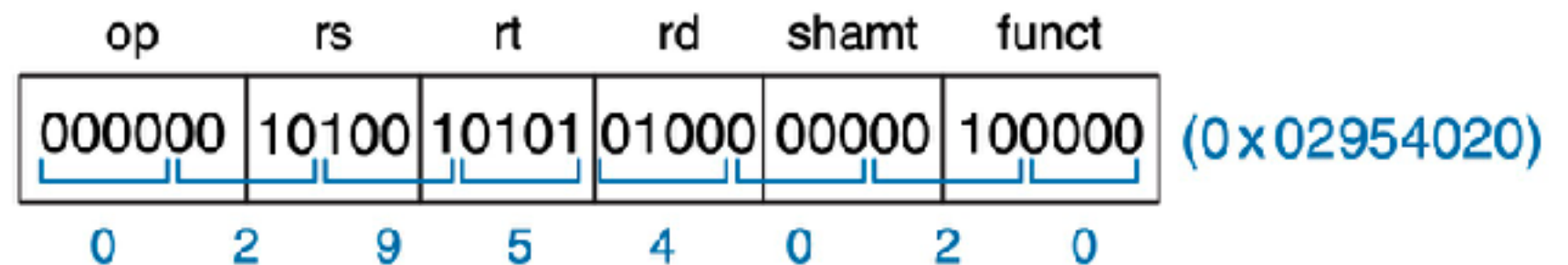

Practice of R-type

add \$t4, \$s4, \$s5

add has op code of 0 and
funct code of 32

Name	Number
\$0	0
\$at	1
\$v0-\$v1	2-3
\$a0-\$a3	4-7
\$t0-\$t7	8-15
\$s0-\$s7	16-23
\$t8-\$t9	24-25
\$k0-\$k1	26-27
\$gp	28
\$sp	29
\$fp	30
\$ra	31

Field Values


op	rs	rt	rd	shamt	funct
0	20	21	8	0	32
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Machine Code

op	rs	rt	rd	shamt	funct		
000000	10100	10101	01000	00000	100000	(0x02954020)	
0	2	9	5	4	0	2	0

Single-Cycle Datapath: R-Type


 
- ❖ Read from `rs` and `rt`
- ❖ Write *ALUResult* to register file
- ❖ Write to `rd` (instead of `rt`)



Single-Cycle Datapath: R-Type

- ❖ Read from `rs` and `rt`
- ❖ Write *ALUResult* to register file
- ❖ Write to `rd` (instead of `rt`)



Field Values

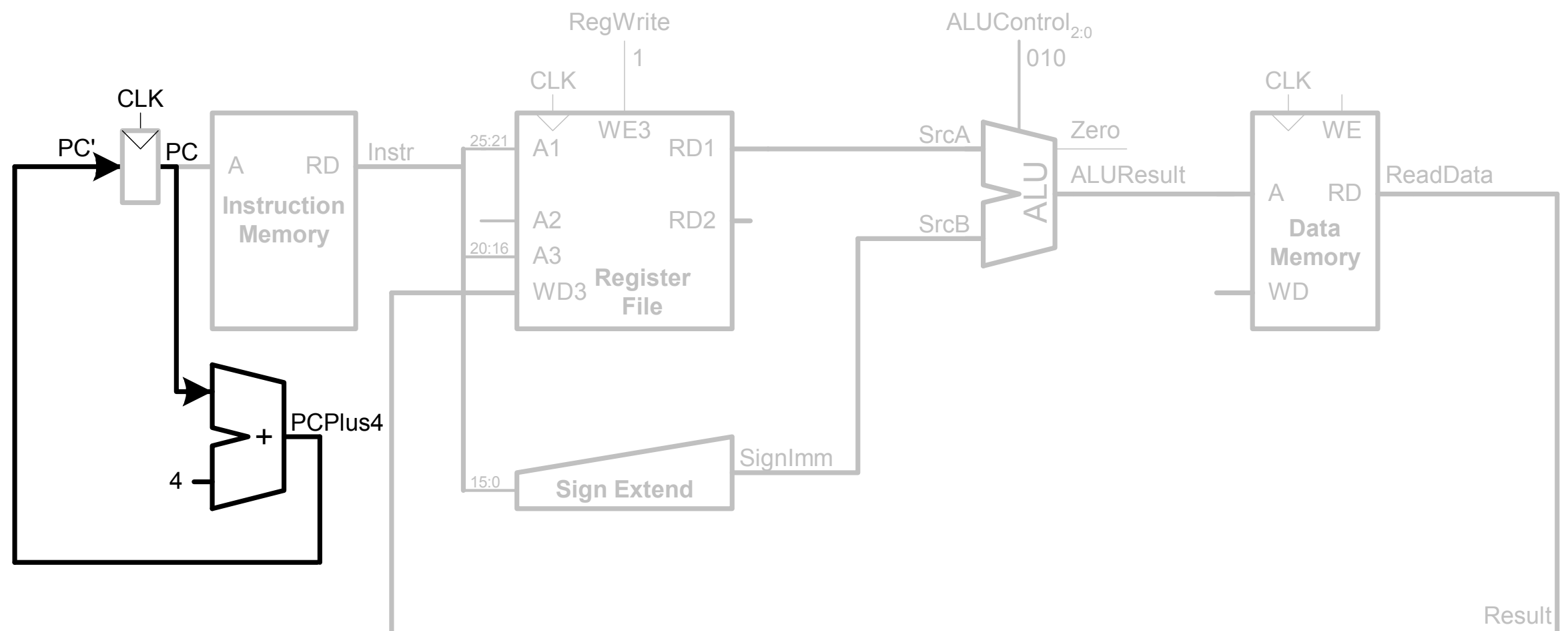 

Single-Cycle Datapath: R-Type

- ❖ Read from `rs` and `rt`
- ❖ Write *ALUResult* to register file
- ❖ Write to `rd` (instead of `rt`)



Field Values

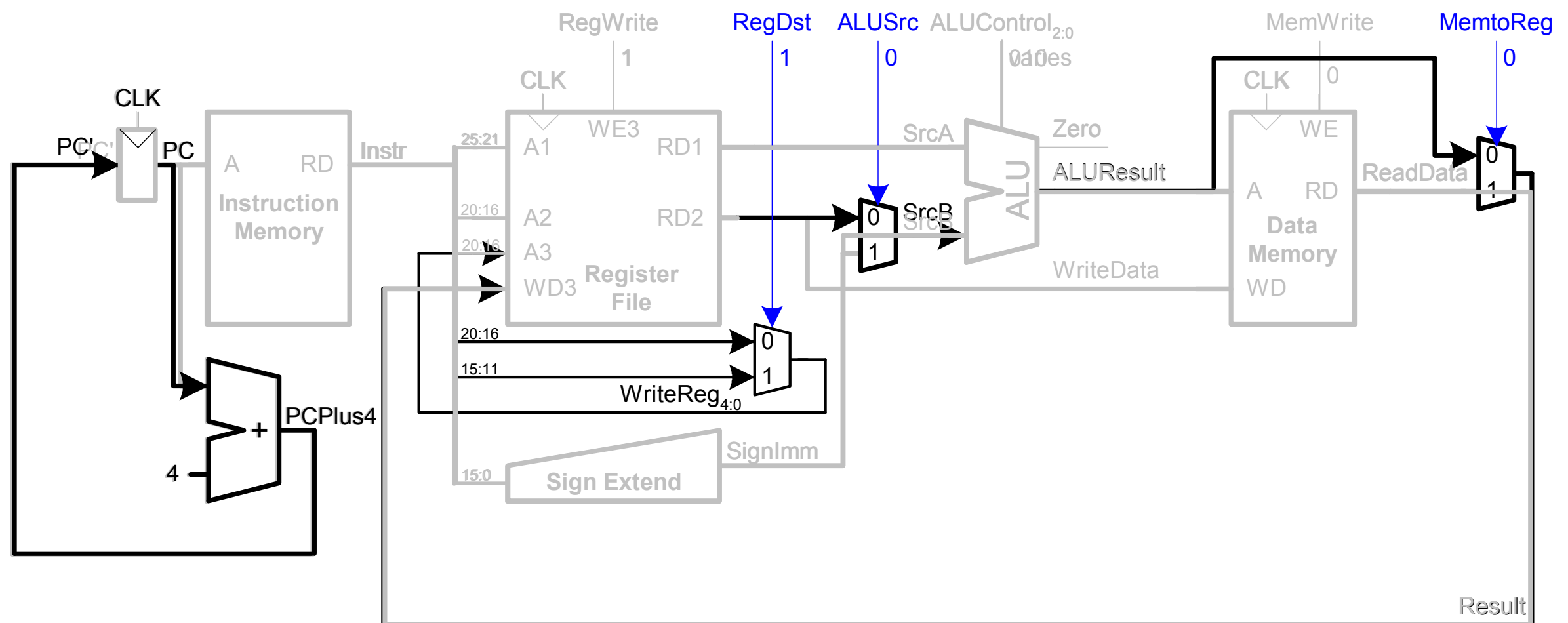 

Single-Cycle Datapath: R-Type

- ❖ Read from `rs` and `rt`
- ❖ Write *ALUResult* to register file
- ❖ Write to `rd` (instead of `rt`)

Field Values

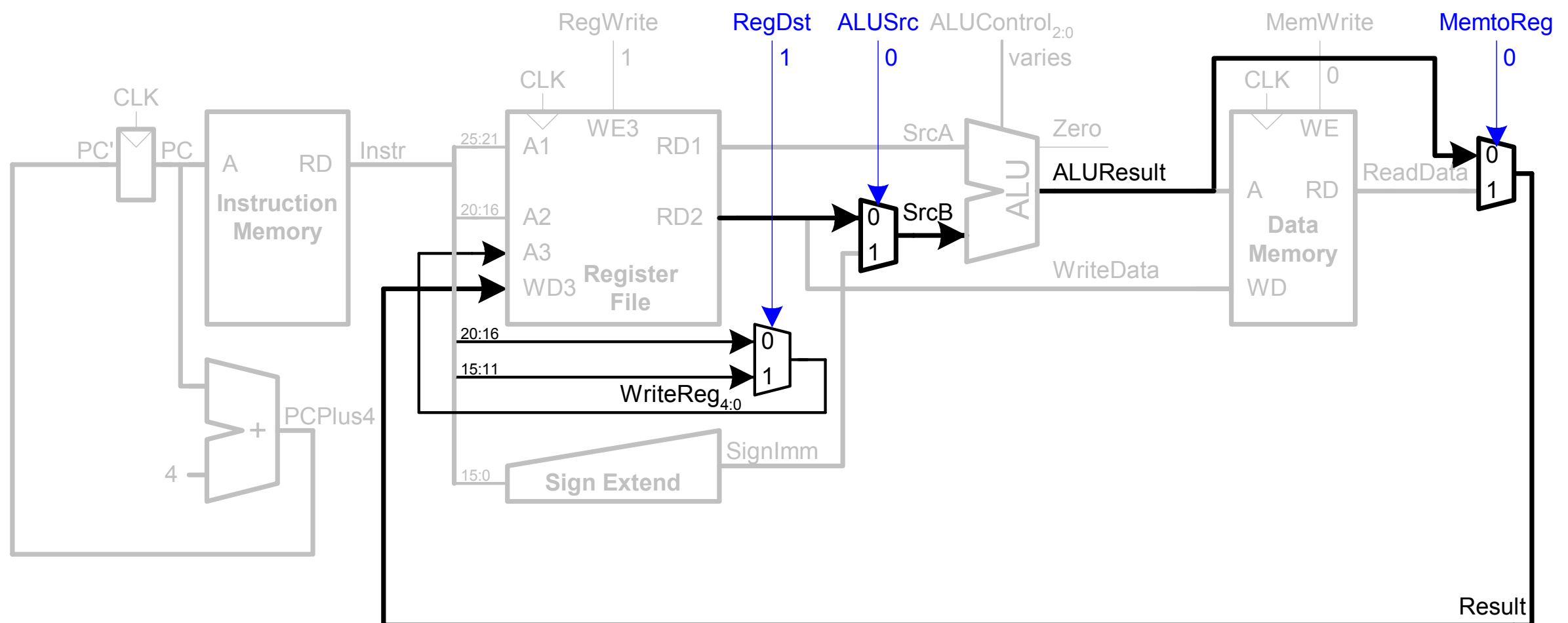 

Single-Cycle Datapath: beq

- ❖ Determine whether values in r_s and r_t are equal

Instruction	Example	Meaning	Comments
branch on equal	beq \$1, \$2, 100	if(\$1==\$2) go to PC+4+100	Test if registers are equal
branch on not equal	bne \$1, \$2, 100	if(\$1!=\$2) go to PC+4+100	Test if registers are not equal

Conditional Branching (beq)

MIPS assembly

Results per line?

```
addi $s0, $0, 4
addi $s1, $0, 1
sll  $s1, $s1, 2
beq  $s0, $s1, target
addi $s1, $s1, 1
sub  $s1, $s1, $s0
```

Is this “targeted” instruction executed or not? and its results?

```
target:      # label
    add  $s1, $s1, $s0
```

Labels indicate instruction location. They can't be reserved words and must be followed by colon (:)

Conditional Branching (beq)

MIPS assembly

Results per line?

<code>addi \$s0, \$0, 4</code>	<code># \$s0 = 0 + 4 = 4</code>
<code>addi \$s1, \$0, 1</code>	<code># \$s1 = 0 + 1 = 1</code>
<code>sll \$s1, \$s1, 2</code>	<code># \$s1 = 1 << 2 = 4</code>
<code>beq \$s0, \$s1, target</code>	<code># branch is taken</code>
<code>addi \$s1, \$s1, 1</code>	<code># not executed</code>
<code>sub \$s1, \$s1, \$s0</code>	<code># not executed</code>

Is this “targeted” instruction executed or not? and its results?

```
target:      # label
    add $s1, $s1, $s0
```

Labels indicate instruction location. They can't be reserved words and must be followed by colon (:)

Conditional Branching (beq)

MIPS assembly

Results per line?

addi \$s0, \$0, 4	# $\$s0 = 0 + 4 = 4$
addi \$s1, \$0, 1	# $\$s1 = 0 + 1 = 1$
sll \$s1, \$s1, 2	# $\$s1 = 1 \ll 2 = 4$
beq \$s0, \$s1, target	# branch is taken
addi \$s1, \$s1, 1	# not executed
sub \$s1, \$s1, \$s0	# not executed

Is this “targeted” instruction executed or not? and its results?

target:	# label
add \$s1, \$s1, \$s0	# $\$s1 = 4 + 4 = 8$

Labels indicate instruction location. They can't be reserved words and must be followed by colon (:)


Single-Cycle Datapath: beq

- ❖ Determine whether values in rs and rt are equal
- ❖ Calculate branch target address:
$$BTA = (\text{sign-extended immediate} \ll 2) + (PC+4)$$

Single-Cycle Datapath: beq

- ❖ Determine whether values in rs and rt are equal
- ❖ Calculate branch target address:

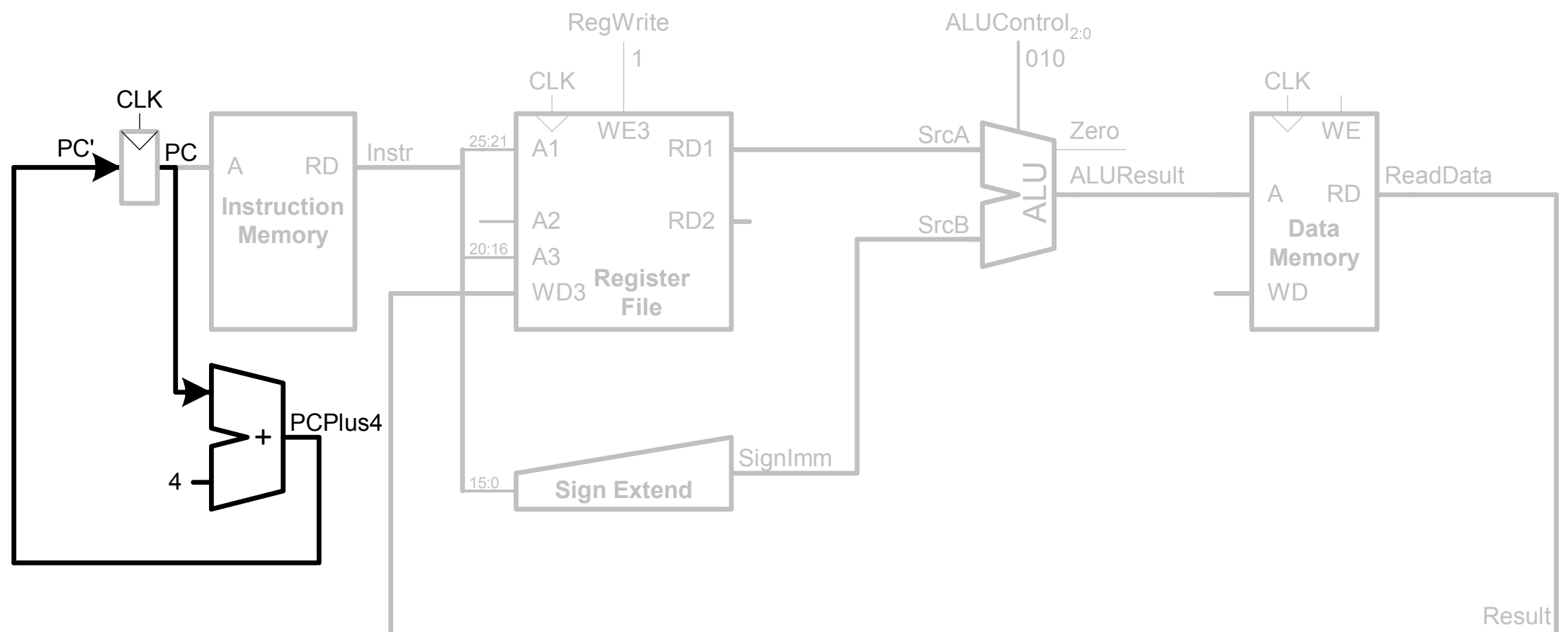
$$BTA = (\text{sign-extended immediate} \ll 2) + (PC+4)$$



Single-Cycle Datapath: beq

- ❖ Determine whether values in `rs` and `rt` are equal
- ❖ Calculate branch target address:

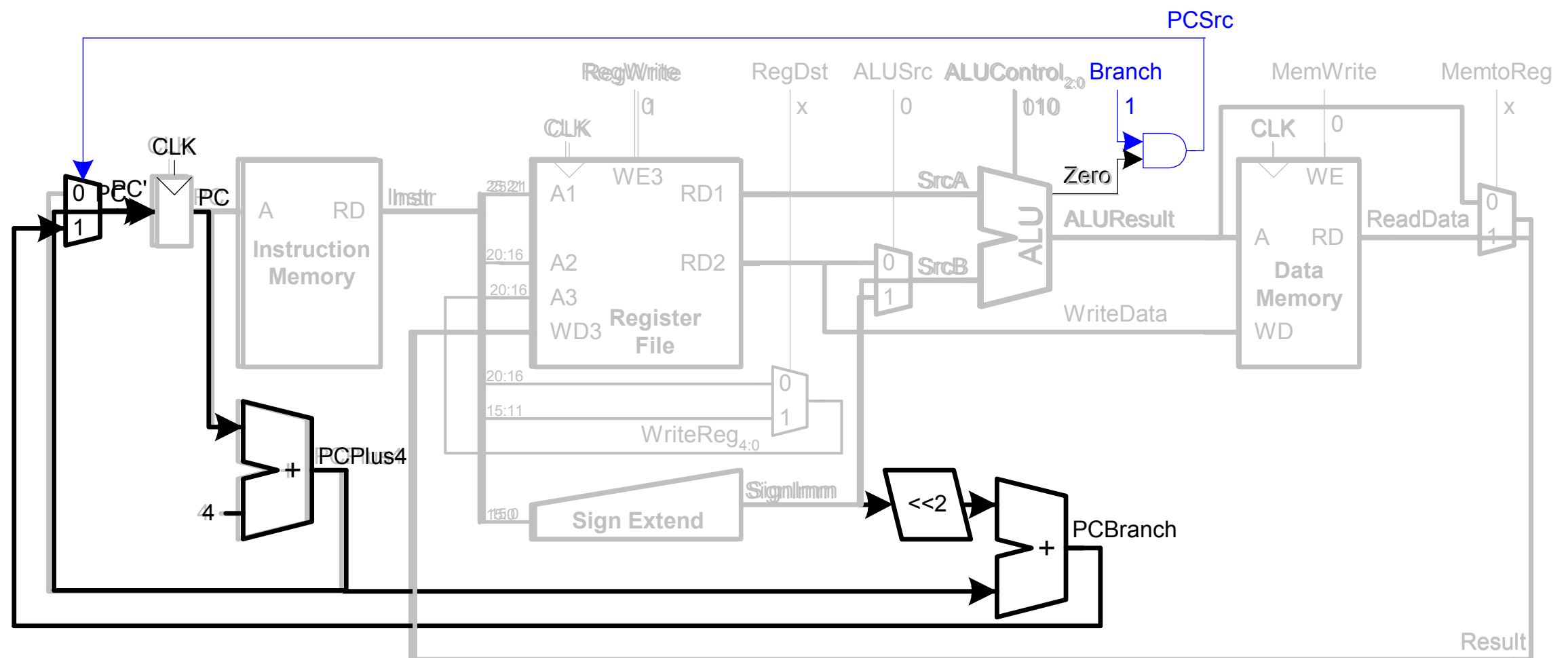
$$\text{BTA} = (\text{sign-extended immediate} \ll 2) + (\text{PC} + 4)$$




Single-Cycle Datapath: beq

- ❖ Determine whether values in `rs` and `rt` are equal
- ❖ Calculate branch target address:
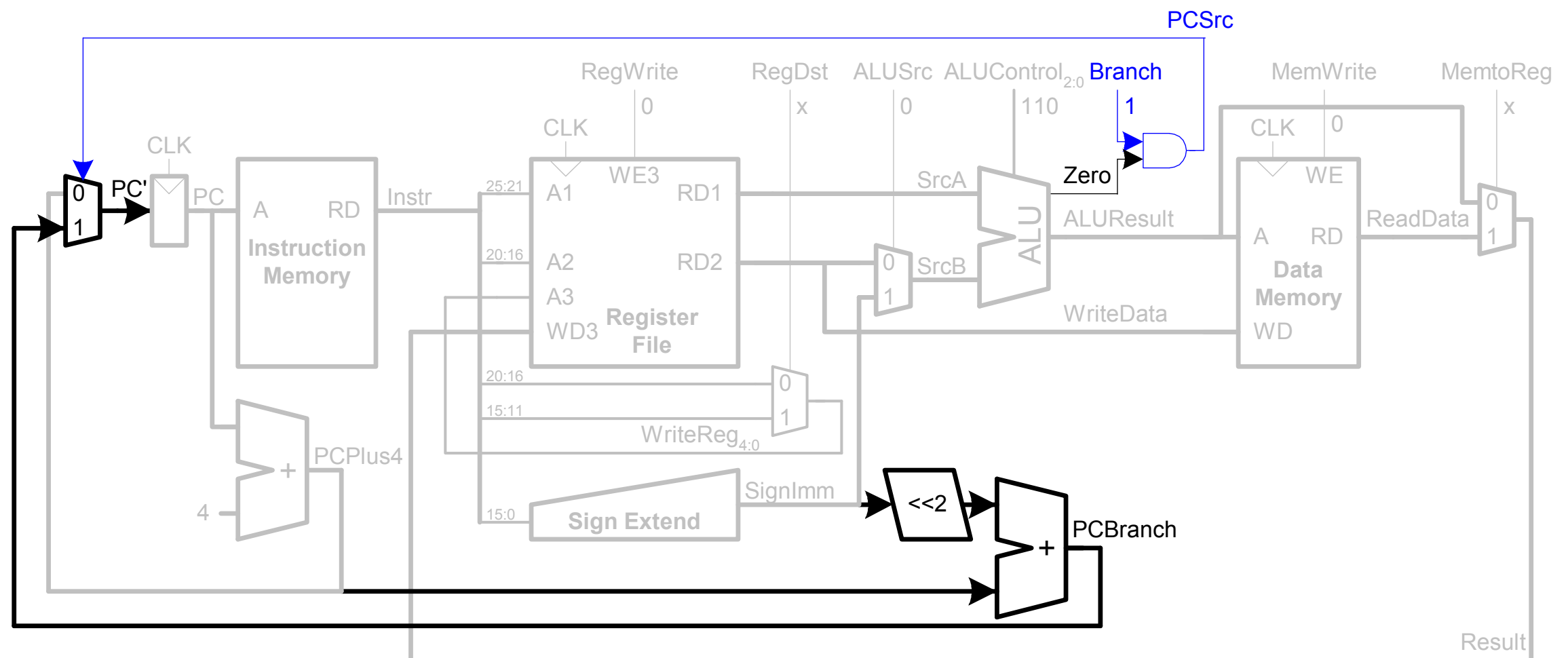
$$\text{BTA} = (\text{sign-extended immediate} \ll 2) + (\text{PC} + 4)$$




Design of the Single-Cycle Control

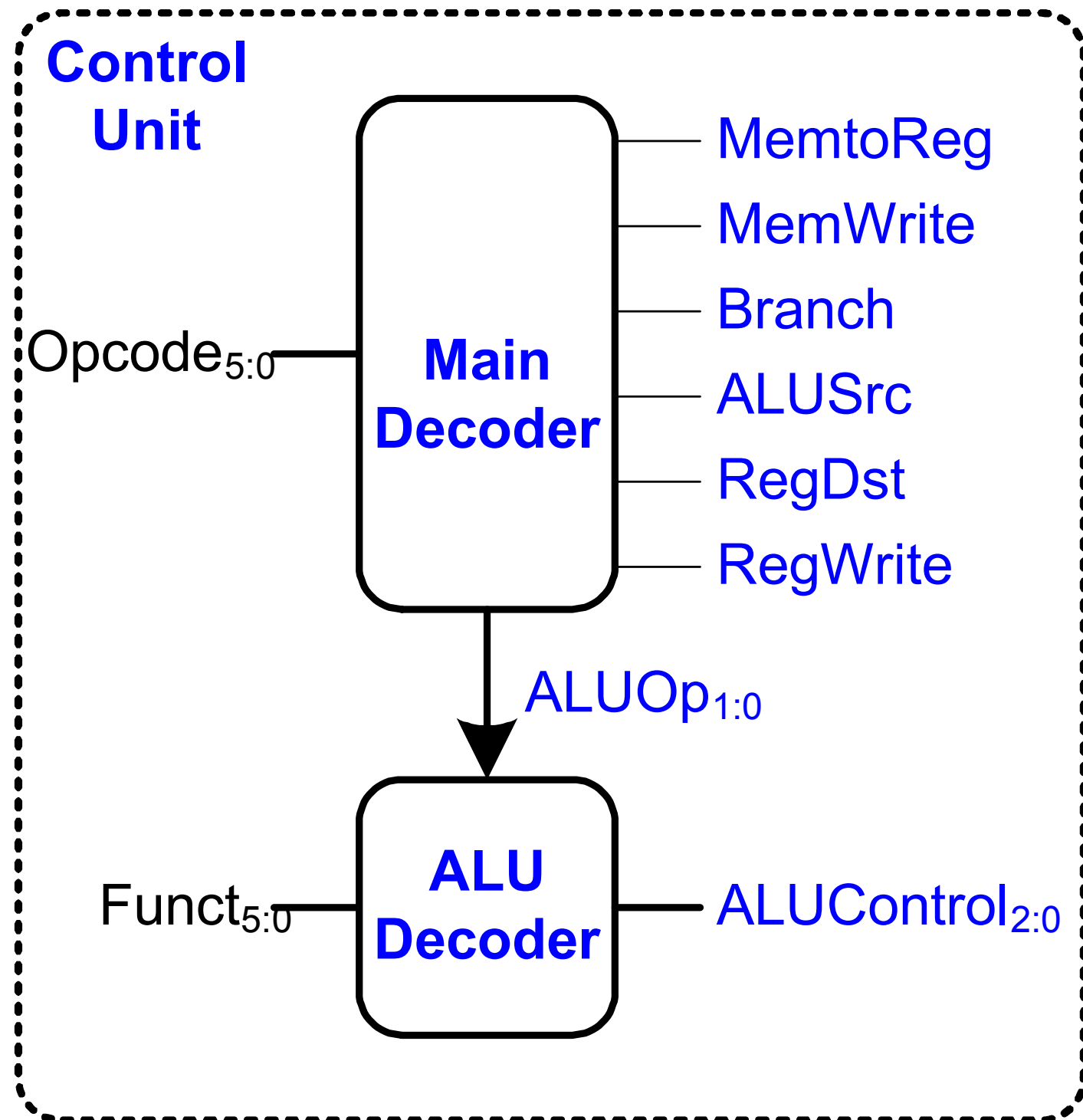


ALU: Arithmetic Logic Unit

 - ❖ Digital circuit that performs arithmetic and bitwise operations



ALU: Arithmetic Logic Unit

 - ❖ Digital circuit that performs arithmetic and bitwise operations
 - ❖ Data, Opcode, Status
- ❖ Arithmetic
 - ❖ Add, Add with carry, Subtract, Subtract with borrow ...
- ❖ Bite-wise logic
 - ❖ AND, OR, XOR ...




ALU Schematic

- ❖ Abstraction of ALU, three components

- ❖ Two inputs (A, B)
- ❖ One output (Y)
- ❖ Control signal F (3-bit)


$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND \bar{B}
101	A OR \bar{B}
110	A - B
111	SLT

 

SLT: Set less than (later)



ALU Operations: Addition

 - ❖ Adder, already introduced
- ❖ Replace the ALU with +



$$S = A \oplus B$$

$$C_{out} = AB$$

  


C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$


$$C_{out} = AB + AC_{in} + BC_{in}$$

Review: ALU

 

$F_{2:0}$	Function
000	$A \& B$
001	$A B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A \sim B$
110	$A - B$
111	SLT


Review: ALU

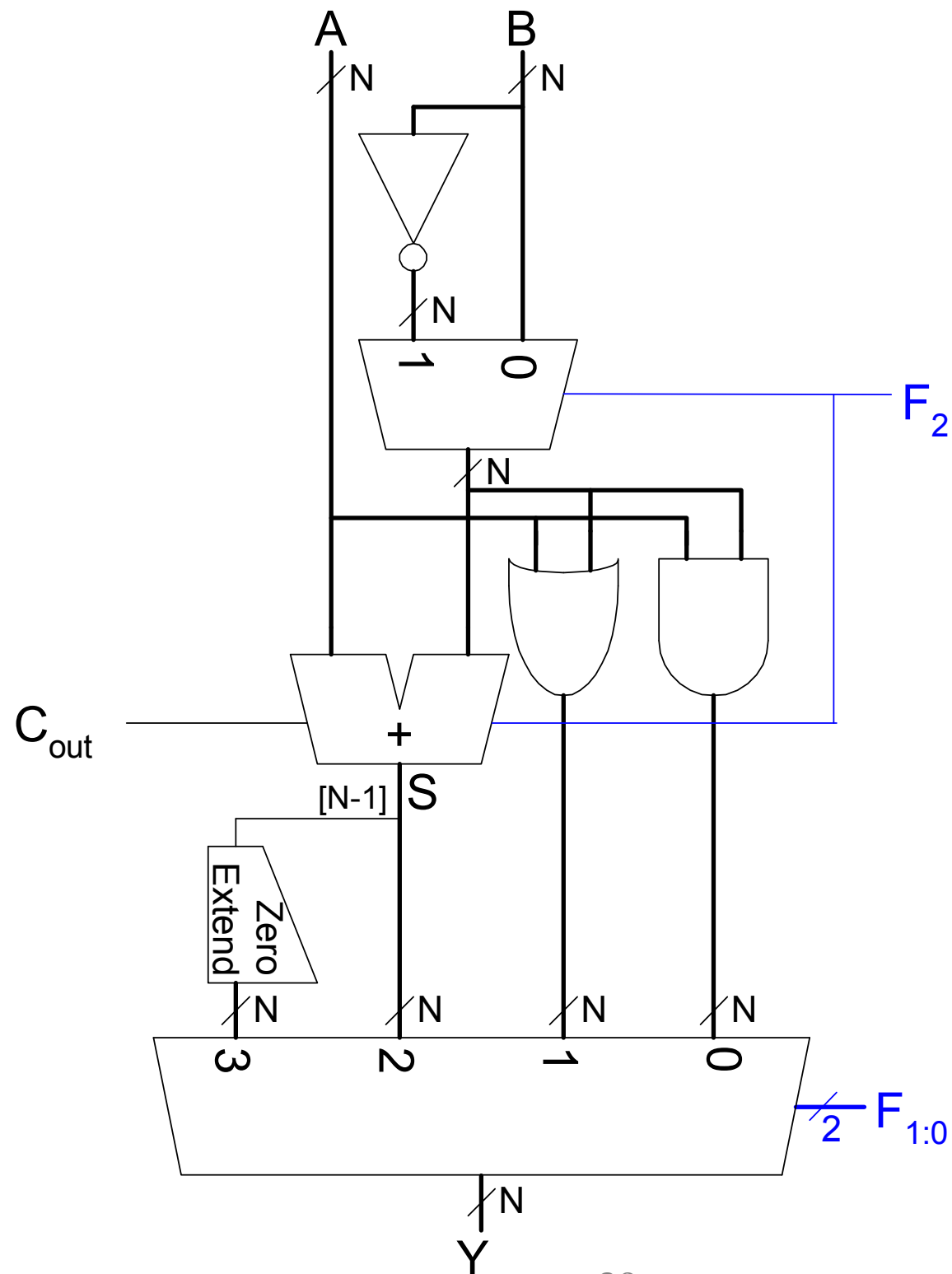

Control Unit: ALU Decoder


ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used

ALUOp _{1:0}	Funct	ALUControl _{2:0}
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)

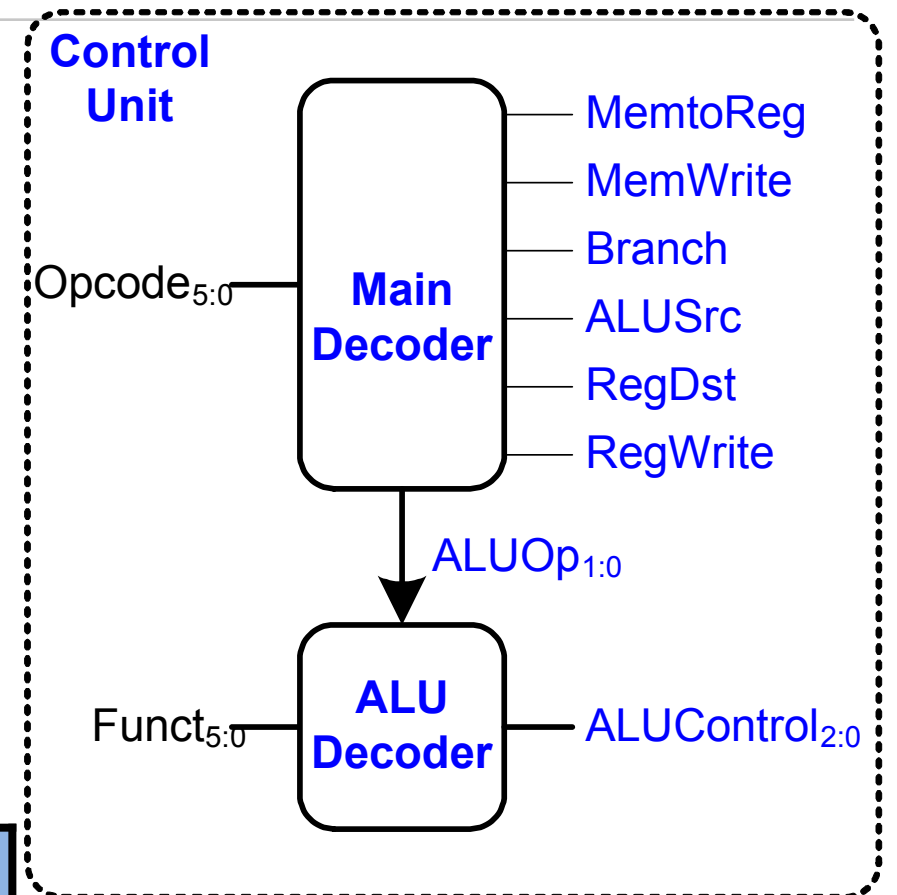

Control Unit Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000							
lw	100011							
sw	101011							
beq	000100							

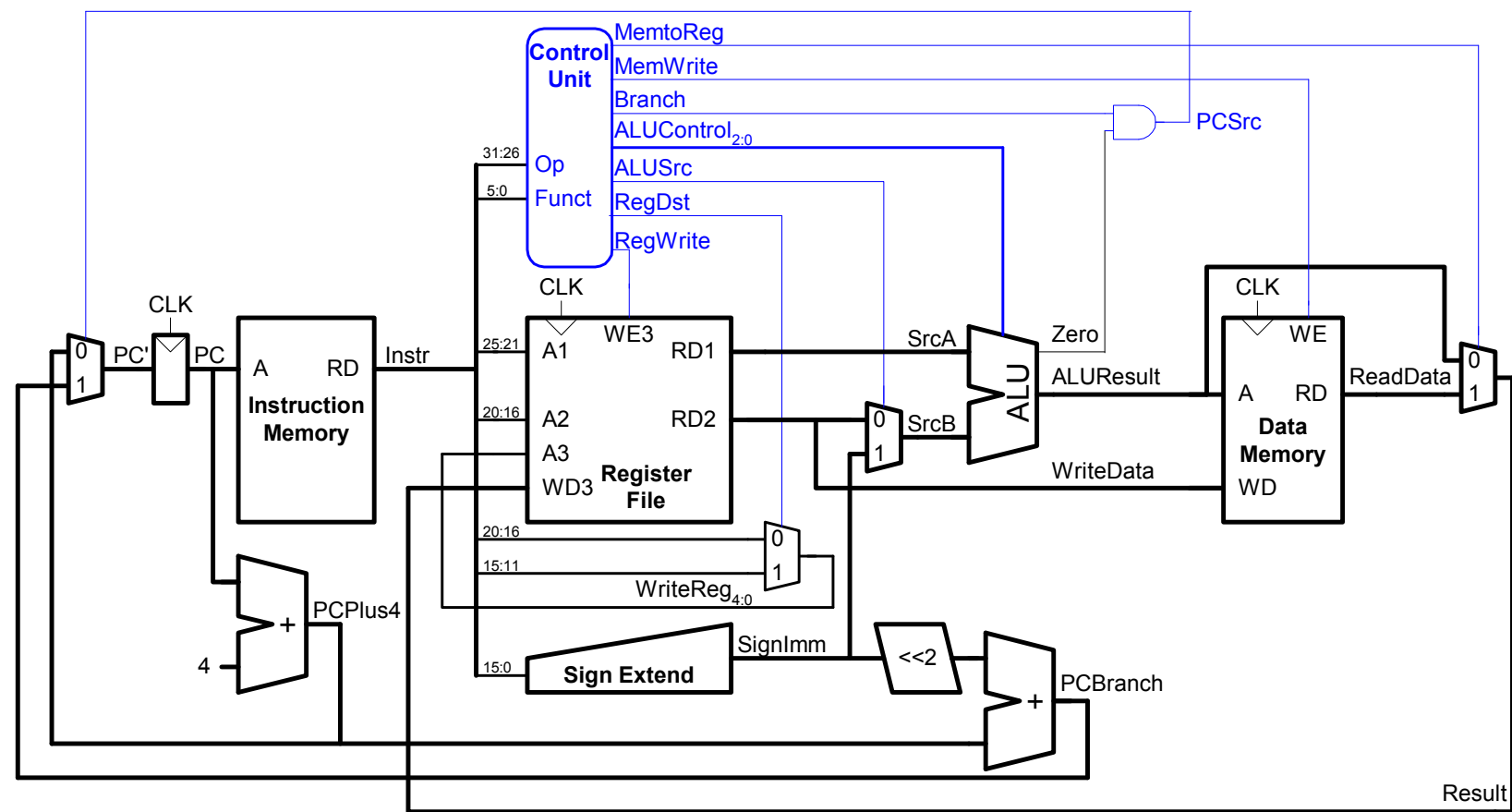


Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	0	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

Review: What We Have So Far

MIPS State Elements

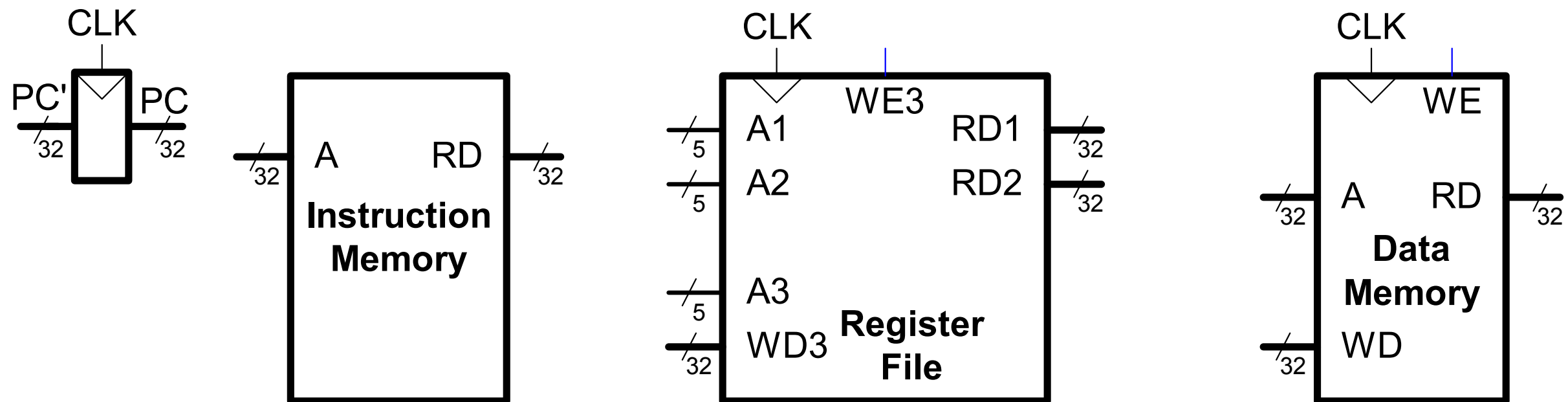

- ❖ Instruction memory, register file, and data memory, are being **read** as combinational circuit, i.e., data change follows address change, while the writing follows clock-edge
- ❖ **Benefits:** all elements are synchronized, while MIPS processor is a FSM!

Overview: Single-Cycle Control

R-Type


op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

I-Type


op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

J-Type


op	addr
6 bits	26 bits

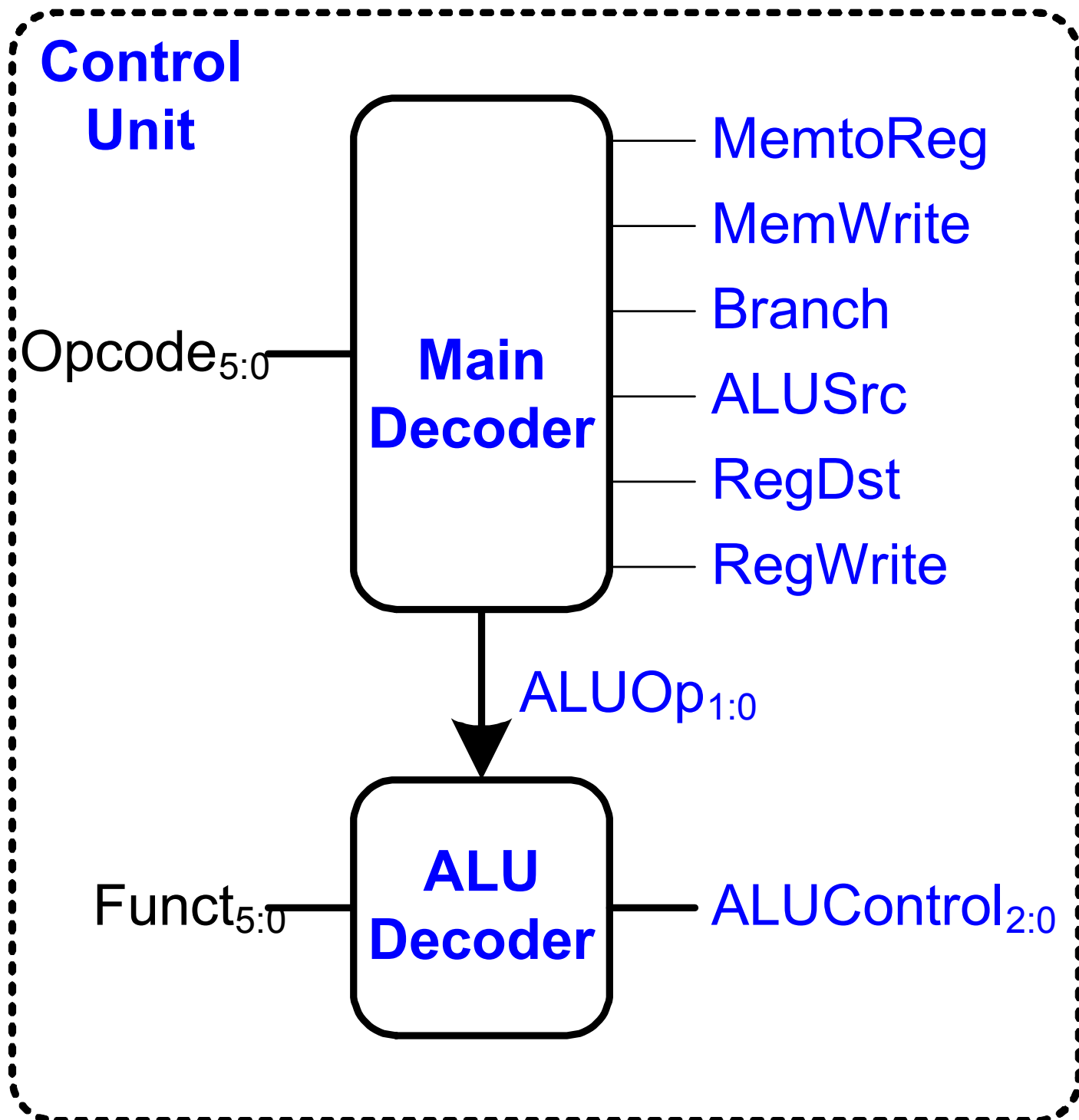

Single-Cycle Datapath

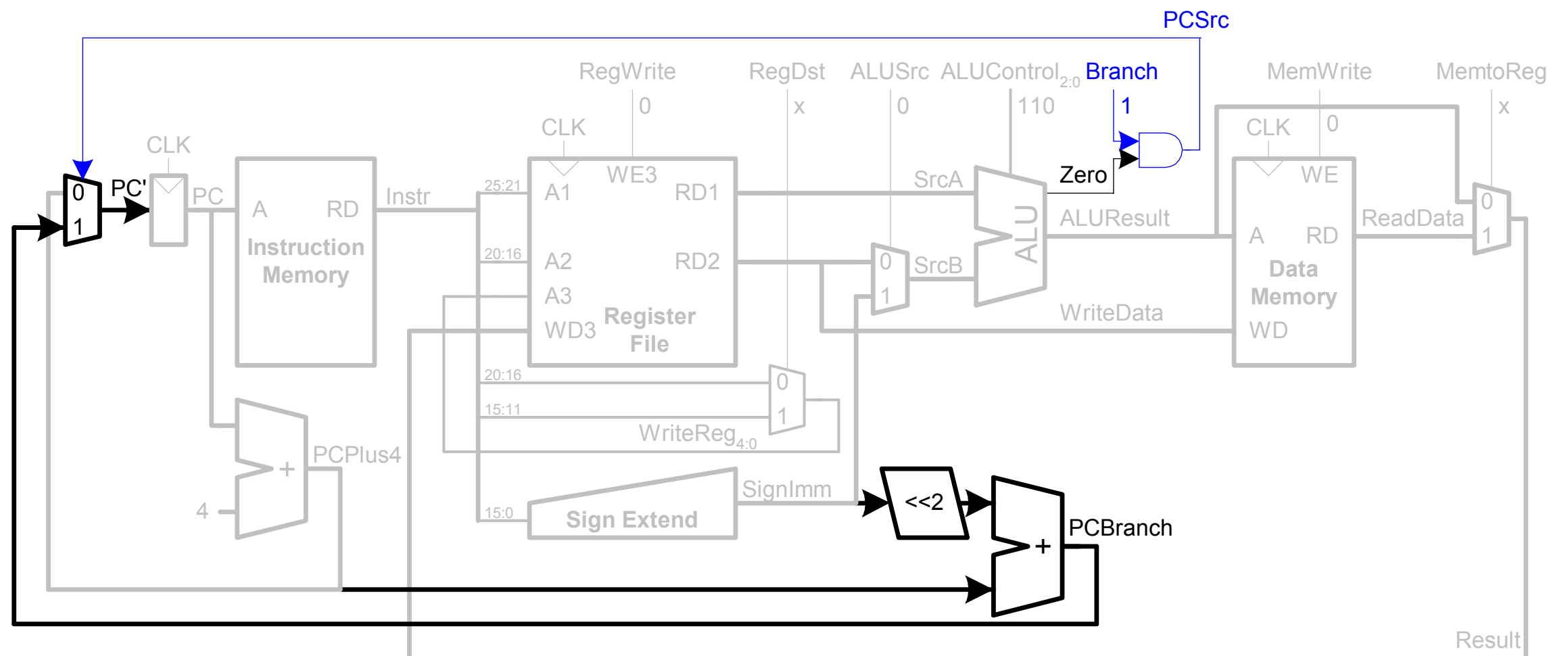


Single-Cycle Processor

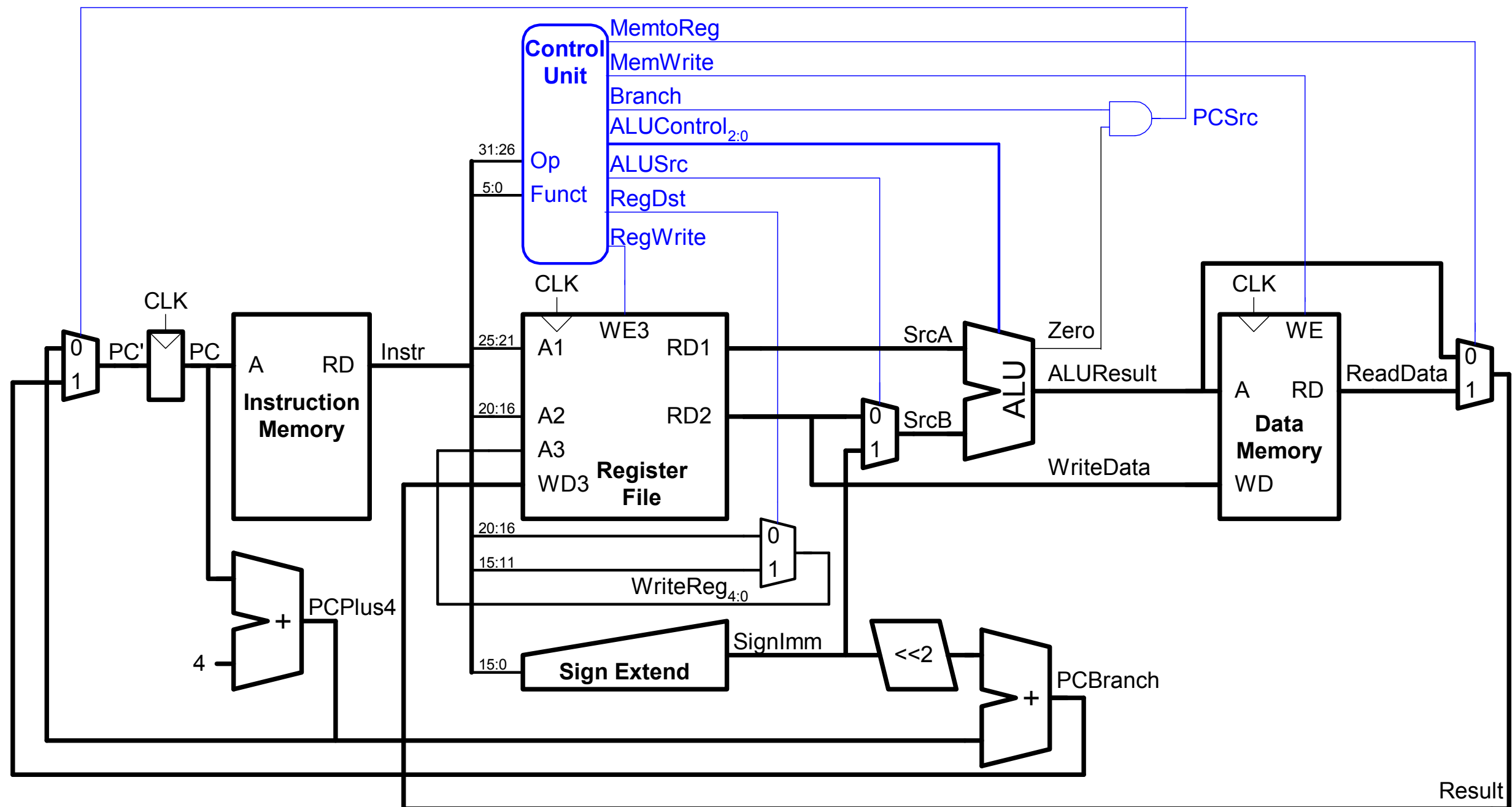

Single-Cycle Datapath: or

or	<code>or \$1, \$2, \$3</code>	<code>\$1=\$2 \$3</code>	Bitwise OR
-----------	-------------------------------	--------------------------	------------

Single-Cycle Datapath: or

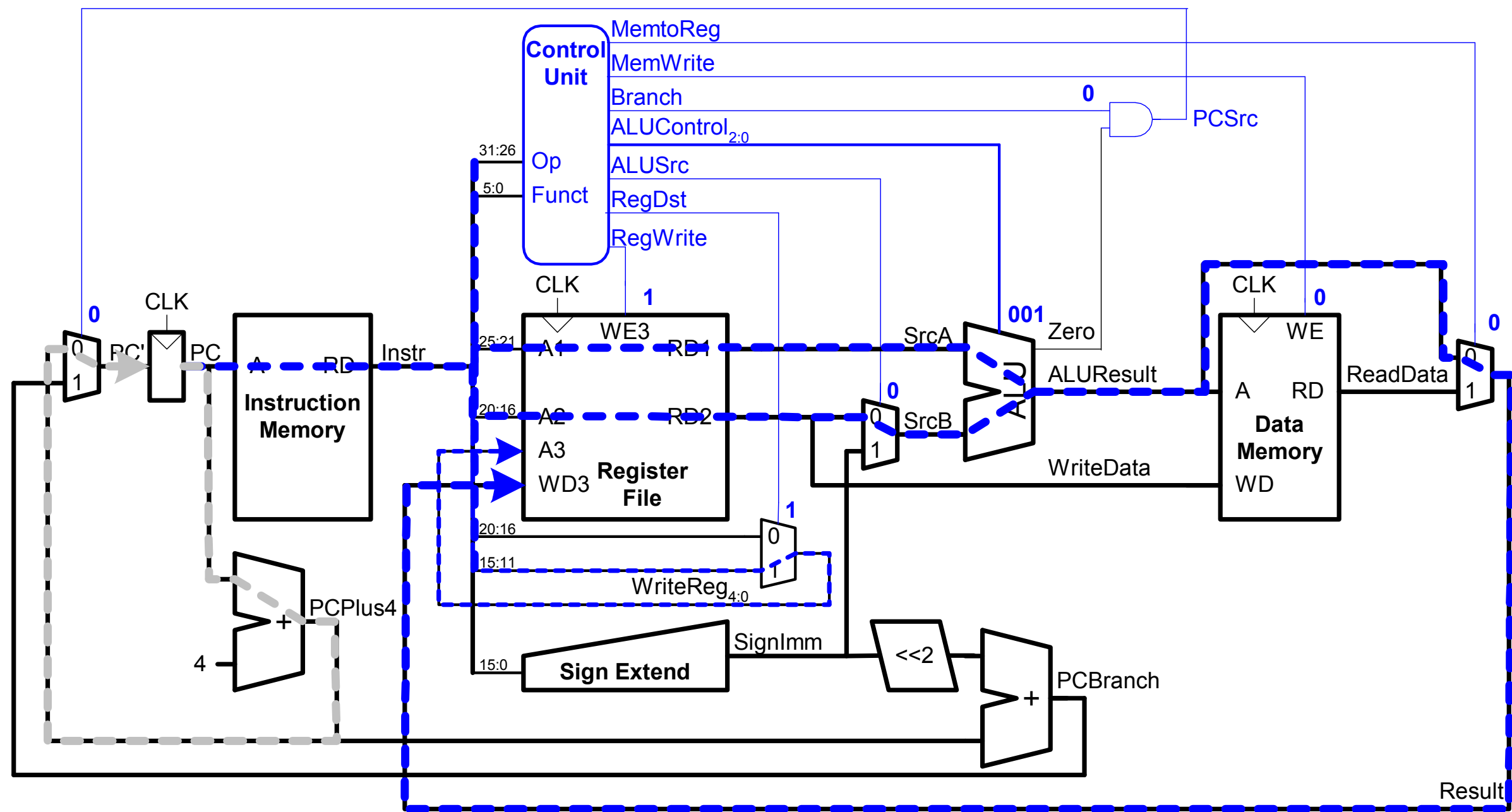

or

or \$1, \$2, \$3


\$1=\$2|\$3

Bitwise OR

Extended Functionality: addi

and immediate	<code>andi \$1, \$2, 100</code>	<code>\$1=\$2&100</code>	Bitwise AND with immediate value
----------------------	---------------------------------	------------------------------	----------------------------------

Extended Functionality: addi

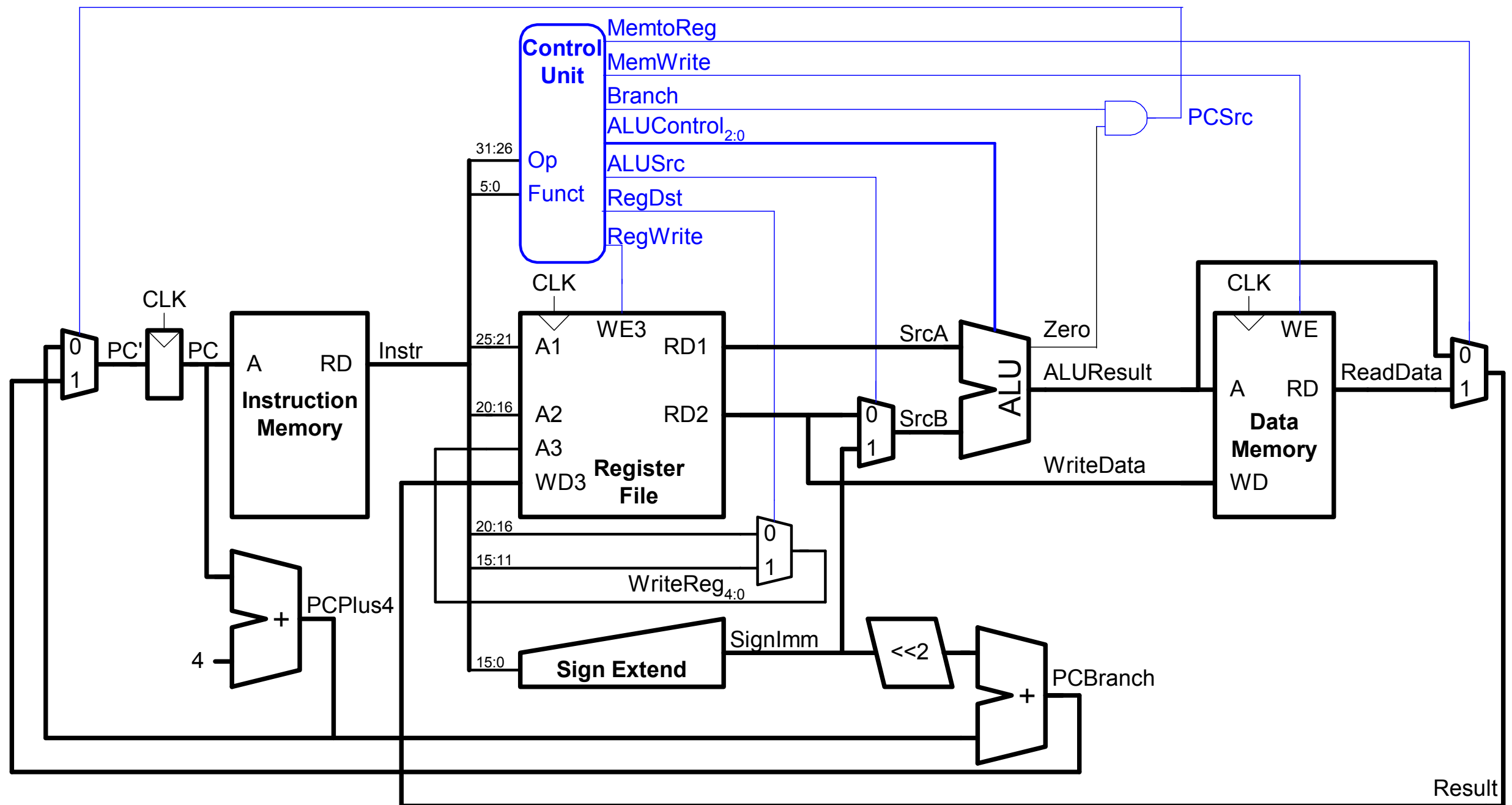


and immediate

`andi $1, $2, 100`

`$1=$2&100`

Bitwise AND with immediate value

Extended Functionality: addi

 

and immediate

`andi $1, $2, 100`

`$1=$2&100`

Bitwise AND with immediate value

Control Unit: addi

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
addi	001000							

Control Unit: addi

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
addi	001000	1	0	1	0	0	0	00

Extended Functionality: j

Unconditional Branching: jump (j)

MIPS assembly

```
addi $s0, $0, 4      # $s0 = 4
addi $s1, $0, 1      # $s1 = 1
j      target        # jump to target
sra   $s1, $s1, 2
addi  $s1, $s1, 1
sub   $s1, $s1, $s0

target:
add   $s1, $s1, $s0
```


Unconditional Branching: jump (j)

MIPS assembly

```
addi $s0, $0, 4      # $s0 = 4
addi $s1, $0, 1      # $s1 = 1
j      target        # jump to target
sra   $s1, $s1, 2     # not executed
addi  $s1, $s1, 1     # not executed
sub   $s1, $s1, $s0    # not executed

target:
add   $s1, $s1, $s0    # $s1 = 1 + 4 = 5
```

Extended Functionality: j

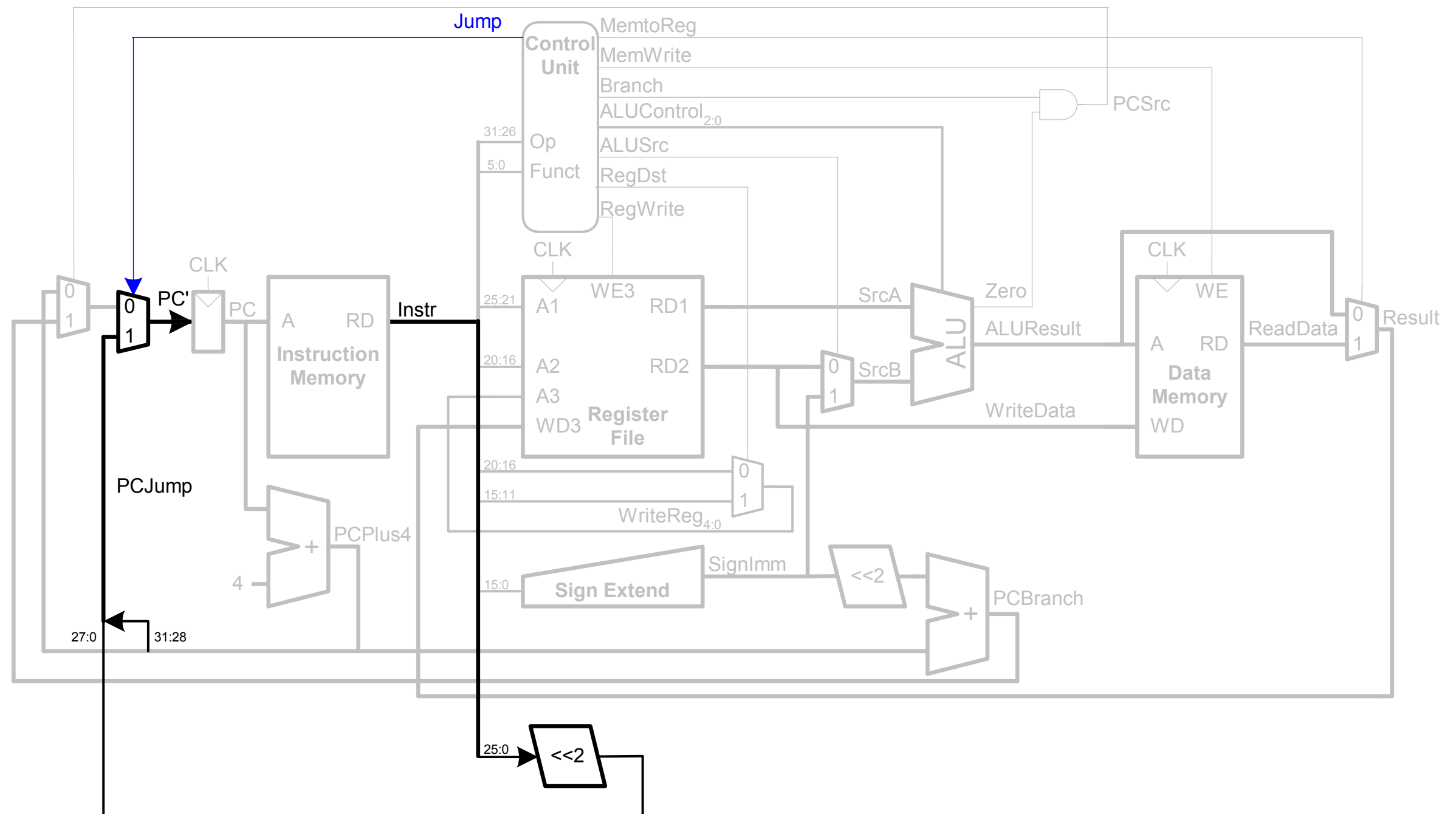

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	000100								

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	000100	0	X	X	X	0	X	XX	1


Review: Processor Performance

Program Execution Time

= (#instructions)(cycles/instruction)(seconds/cycle)

= # instructions x CPI x T_c

Single-Cycle Performance

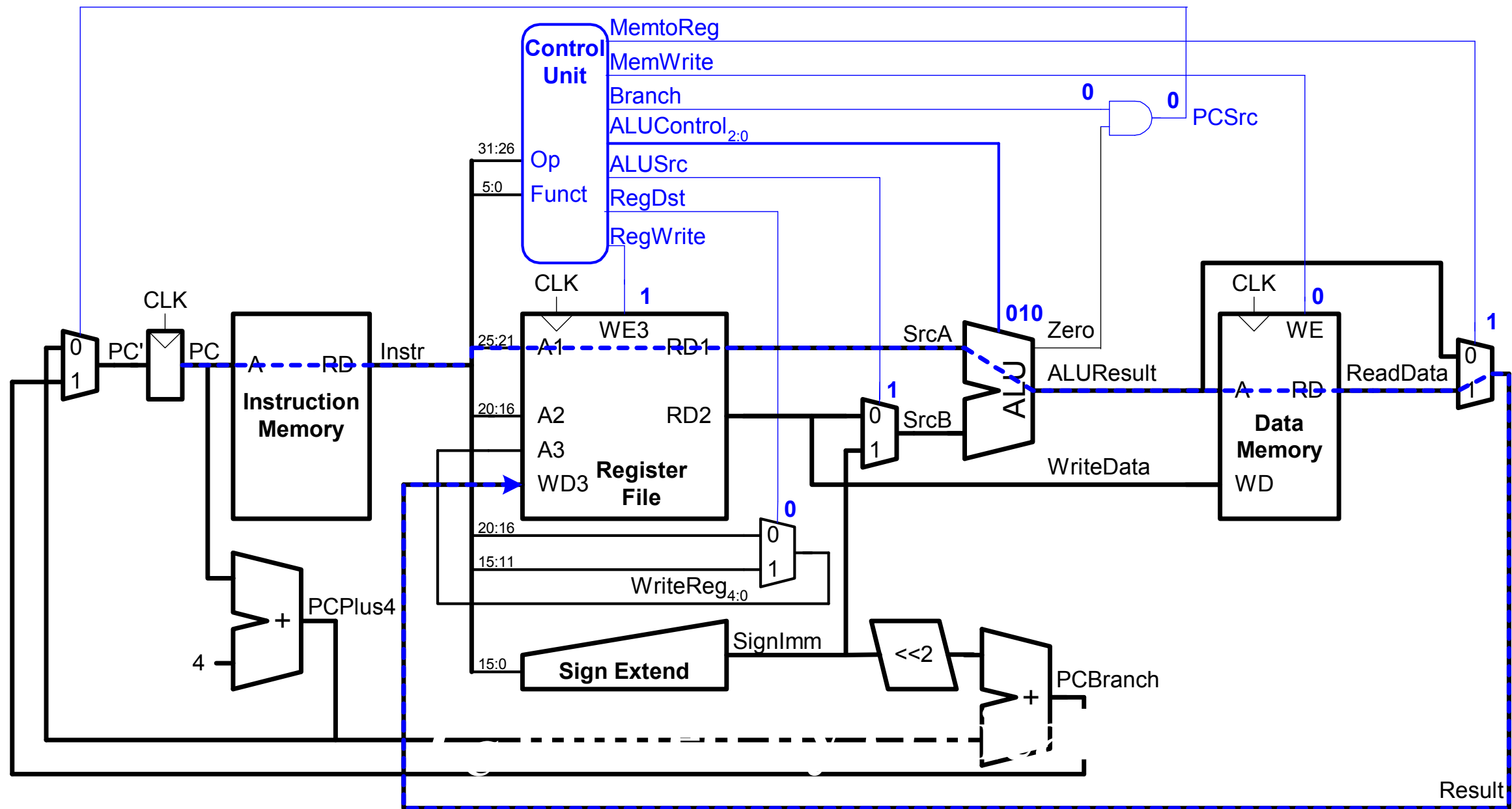

Single-Cycle Performance

- Single-cycle critical path:

$$T_c = t_{pcq_PC} + t_{mem} + \max(t_{RFread}, t_{sext} + t_{mux}) + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- Typically, limiting paths are:

- memory, ALU, register file

- $T_c = t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup}$

Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}T_c &= t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup} \\&= [30 + 2(250) + 150 + 25 + 200 + 20] \text{ ps} \\&= 925 \text{ ps}\end{aligned}$$

Single-Cycle Performance Example

Program with 100 billion instructions:

$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_C \\ &= (100 \times 10^9)(1)(925 \times 10^{-12} \text{ s}) \\ &= \mathbf{92.5 \text{ seconds}}\end{aligned}$$