

EECE 2322: Fundamentals of Digital Design and Computer Organization


Lecture 2_2: Gates and Numbers

Xiaolin Xu

Department of ECE
Northeastern University


Gate Outputs Created by All Input Combinations

- ❖ XN stands for X' or NOT(X)

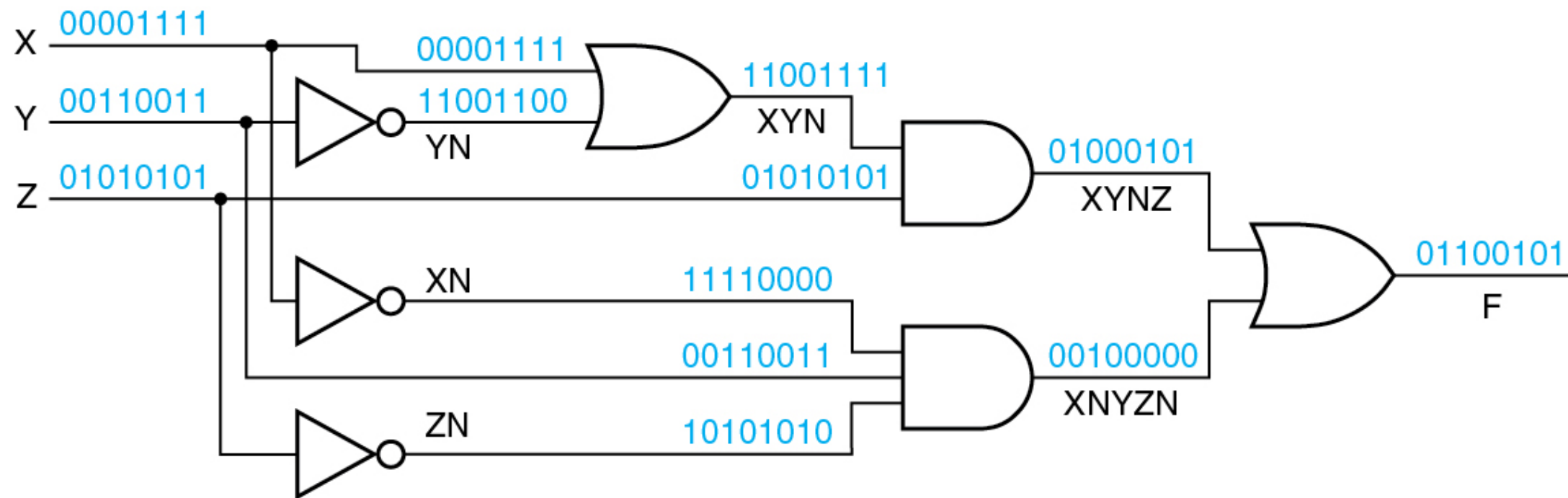


From Circuit to Truth Table

❖ Think about why

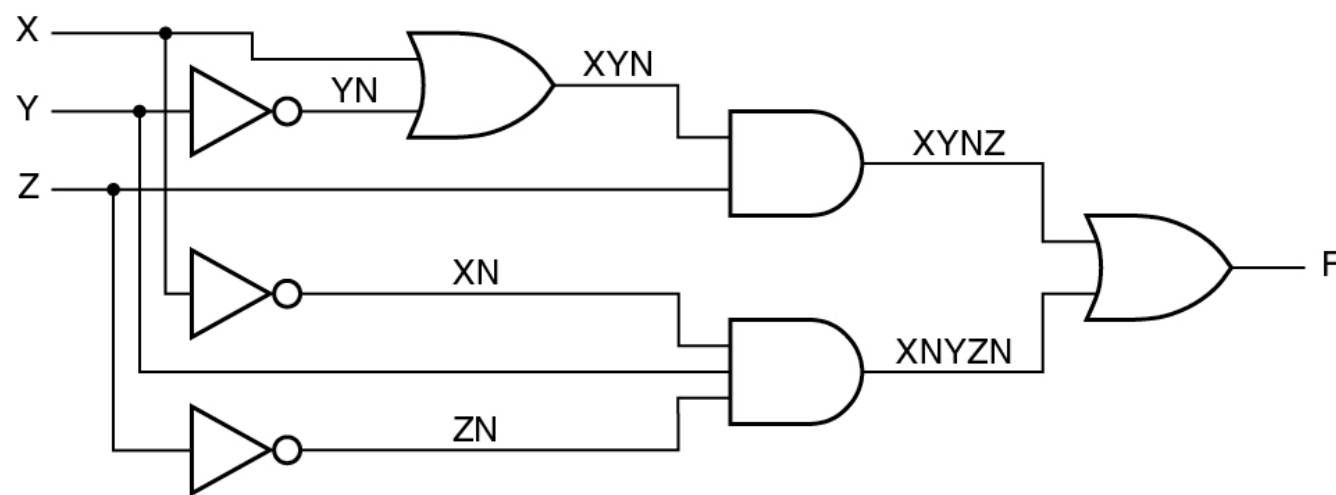


<i>Row</i>	<i>X</i>	<i>Y</i>	<i>Z</i>	<i>F</i>
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1


Logic Expressions for Signal Lines

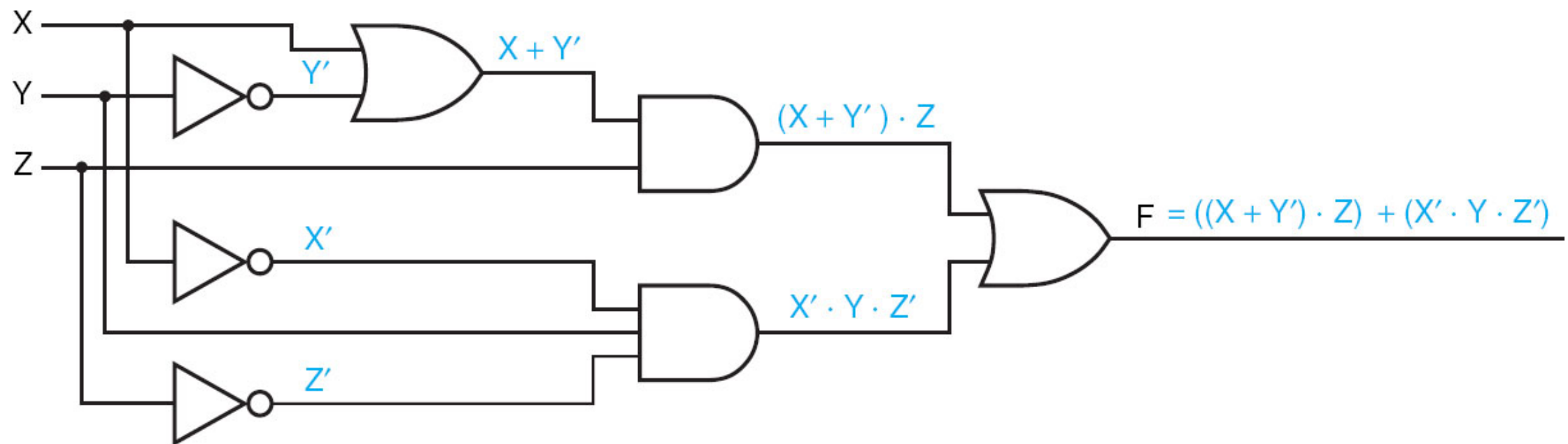


Two-Level AND-OR Circuit

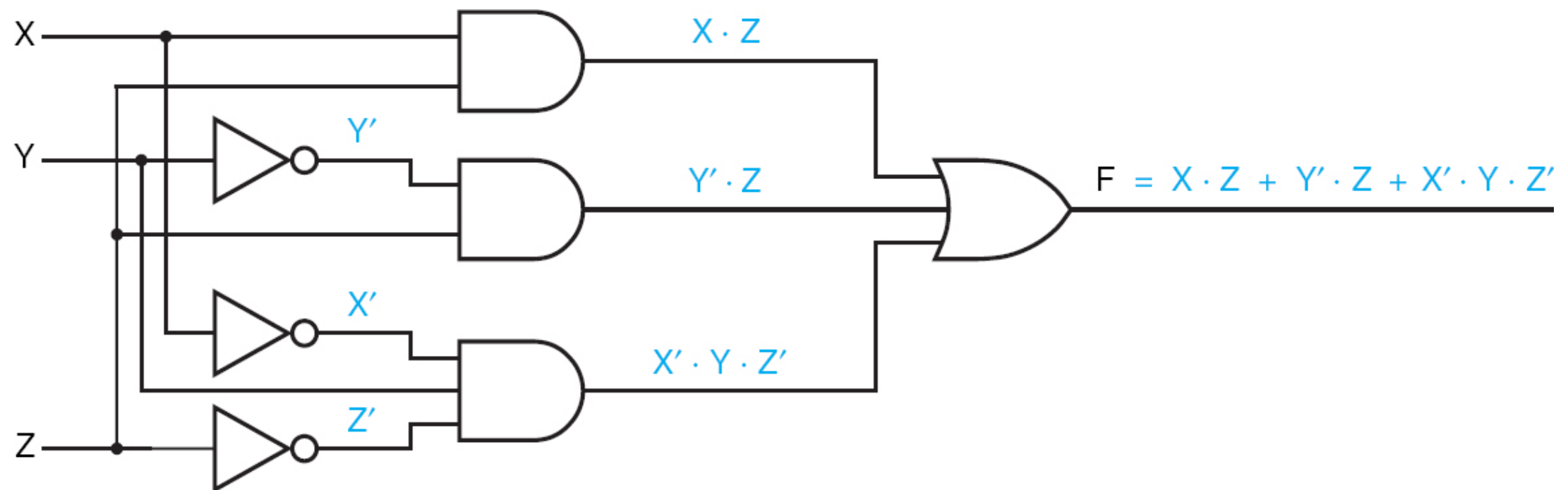

Two-Level OR-AND Circuit

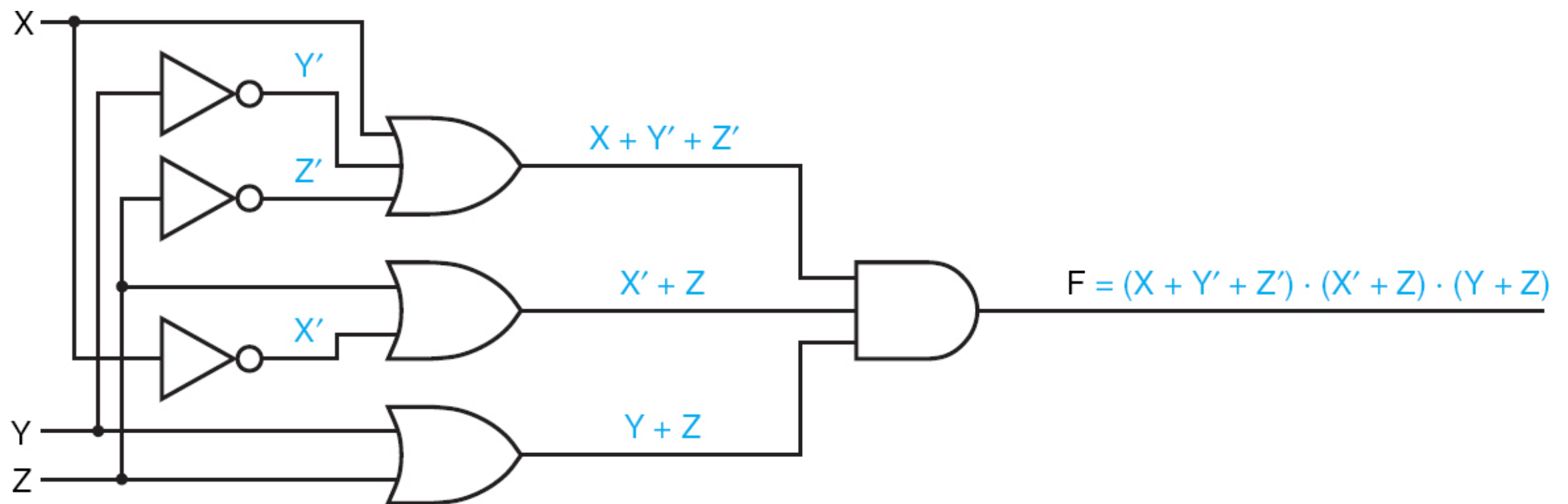

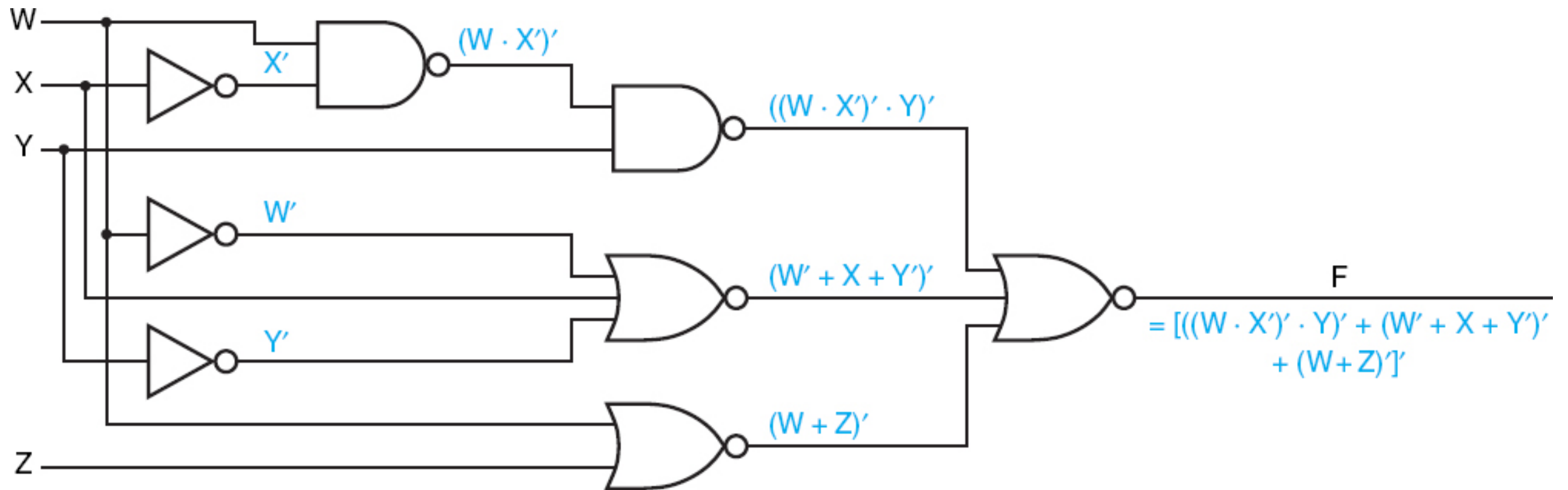Algebraic Analysis of a Logic Circuit with NAND and NOR Gates



Logic Synthesis


- ❖ What is logic synthesis? and Why?

Logic Synthesis

- ❖ What is logic synthesis? and Why?
- ❖ Only some standard logic cells are used in practical design.

Lab 0: XOR Gate

- ❖ XOR: Exclusive-OR gate

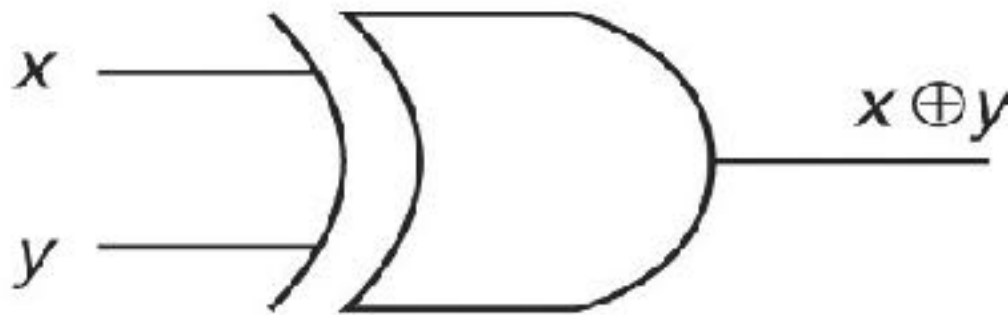


Truth Table:

X	Y	F
0	0	0
0	1	1
1	0	1
1	1	0

Symbol \oplus to designate its operation.

Similar to the OR gate but excludes (has the value 0 for) the combination with both X and Y equal to 1.

Lab 0: XOR with NAND Gates

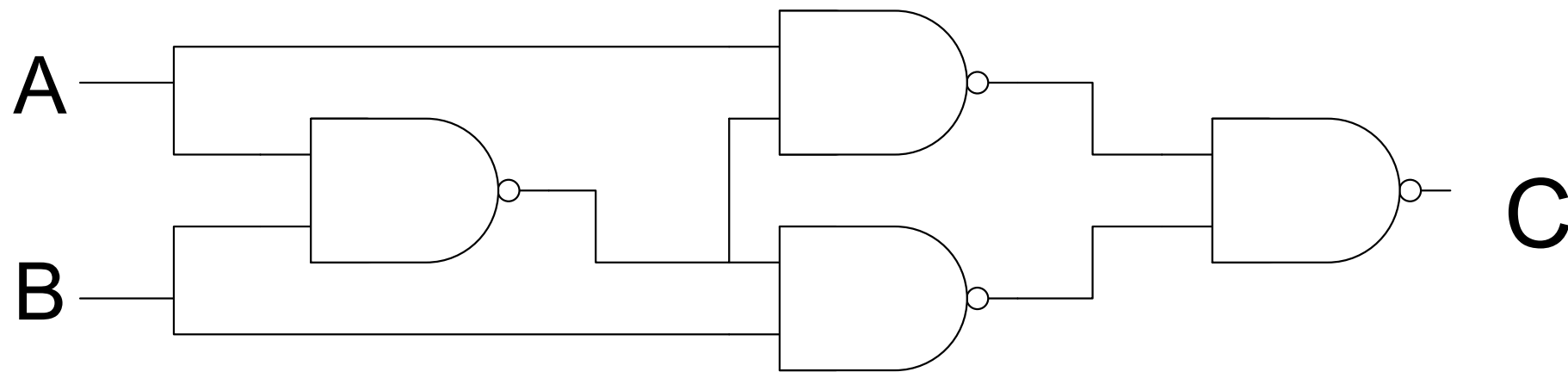

Properties of XOR Gate

$$X \oplus 0 = X$$

$$X \oplus X = 0$$

$$X \oplus \bar{Y} = \overline{X \oplus Y}$$

$$X \oplus 1 = \bar{X}$$

$$X \oplus \bar{X} = 1$$

$$\bar{X} \oplus Y = \overline{X \oplus Y}$$

Commutative:

$$A \oplus B = B \oplus A$$

Associative:


$$(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$$

Binary, Decimal, Octal, and Hexadecimal Numbers


<i>Binary</i>	<i>Decimal</i>	<i>Octal</i>	<i>3-Bit String</i>	<i>Hexadecimal</i>	<i>4-Bit String</i>
0	0	0	000	0	0000
1	1	1	001	1	0001
10	2	2	010	2	0010
11	3	3	011	3	0011
100	4	4	100	4	0100
101	5	5	101	5	0101
110	6	6	110	6	0110
111	7	7	111	7	0111
1000	8	10	—	8	1000
1001	9	11	—	9	1001
1010	10	12	—	A	1010
1011	11	13	—	B	1011
1100	12	14	—	C	1100
1101	13	15	—	D	1101
1110	14	16	—	E	1110
1111	15	17	—	F	1111

Binary Additions

X	190		1	0	1	1	1	1	1	0
Y	+ 141	+	1	0	0	0	1	1	0	1
X + Y	<u>331</u>		1	0	1	0	0	1	0	1

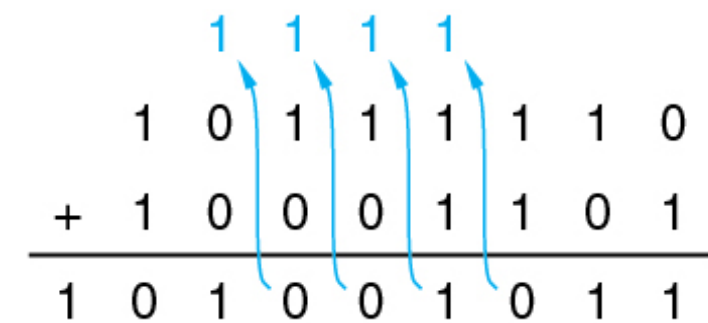

X	173		1	0	1	0	1	1	0	1
Y	+ 44	+	0	0	1	0	1	1	0	0
X + Y	<u>217</u>		1	1	0	1	1	0	0	1

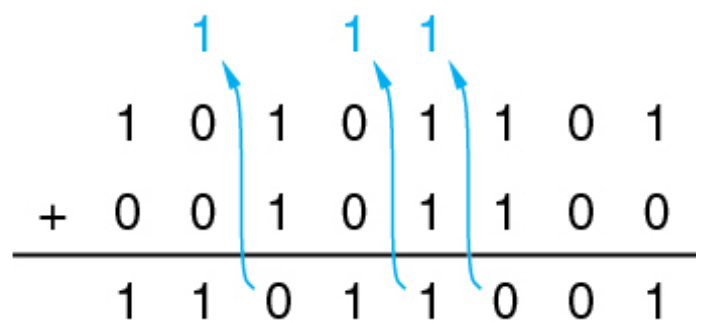

Binary Subtractions

Example 1: 229 - 46

minuend	X	229
subtrahend	Y	- 46
difference	X - Y	183

Binary representation of 229: 11100101
 Binary representation of 46: 0010110
 Binary representation of 183: 10110111

(Note: In the original image, the 10110111 result is shown with a leading 1, making it 110110111, which is 223. This appears to be a typo in the original image.)

Example 2: 210 - 109

	X	210
	Y	- 109
X - Y		101

Binary representation of 210: 11010110
 Binary representation of 109: 01101101
 Binary representation of 101: 0110101

Borrowing Process for Example 1:

Must borrow 1, yielding the new subtraction $10 - 1 = 1$

After the first borrow, the new subtraction for this column is $0 - 1$, so we must borrow again.

The borrow ripples through three columns to reach a borrowable 1, i.e., $100 = 011$ (the modified bits) + 1 (the borrow)

Representation of Negative Numbers

- ❖ Computer needs to know negative numbers as well!
- ❖ Signed-Magnitude Representation
- ❖ Complement Number Systems
 - ❖ Two's complement representation
 - ❖ One's complement representation

Signed-Magnitude Representation

- ❖ In the sign-magnitude system, a number is interpreted in the usual way, and the sign is denoted with:
 - ❖ 1 for -
 - ❖ 0 for +
- ❖ $01010101_2 = +85_{10}$ $11010101_2 = -85_{10}$
- ❖ $01111111_2 = +127_{10}$ $11111111_2 = -127_{10}$

Two's Complement Representation

- ❖ In the two's complement system, a n-bit number is obtained by subtracting it from 2^n
- ❖ Suppose we want to get -17
- ❖ $17_{10} = 00010001_2$
- ❖ $2^8 - 17_{10} = ?$
 - ❖ $2^n = (2^{n-1}) + 1$
 - ❖ $2^n - A = (2^n - 1 - A) + 1$
 - ❖ $2^n - 1 = 1111...111$
- ❖ $-17_{10} = 11111111_2 - 00010001_2 + 1 = ?$

Two's Complement Representation

- ❖ $17_{10} = 11111111_2 - 00010001_2 + 1$
- ❖ $= 11101110_2 + 1$
- ❖ $= 11101111_2$
- ❖ $= -17_{10}$
- ❖ The MSB has a negative weight $-2^{(n-1)}$

Two's Complement Representation

❖ Why?

Two's Complement Representation

- ❖ Computer is stupid
- ❖ Add two numbers 55 and 11 together
- ❖ $0011\ 0111_2(55)$
- ❖ $+\ 0000\ 1011_2(11)$
- ❖ $0100\ 0010_2(66)$

Two's Complement Representation

- ❖ Computer is stupid
- ❖ Subtract 11 from 55
 - ❖ $-11 = 1111\ 1111_2 - 0000\ 1011_2 + 1 = 1111\ 0100_2 + 1 = 1111\ 0101_2$
- ❖ $0011\ 0111_2(55)$
- ❖ $+ 1111\ 0101_2(-11)$
- ❖ $0010\ 1100_2(44)$

Two's Complement Representation

- ❖ Computer is stupid
- ❖ Subtract 55 from 11
 - ❖ $-55 = 1111\ 1111_2 - 0011\ 0111_2 + 1 = 1100\ 1000_2 + 1 = 1100\ 1001_2$
- ❖ $0000\ 1011_2(11)$
- ❖ $+ 1100\ 1001_2(-55)$
- ❖ $1101\ 0100_2(-44)$

What is the “E-reason”?

- ❖ Any reason to design/use two's complement systems?

One's Complement Representation

- ❖ In the one's complement system, a n-bit number is obtained by subtracting it from $2^n - 1$
- ❖ Suppose we want to get -17
- ❖ $17_{10} = 00010001_2$
- ❖ $-17_{10} = 11111111_2 - 00010001_2 = ?$

Decimal and 4-Bit Numbers

<i>Decimal</i>	<i>Two's Complement</i>	<i>Ones' Complement</i>	<i>Signed Magnitude</i>	<i>Excess 2^{m-1}</i>
-8	1000	—	—	0000
-7	1001	1000	1111	0001
-6	1010	1001	1110	0010
-5	1011	1010	1101	0011
-4	1100	1011	1100	0100
-3	1101	1100	1011	0101
-2	1110	1101	1010	0110
-1	1111	1110	1001	0111
0	0000	1111 or 0000	1000 or 0000	1000
1	0001	0001	0001	1001
2	0010	0010	0010	1010
3	0011	0011	0011	1011
4	0100	0100	0100	1100
5	0101	0101	0101	1101
6	0110	0110	0110	1110
7	0111	0111	0111	1111

Binary Multiplication

1 0 1 0	→	Multiplicand
× 1 0 1 1	→	Multiplier

1 0 1 0	→	Partial product 1
1 0 1 0	→	Partial product 2
0 0 0 0	→	Partial product 3
1 0 1 0	→	Partial product 4


1 1 0 1 1 1 0		

Binary Division

19	10011	quotient
11 $\overline{)217}$	1011 $\overline{)11011001}$	dividend
11	1011	shifted divisor
$\underline{107}$	0101	reduced dividend
99	0000	shifted divisor
$\underline{8}$	1010	reduced dividend
	0000	shifted divisor
	10100	reduced dividend
	1011	shifted divisor
	10011	reduced dividend
	1011	shifted divisor
	1000	remainder


Binary Code and Real-world Applications

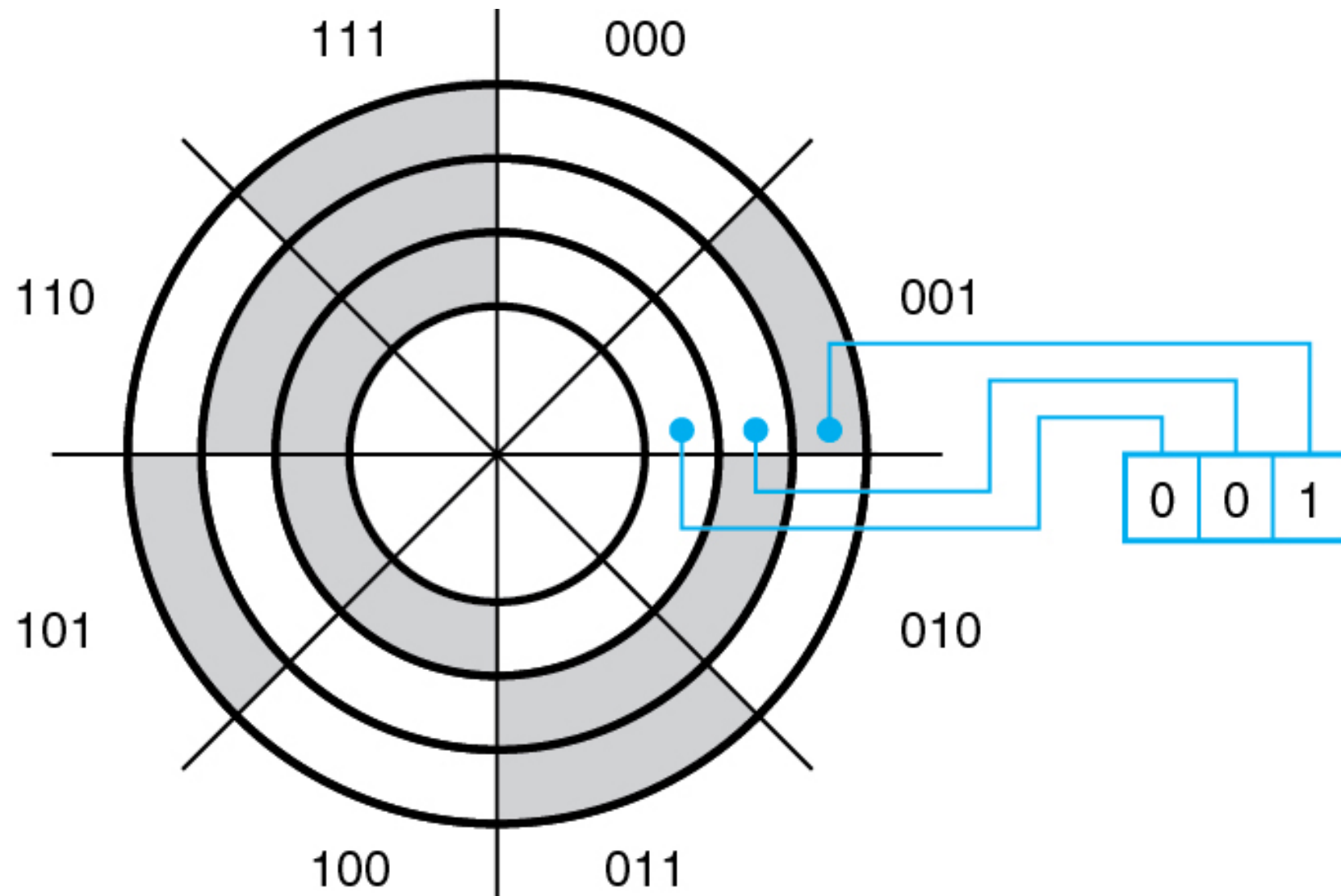- ❖ A Mechanical Encoding Disk Using a 3-Bit Binary Code
- ❖ Any problem?



Binary Code and Real-world Applications

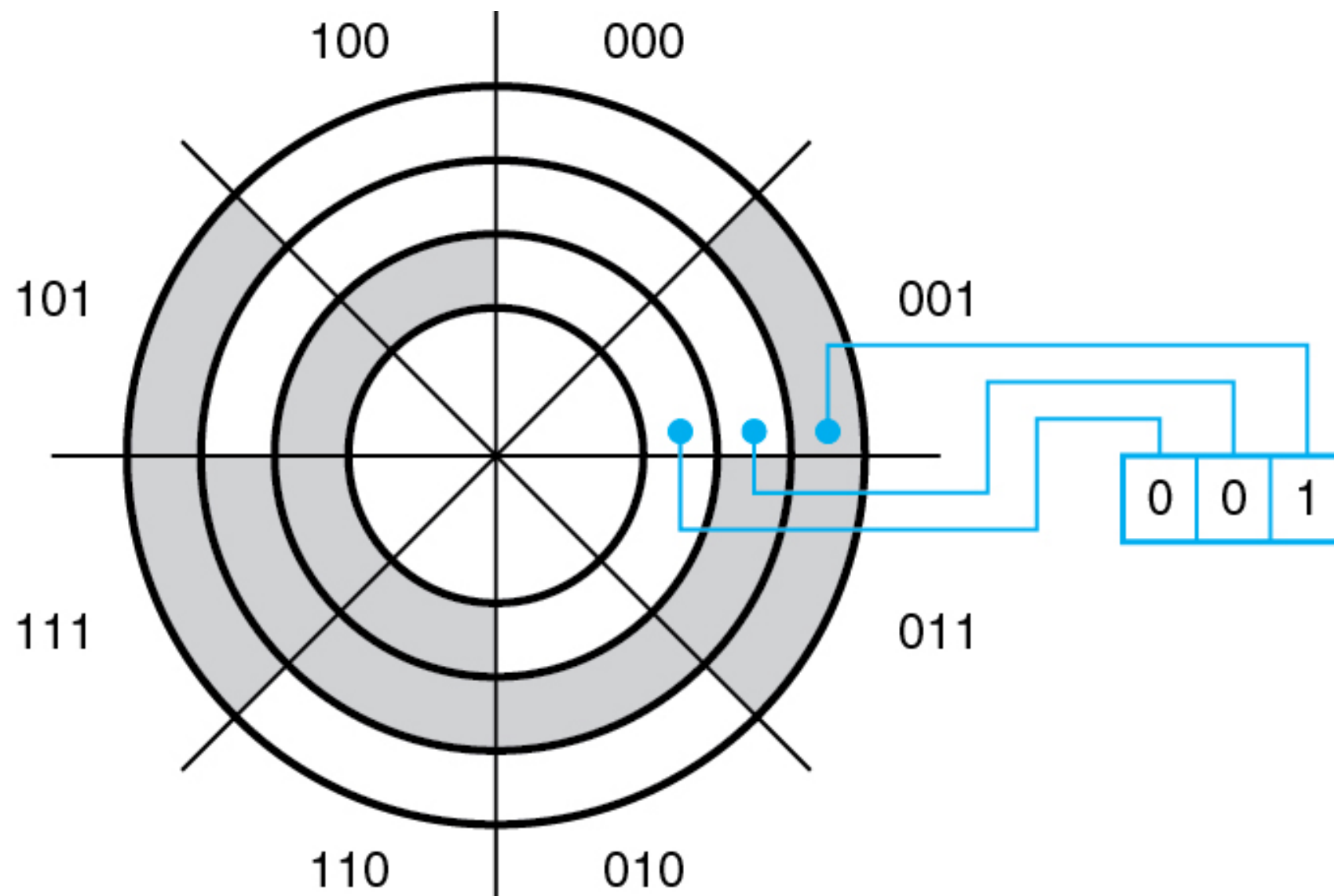- ❖ A Mechanical Encoding Disk Using a 3-Bit Binary Code
 - ❖ Gray Code



Hamming Distance

- ❖ In information theory, the Hamming distance between two strings of equal length is the number of positions at which the corresponding symbols are different