

EECE 2322: Fundamentals of Digital Design and Computer Organization

Lecture 3_2: Verilog and FPGA

Xiaolin Xu
Department of ECE
Northeastern University

Blocking and Non-blocking

```
always @ (posedge clk )
if (reset == 0) begin
    y <= 0;
end else if (sel == 0) begin
    y <= a;
end else begin
    y <= b;
end
```

- ❖ initial
- ❖ begin
- ❖ B <= A;
- ❖ C <= B;
- ❖ end
- ❖ All results evaluated first, then assigned
 - ❖ Result is that old contents of B are in C

How to Make a Device Reconfigurable to Any Logic?

❖ In[1:0] Out

❖ 00 ?

❖ 01 ?

❖ 10 ?

❖ 11 ?

How to Make a Device Reconfigurable to Any Logic?

❖ In[1:0] Out

❖ 00 ?

❖ 01 ?

❖ 10 ?


❖ 11 ?

❖ **Reconfigure the memory!**

❖ **A memory cell can be written with a 1 or a 0**

Addressable Memory

 - ❖ SRAM: Static Random Accessible Memory
- ❖ A0-A3: address
- ❖ F: output
- ❖ How many memory cells?




LUT: Look-Up Table

- ❖ Look-up tables are how your logic actually gets implemented. Users can program what the output should be for every single possible input
- ❖ A LUT consists of a block of RAM that is indexed by the LUT's inputs. The output of the LUT is whatever value is in the indexed location in its RAM cell

LUT: Look-Up Table


- ❖ Look-up tables are how a function that a program actually gets implemented by looking up what the output is for every single possible input

 - ❖ A LUT consists of a block of memory indexed by the LUT's inputs. The output of the LUT is whatever is stored at the indexed location in its memory.




LUT: Look-Up Table

 - ❖ A K input LUT requires 2^k RAM cells to store function
- ❖ K Inputs are fed into LUT Mux to choose outputs
- ❖ An example 2-input LUT



2-input LUT with MUXes

- ❖ Muxes are built as a tree of Muxes

 

LUT: Look-Up Table



❖ In[1:0] Out

❖ 00 0

❖ 01 0


❖ 10 0

❖ 11 1

  

Implement an XOR gate with a 2-input LUT

 - ❖ What are the values stored in the memory cells?



Practice: Mapping a Random Function to a 4-input LUT


❖ Write down your answers

A	—	
B	—	
C	—	
D	—	

$$F = A C' + A B D' + B C' D'$$

A	B	C	D	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

 Practice: Mapping a Random Function to a 4-input LUT




$$F = A C' + A B D' + B C' D'$$

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0


Building more Complicated Logic

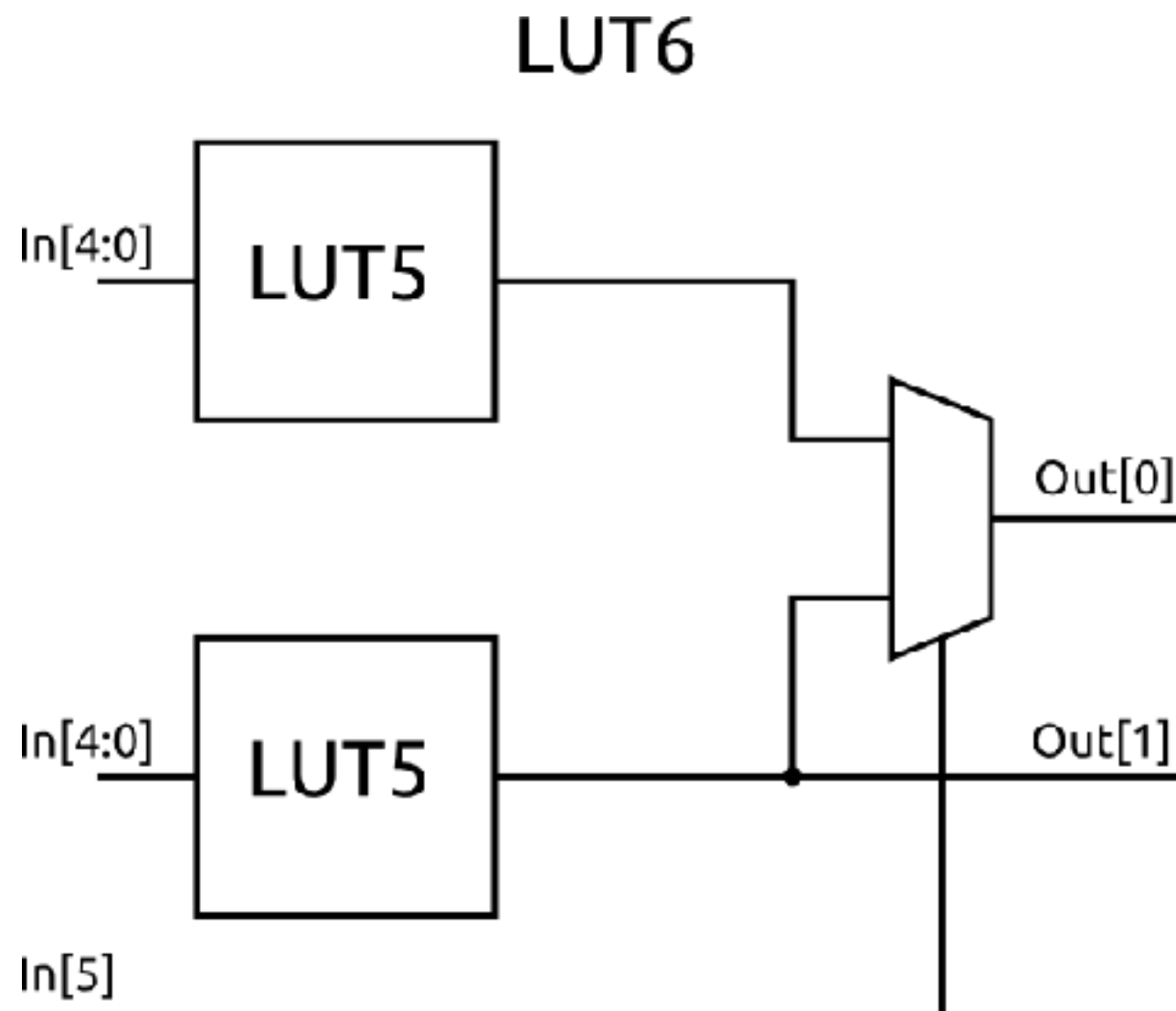- ❖ In the Xilinx Spartan 6 FPGA, each LUT is a 6-input LUT




Logic Slice

❖ LUT + MUXes + Flip-flop

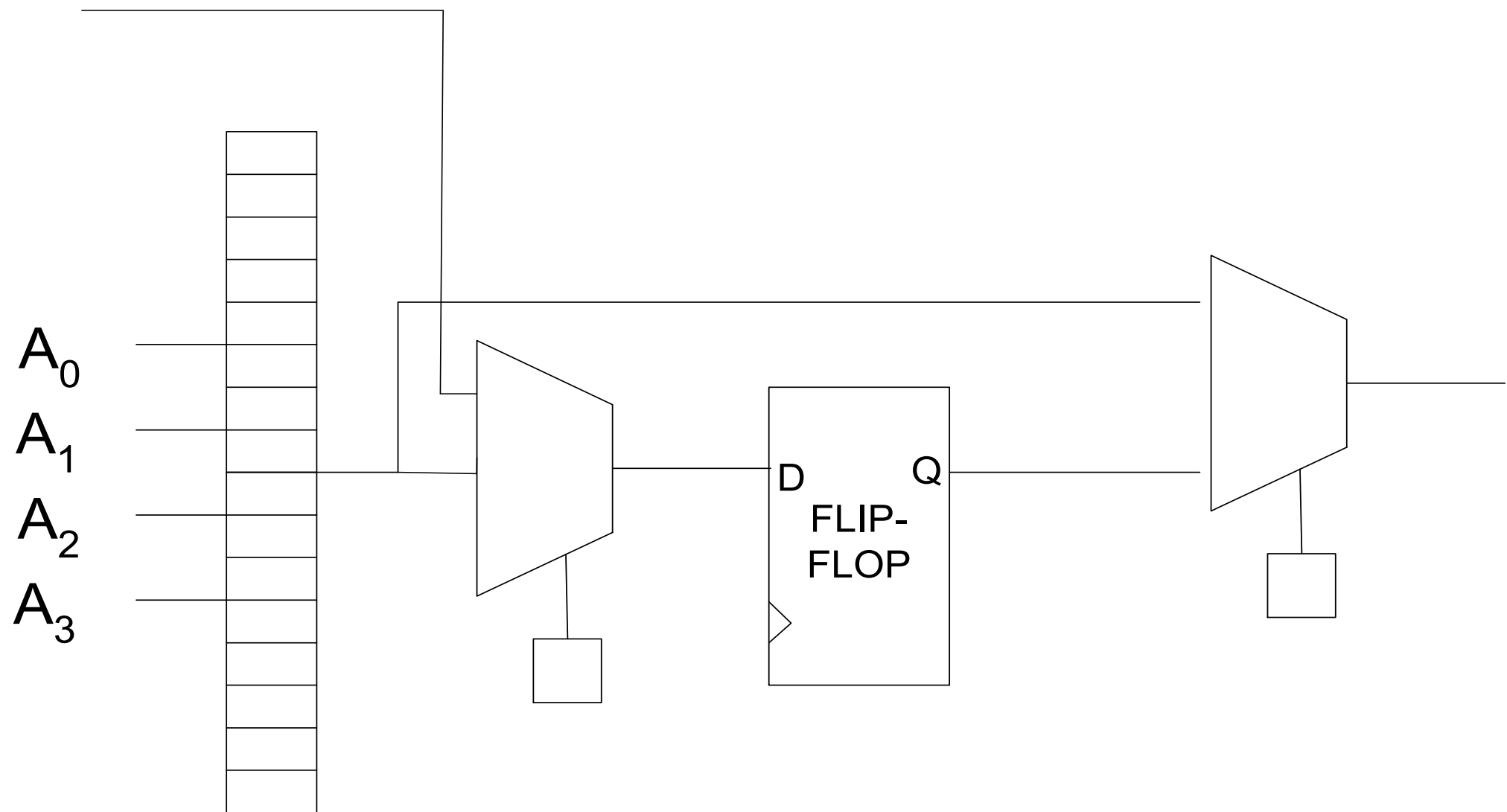


CLB: Configurable Logic Block


- ❖ Each CLB has two Slices

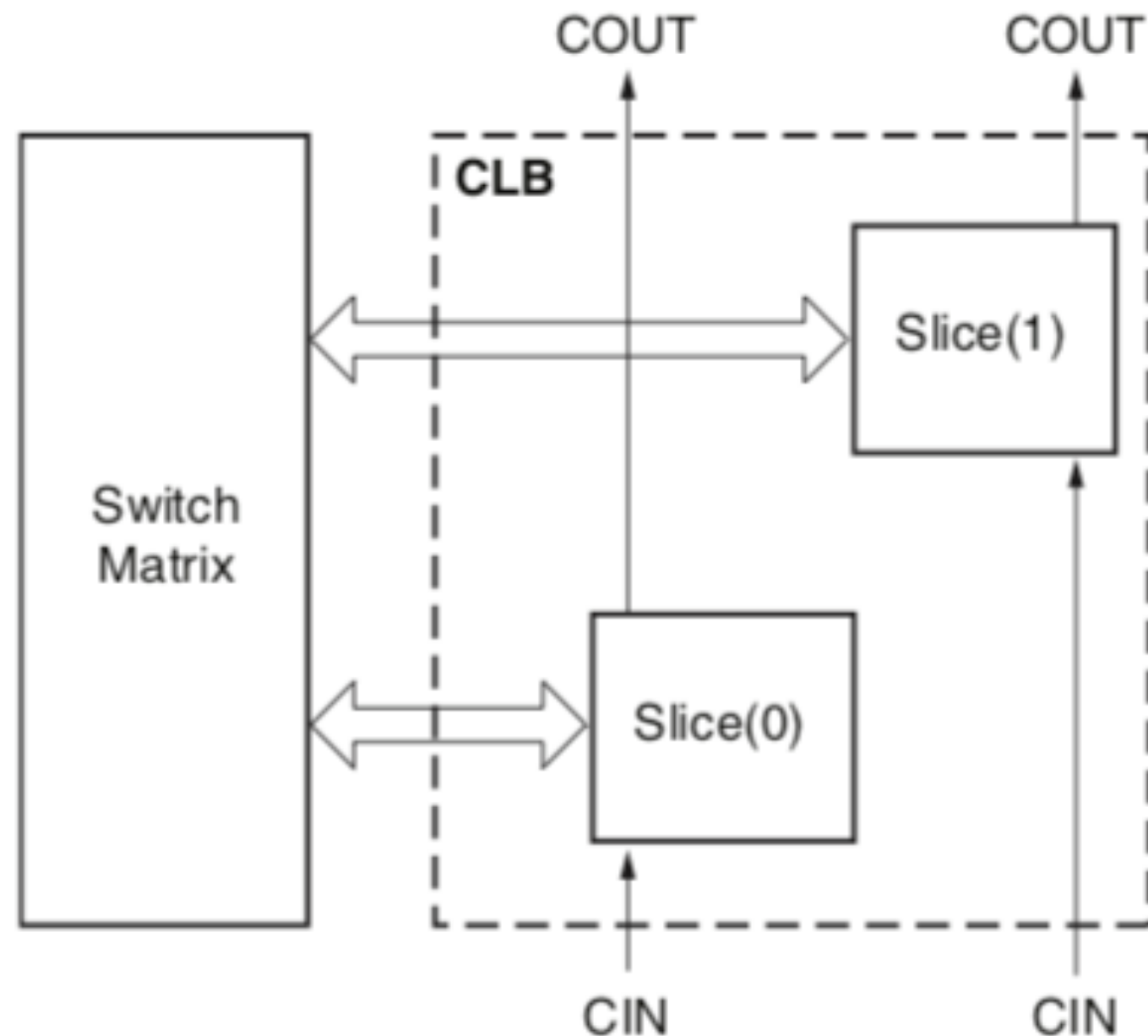


Combinational Logic Design

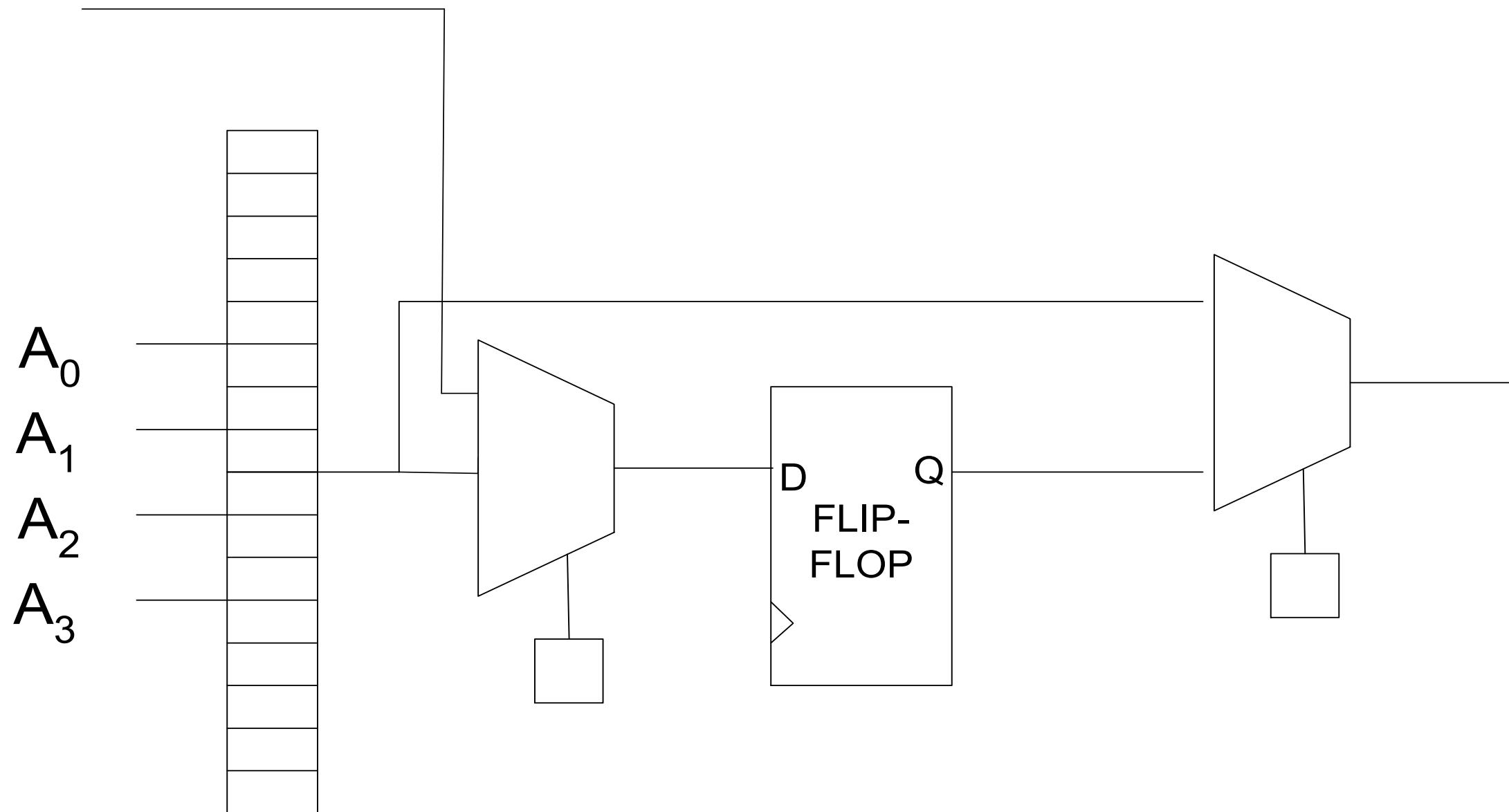

Sequential Logic Design

 


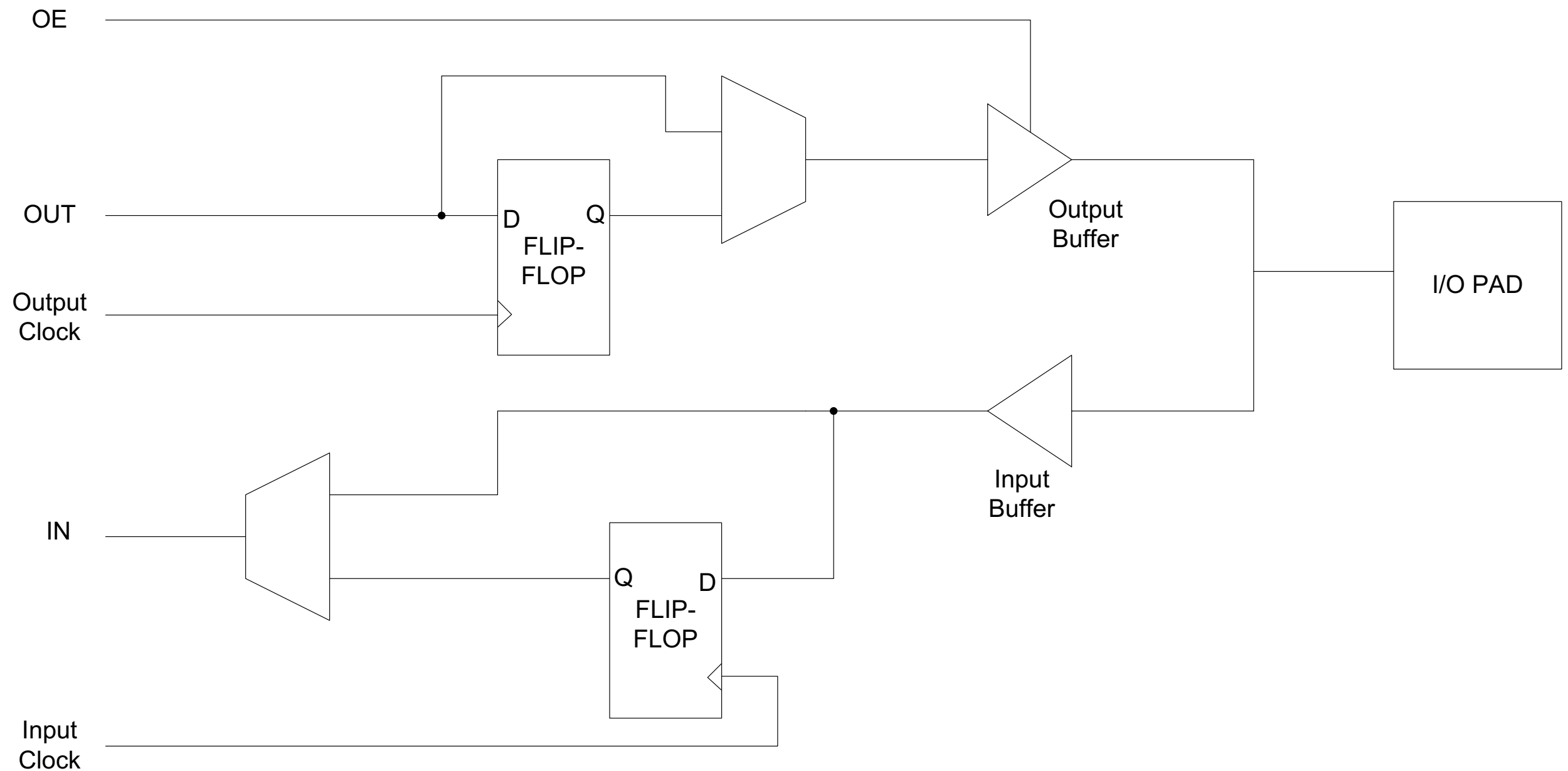I/O Block Xilinx 4000 Family -- Simplified




Programmable Interconnect Point (PIP)

 - ❖ The basic unit of programmable interconnect
 - ❖ 1 stands for connected
 - ❖ 0 stands for dis-connected




Programmable Interconnect Point (PIP)

 - ❖ The basic unit of programmable interconnect
 - ❖ 1 stands for connected
 - ❖ 0 stands for dis-connected




Xilinx FPGA Interconnect Example

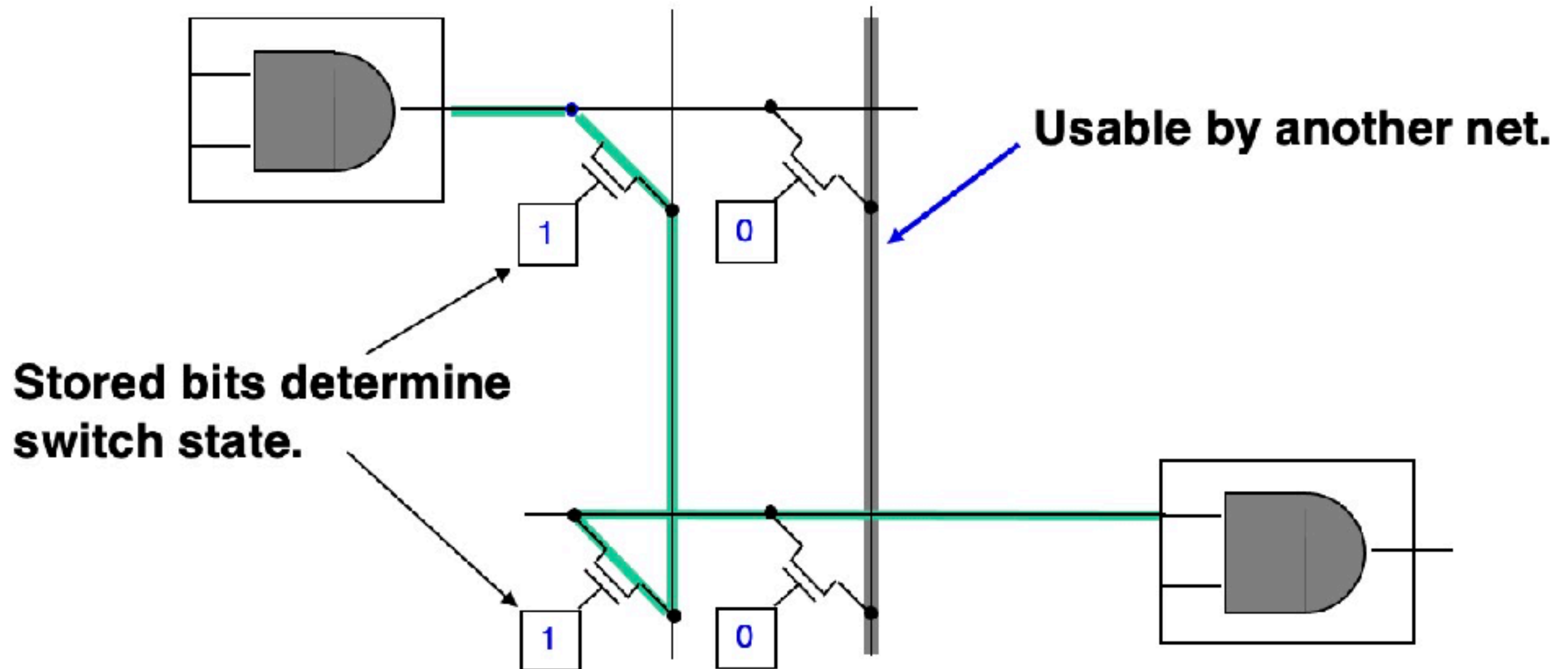
- ❖ Programmable Interconnect
 - ❖ Pass Transistors as switches



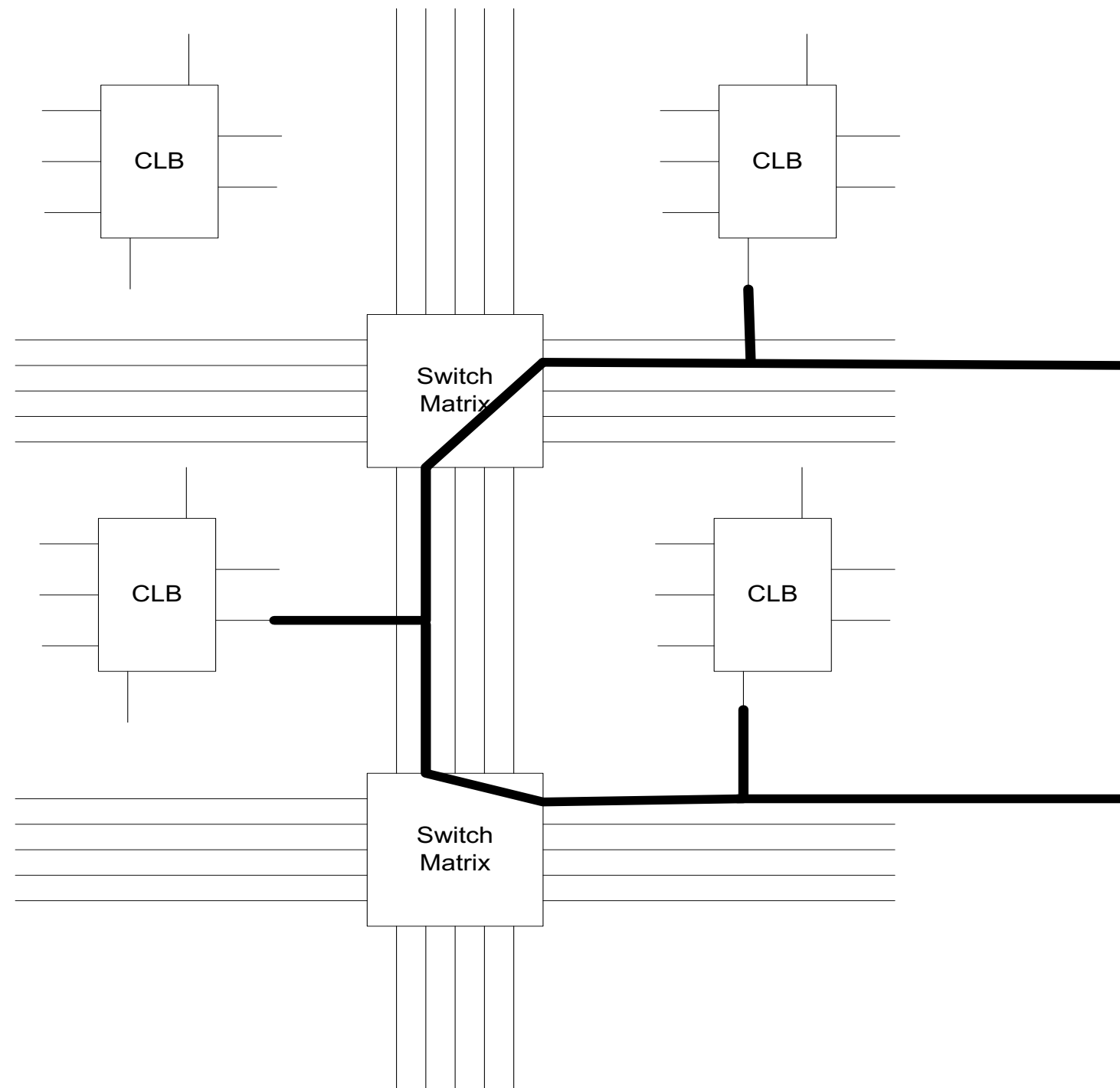Interconnect: Switch Matrixes and Programmable Interface Points



Xilinx 4000 Interconnect

 

Xilinx FPGA Design Flow

- ❖ Step1: Design

- ❖ Two design entry methods: HDL(Verilog or VHDL) or schematic drawings

- ❖ Step 2: Synthesize to create Netlist


- ❖ Translates V, VHD, SCH files into an industry standard EDIF file

- ❖ Step 3: Implement design (netlist)

- ❖ Translate, Map, Place & Route

- ❖ Step 4: Configure FPGA

- ❖ Download BIT file into FPGA

 


Important Step: Synthesis

- ❖ Enabled by sophisticated computer-aided design (CAD) tools
- ❖ A full set of programs and tools that allow automatic synthesis and compilation from a high level hardware description language, such as Verilog or VHDL to a string of bits, commonly termed a **bitstream**


FPGA Synthesis Flow

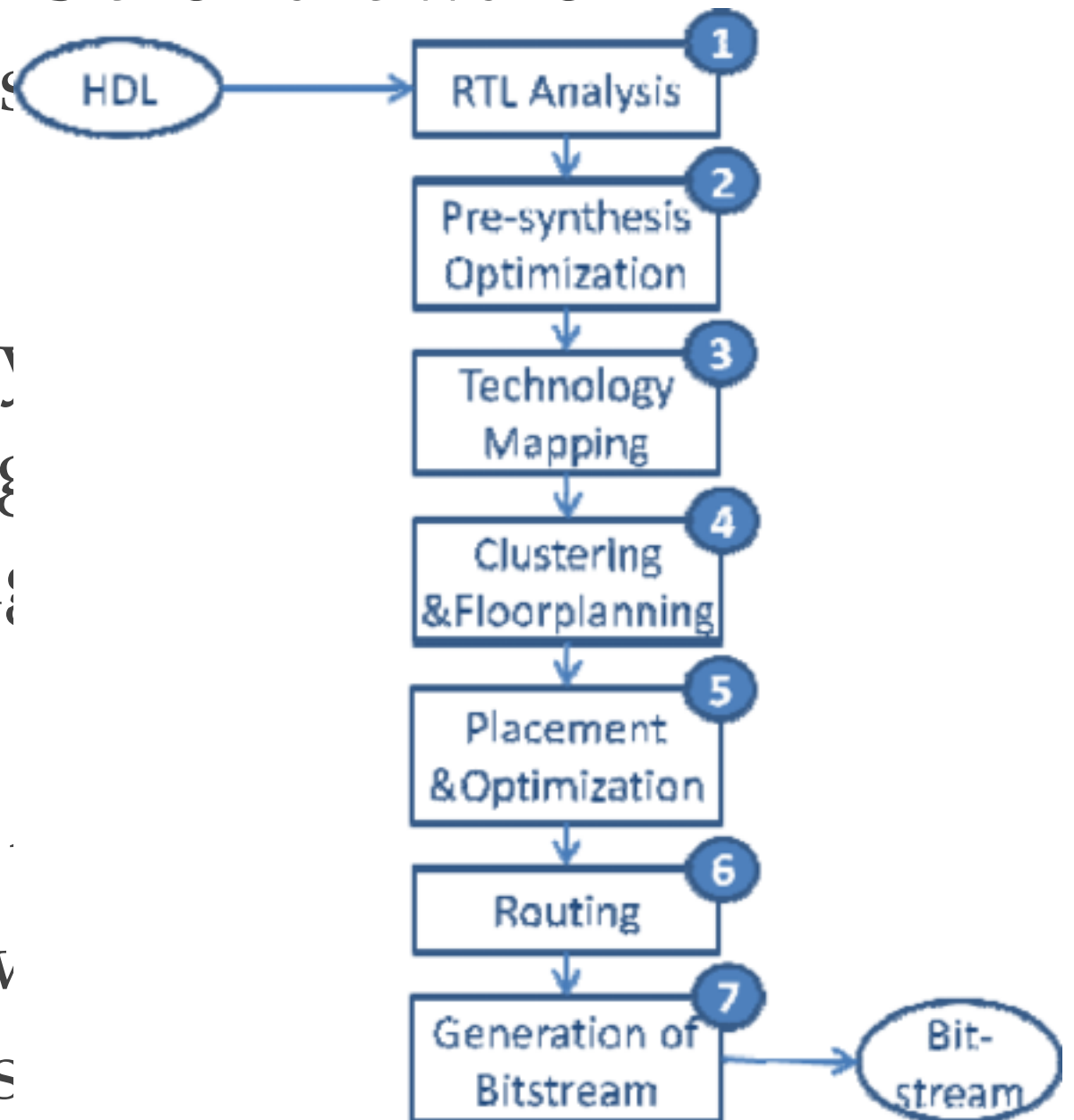- ❖ The input to the synthesis flow is the hardware specification, design constraints, and FPGA-specific commands
- ❖ The set of inputs is symbolically (hardware Description Language) contains the knowledge of design specifications
- ❖ The design constraints include the input and output pads, between registers, and between the registers



FPGA Design Example

- ❖ Lets reverse the function from LUT

 

FPGA Design Example

- ❖ A Boolean Function of four input variables A, B, C and D using a 4-input LUT.
- ❖ Here, let the output become high only when any of the two input variables are one.
- ❖ What is the hardware realization?

FPGA Design Example

- ❖ A Boolean Function of four inputs A, B, C and D using a 4-input LUT.
- ❖ Here, let the output become high if two input variables are one.
- ❖ What is the hardware realization of the

Truth Table

Inputs				Output
A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0


C and
of the

FPGA Implementation on a Slice


- ❖ Design the schematic yourself, using a 4-input LUT

FPGA Implementation on a Slice

 
- ❖ Design the schematic yourself, using a 4-input LUT




Practice

 

Practice

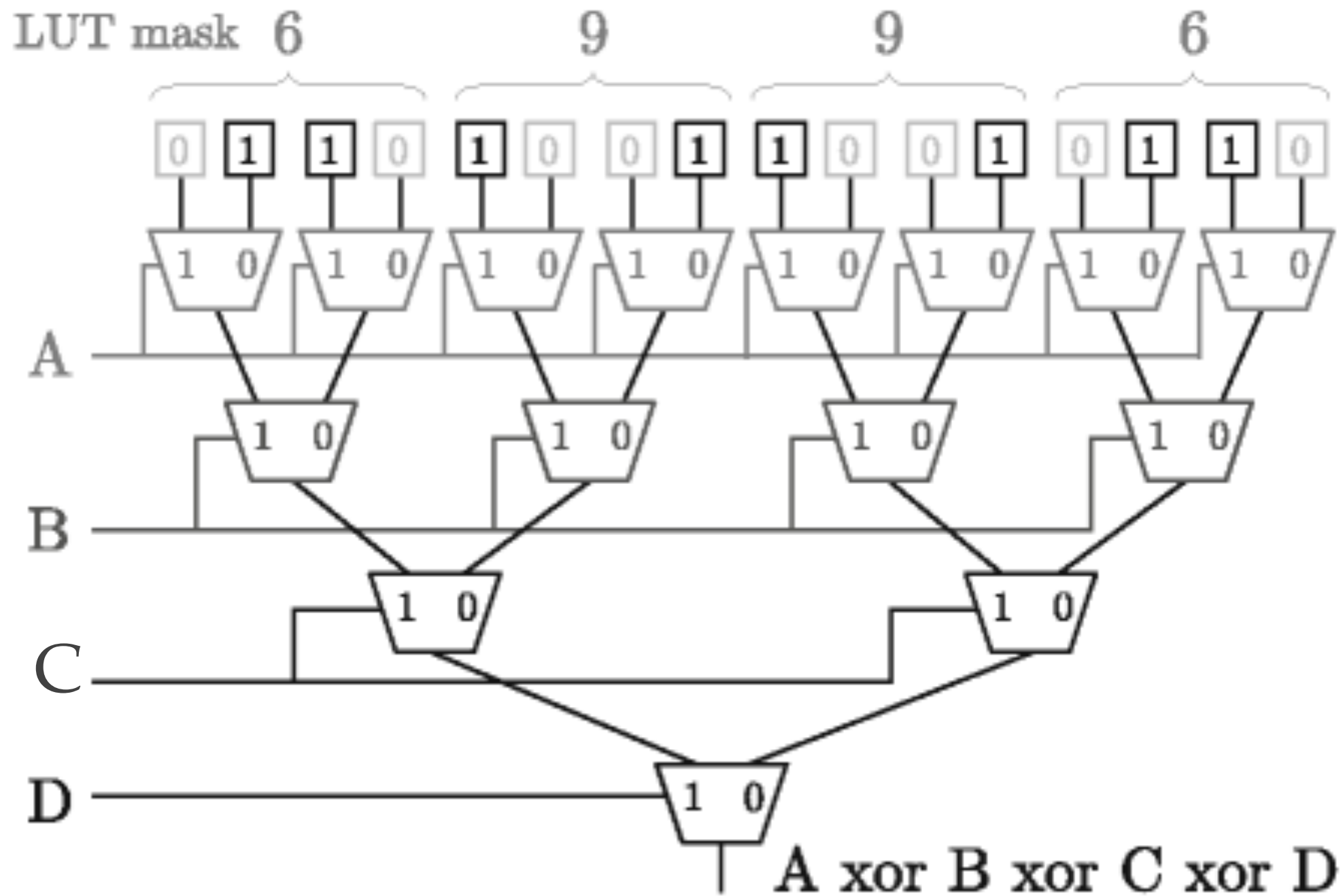

Practice

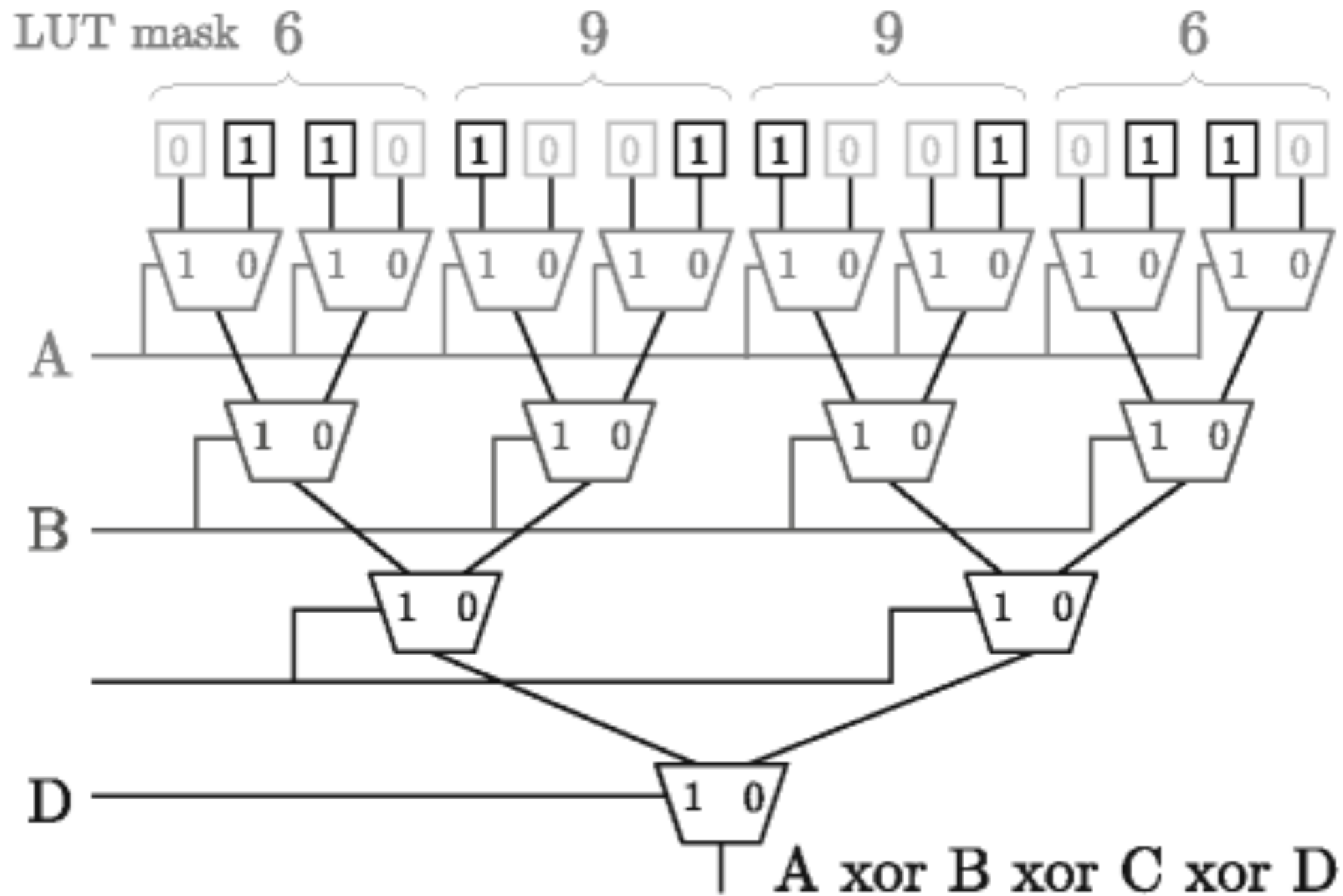


Direct Programming LUT

- ❖ LUT6 #(.INIT(64'h00000000000000000000) // Specify LUT Contents
- ❖ LUT6_inst (.O(O), // LUT general output
- ❖ .I0(I0), // LUT input
- ❖ .I1(I1), // LUT input
- ❖ .I2(I2), // LUT input
- ❖ .I3(I3), // LUT input
- ❖ .I4(I4), // LUT input
- ❖ .I5(I5) // LUT input); // End of LUT6_inst instantiation


FPGA Design Example

 - ❖ How should the LUT be programmed?
 - ❖ LUT6 #(.INIT(64'h0000_0000_0000_0001))
 - ❖ AND_6IN(.IO0(A),.I1(B),.I2(C),.I3(D),.I4(E),.I5(F),.O(Q));




Other Programmable Devices

 - ❖ The first programmable logic device (PLD) was programmable logic arrays (PLAs)
- ❖ Connection with fuse




Other Programmable Devices

- ❖ Compact representation of a 4×3 PLA with six product terms

 

HW2: Adder

❖ $1101 + 0110 = ?$

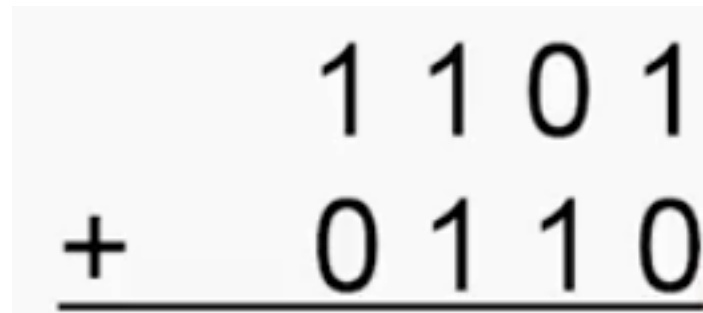
$$\begin{array}{r} 1101 \\ + 0110 \\ \hline \end{array}$$

Binary Adder

- ❖ $1101 + 0110 = ?$
- ❖ Calculation by hand...

$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 10011 \end{array}$$

Half Adder

❖ What is a half adder?

Half Adder

- ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added

Half Adder

- ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B

Half Adder

- ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B
 - ❖ Two outputs S(um) and C(arry out)

Half Adder

- ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B
 - ❖ Two outputs S(um) and C(arry out)
- ❖ No carry in

Half Adder

- ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B
 - ❖ Two outputs S(um) and C(arry out)
- ❖ No carry in
- ❖ $S = ?$

Half Adder

- ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B
 - ❖ Two outputs S(um) and C(arry out)
- ❖ No carry in
- ❖ $S = ?$
- ❖ $C = ?$

Half Adder

- ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B
 - ❖ Two outputs S(um) and C(arry out)
- ❖ No carry in
- ❖ $S = ?$
- ❖ $C = ?$

A	B
0	0
0	1
1	0
1	1

Half Adder

- ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B
 - ❖ Two outputs S(um) and C(arry out)
- ❖ No carry in
- ❖ $S = ?$
- ❖ $C = ?$
- ❖ Please write down your answer

A	B
0	0
0	1
1	0
1	1

Half Adder


- ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B
 - ❖ Two outputs S(um) and C(arry out)
- ❖ No carry in
- ❖ $S = ?$
- ❖ $C = ?$
- ❖ Please write down your answer

A	B
0	0
0	1
1	0
1	1

C	S
0	0
0	1
0	1
1	0

Half Adder

 - ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B
 - ❖ Two outputs S(sum) and C(carry out)
- ❖ No carry in
- ❖ $S = ?$
- ❖ $C = ?$
- ❖ Please write down your answer



A	B
0	0
0	1
1	0
1	1


C	S
0	0
0	1
0	1
1	0

Half Adder

- ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B
 - ❖ Two outputs S(um) and C(arry out)
- ❖ No carry in
- ❖ $S = A \text{ XOR } B$
- ❖ $C = A \text{ AND } B$


Half Adder

 - ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B
 - ❖ Two outputs S(um) and C(arry out)
- ❖ No carry in
- ❖ $S = A \text{ XOR } B$
- ❖ $C = A \text{ AND } B$




Half Adder

 - ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B
 - ❖ Two outputs S(um) and C(arry out)
- ❖ No carry in
- ❖ $S = A \text{ XOR } B$
- ❖ $C = A \text{ AND } B$




Half Adder

 - ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B
 - ❖ Two outputs S(um) and C(arry out)
- ❖ No carry in
- ❖ $S = A \text{ XOR } B$
- ❖ $C = A \text{ AND } B$



Half Adder

 - ❖ What is a half adder?
- ❖ Two 1-bit numbers are being added
 - ❖ Two inputs A and B
 - ❖ Two outputs S(um) and C(arry out)
- ❖ No carry in
- ❖ $S = A \text{ XOR } B$
- ❖ $C = A \text{ AND } B$



Full Adder

❖ What is a full adder?

Full Adder

- ❖ What is a full adder?
 - ❖ Has 3-bit input

Full Adder

- ❖ What is a full adder?
 - ❖ Has 3-bit input
 - ❖ Has a C_{in} (carry in) bit

Full Adder

- ❖ What is a full adder?
 - ❖ Has 3-bit input
 - ❖ Has a C_{in} (carry in) bit
 - ❖ Has two outputs: S_{um} and C_{out}

Full Adder

- ❖ What is a full adder?
 - ❖ Has 3-bit input
 - ❖ Has a C_{in} (carry in) bit
 - ❖ Has two outputs: $S(u)$ and C_{out}

Full Adder

- ❖ What is a full adder?
 - ❖ Has 3-bit input
 - ❖ Has a C_{in} (carry in) bit
 - ❖ Has two outputs: S(um) and C_{out}

A	B	C_{in}
0	0	0
0	1	0
1	0	0
1	1	0
0	0	1
0	1	1
1	0	1
1	1	1

Full Adder

- ❖ What is a full adder?
 - ❖ Has 3-bit input
 - ❖ Has a C_{in} (carry in) bit
 - ❖ Has two outputs: S(um) and C_{out}

A	B	C_{in}
0	0	0
0	1	0
1	0	0
1	1	0
0	0	1
0	1	1
1	0	1
1	1	1


- ❖ Write down the truth table for C_{out} and S

Full Adder

- ❖ What is a full adder?
 - ❖ Has 3-bit input
 - ❖ Has a C_{in} (carry in) bit
 - ❖ Has two outputs: S (um) and C_{out}
- ❖ Write down the truth table for (


A	B	C_{in}	C_{out}	S
0	0	0	0	0
0	1	0	0	1
1	0	0	0	1
1	1	0	1	0
0	0	1	0	1
0	1	1	1	0
1	0	1	1	0
1	1	1	1	1

Full Adder

 

Full Adder

 - ❖ Composition
 - ❖ Two half-adders: colored differently!



4-bit Full Adder

❖ $A=1101$

❖ $B=0110$

4-bit Full Adder

❖ A=1101

❖ B=0110

A hand-drawn binary addition problem. The first number, 1101, is written in orange. The second number, 0110, is written in blue with a plus sign to its left. A horizontal blue line separates the addends from the sum. The sum, 10011, is written in red below the line.

$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 10011 \end{array}$$

4-bit Full Adder

❖ A=1101

❖ B=0110

A hand-drawn binary addition problem. The first number, 1101, is written in orange. The second number, 0110, is written in blue with a plus sign to its left. A horizontal blue line separates the addends from the sum. The sum, 10011, is written in red below the line.

$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 10011 \end{array}$$

❖ How to build a 4-bit full adder?


4-bit Full Adder

❖ $A=1101$

❖ $B=0110$

$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 10011 \end{array}$$

❖ How to build a 4-bit full adder?

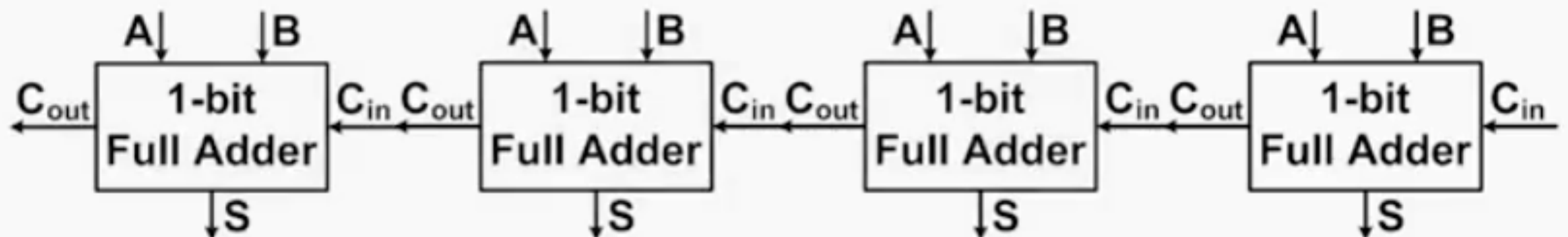

4-bit Full Adder

❖ How it works?

4-bit Full Adder

❖ How it works?


A 4-bit full adder calculation is shown. The first number, 1101, is in orange. The second number, 0110, is in blue. A blue plus sign is to the left of the second number. A horizontal blue line separates the two numbers from the result. The result, 10011, is in red. The result has five bits, indicating a carry-out from the 4-bit adder.

$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 10011 \end{array}$$

4-bit Full Adder

❖ How it works?

 
$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 10011 \end{array}$$



4-bit Full Adder

- ❖ How it works?
- ❖ Each bit assigned!

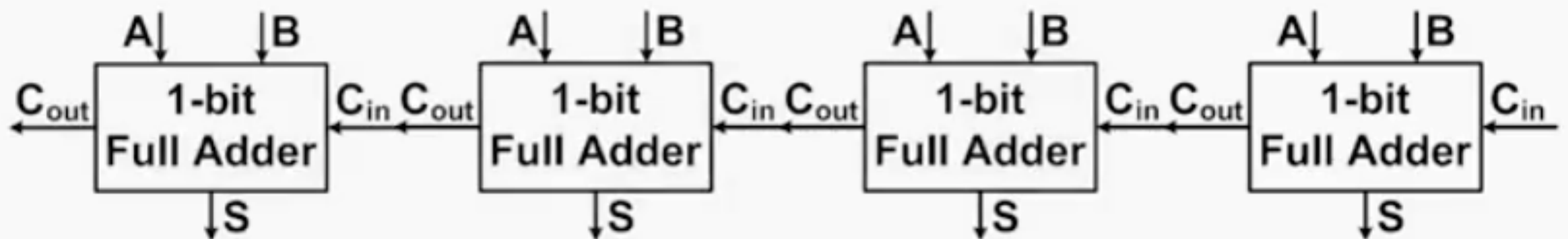
$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 10011 \end{array}$$



4-bit Full Adder

- ❖ How it works?
- ❖ Each bit assigned!

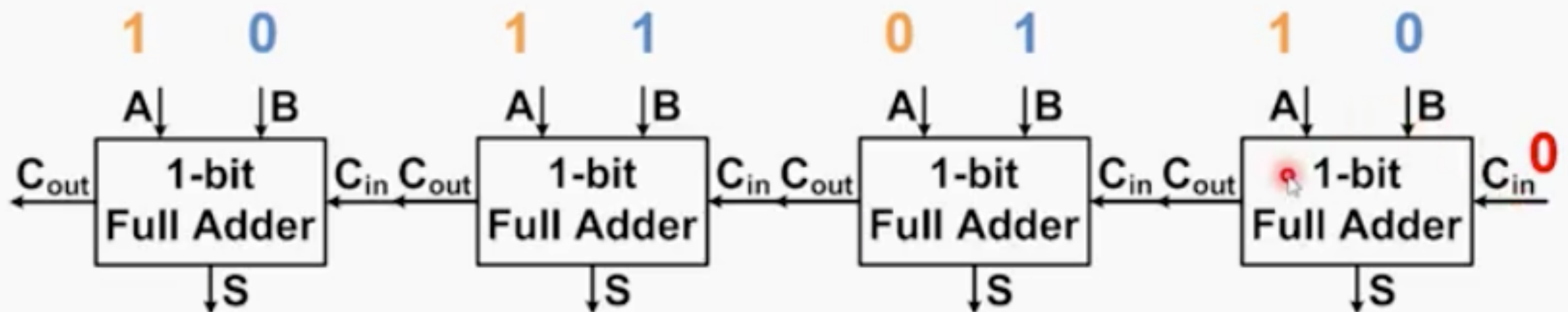
$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 10011 \end{array}$$



4-bit Full Adder

- ❖ How it works?
- ❖ Each bit assigned!

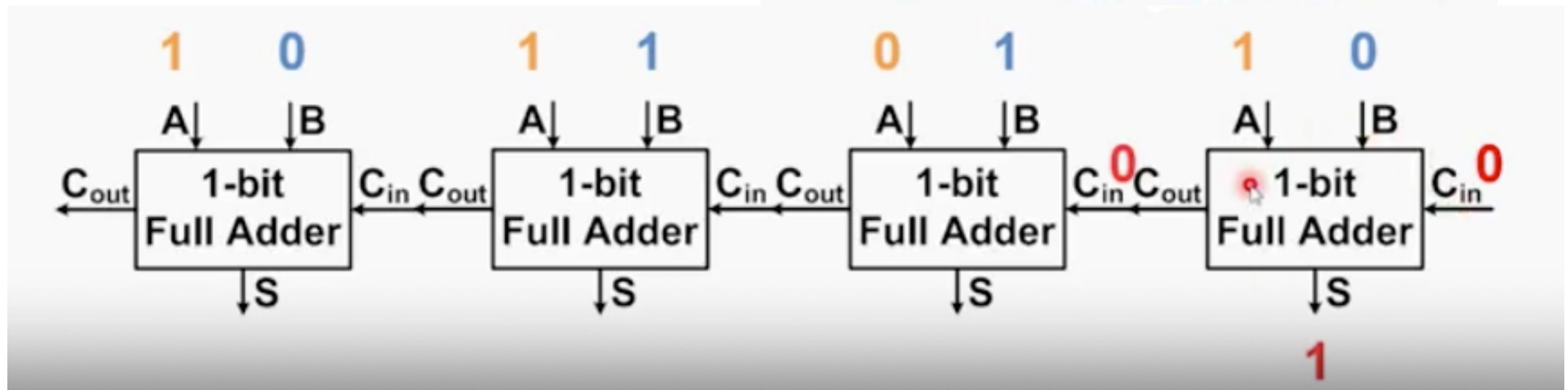
$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 10011 \end{array}$$



4-bit Full Adder

- ❖ How it works?
- ❖ Each bit assigned!

 
$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 10011 \end{array}$$



4-bit Full Adder

- ❖ How it works?
- ❖ Each bit assigned!

 
$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 10011 \end{array}$$



4-bit Full Adder

- ❖ How it works?
- ❖ Each bit assigned!
 
$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 10011 \end{array}$$



More bits Added

- ❖ 32-bit full adder

More bits Added

- ❖ 32-bit full adder
 - ❖ How to design?

More bits Added

- ❖ 32-bit full adder
 - ❖ How to design?

