


# EECE 2322: Fundamentals of Digital Design and Computer Organization

## Lecture 4\_1: Decoder, Encoder

Xiaolin Xu  
Department of ECE  
Northeastern University
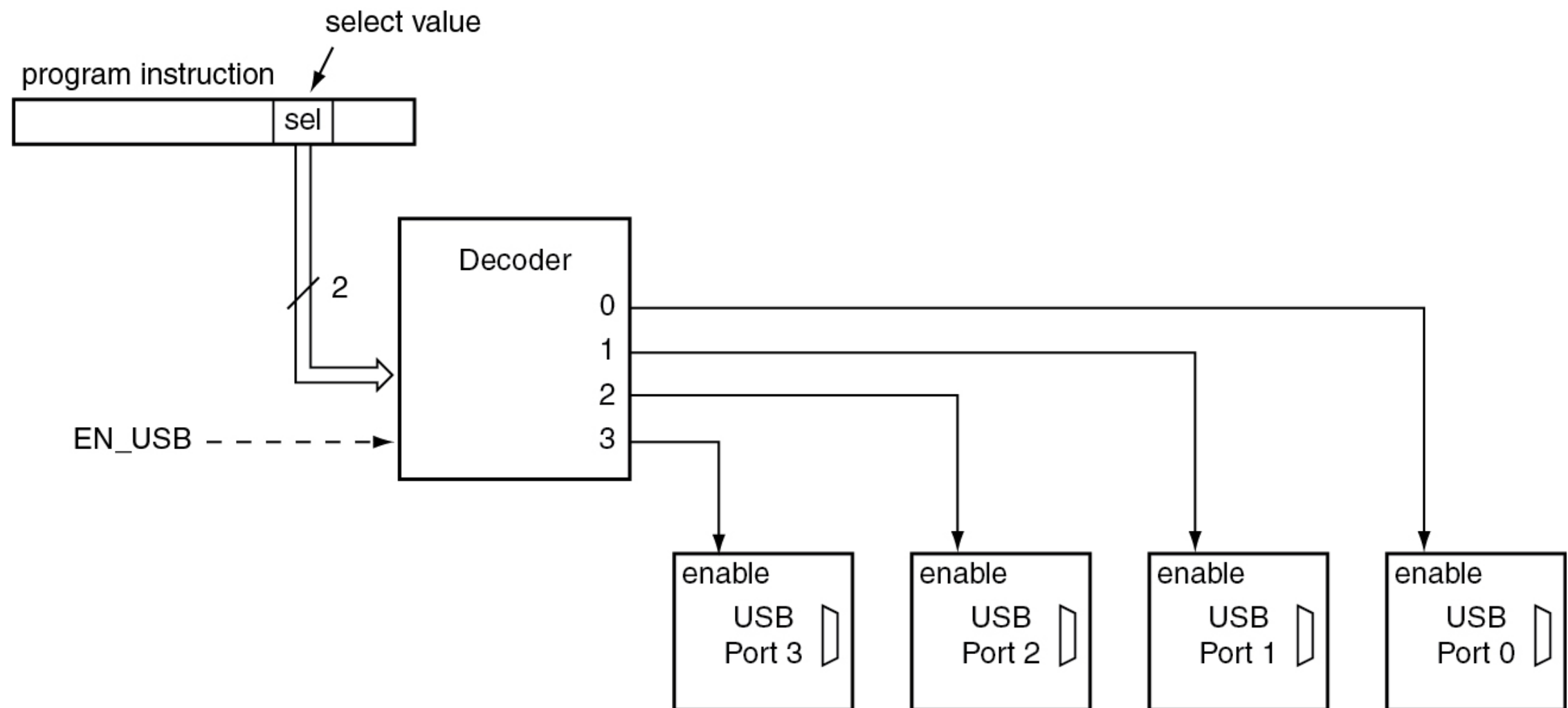
# Typical Decoder Application (1) in a Computer

- ❖ Many applications might require a combinational circuit to activate one or more other circuits, elements.




---
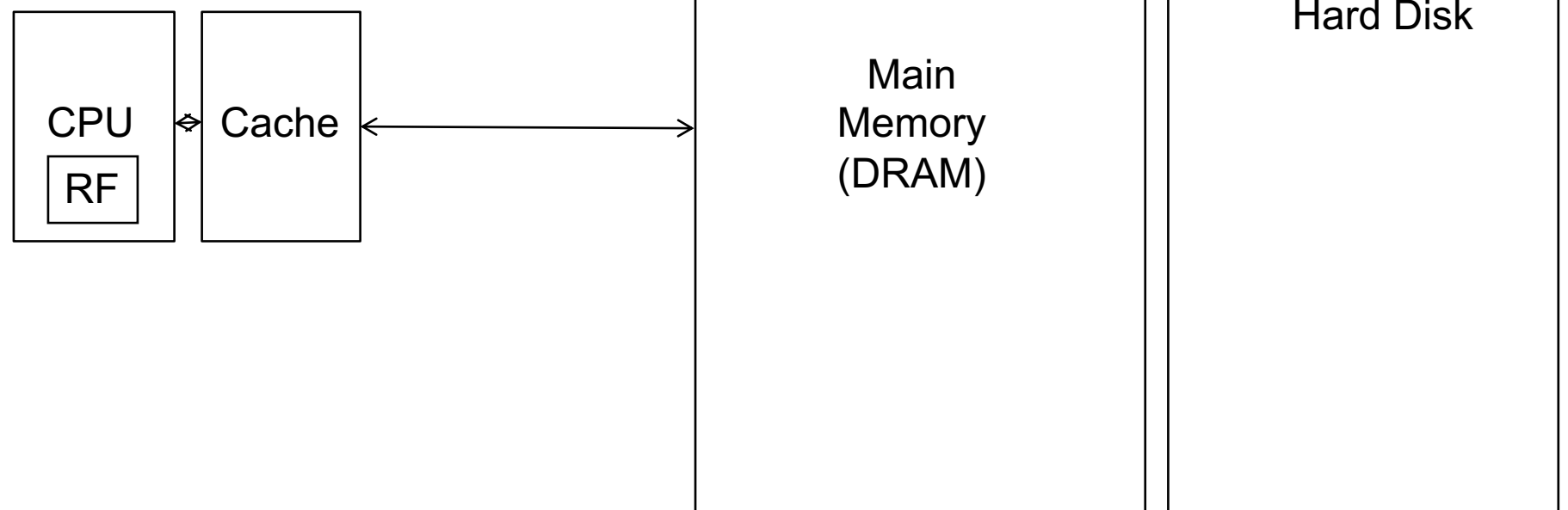
## Typical Decoder Application (2) in a Computer Memory Hierarchy


---

- ❖ Fundamental tradeoff
  - ❖ Fast memory: small
  - ❖ Large memory: slow
- ❖ Idea: Memory hierarchy
- ❖ Latency, cost, size,
- ❖ bandwidth


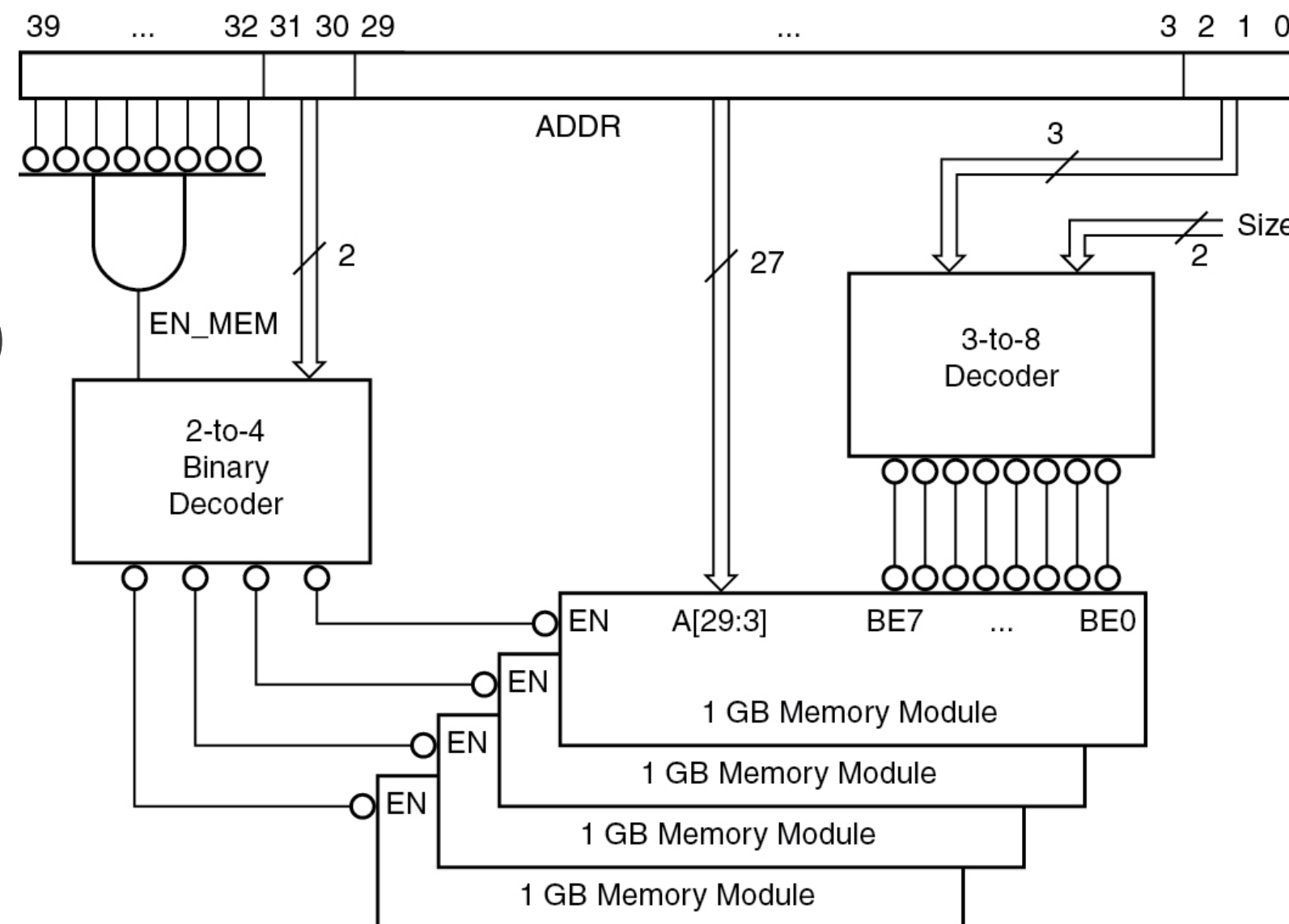
# Memory-Module Decoding in a Computer System

- ❖ 40-bit physical address
- ❖ 8 high-order bits=0
- ❖ 2-4 decoder
- ❖  $2^{27} \rightarrow$  longword(8B)
- ❖ 3-8  $\rightarrow$  1 Byte



---

# Encoder

---

- ❖  $2^n$  (or fewer) input lines and  $n$  output lines.
- ❖ The output lines generate the binary code corresponding to the input value, assuming only one input is high
- ❖ An encoder is the reverse function of a decoder

# Encoder Example

**TABLE 3-5**  
**Truth Table for Octal-to-Binary Encoder**

Inputs								Outputs		
$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

---

# 4-to-2 Binary Encoder in Verilog

---

```
module encoder (Y, W);  
    input [3:0] W;  
    output [1:0] Y;  
    reg [1:0] Y;  
  
    always@ (W)  
        case (W)  
            4'b1000: Y = 2'b11;  
            4'b0100: Y = 2'b10;  
            4'b0010: Y = 2'b01;  
            4'b0001: Y = 2'b00;  
            default: Y = 2'bxx; //don't care case  
        endcase  
    endmodule
```

---

# Encoder Output Ambiguity

---

- ❖ If two inputs are active simultaneously, the output produces an incorrect combination
- ❖ To resolve, some encoders use an input priority to ensure that only one input is encoded.



---

# Priority Encoder

---


- ❖ If two or more inputs are equal to 1 at the same time, the input with highest priority takes precedence.
- ❖ Truth Table of 4-Input Priority Encoder
- ❖

# Priority Encoder

- ❖ If two or more inputs are equal to 1 at the same time, the input with highest priority takes precedence.
- ❖ Truth Table of 4-Input Priority Encoder

Inputs				Outputs		
$D_3$	$D_2$	$D_1$	$D_0$	$A_1$	$A_0$	$V$
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1
 
# Priority Encoder: Circuit Implementation



# 4-to-2 Priority Encoder in Verilog

```
module priority (Y, V, W);  
    input [3:0] W;  
    output [1:0] Y;  
    output V;  
    reg [1:0] Y;  
    reg V;  
    always@ (W) begin  
        V = 1; // assume valid output  
        casex (W)  
            4'b1xxx: Y = 2'b11;  
            4'b01xx: Y = 2'b10;  
            4'b001x: Y = 2'b01;  
            4'b0001: Y = 2'b00;  
            default: begin  
                V = 0;  
                Y = 2'bxx; //don't care case  
            end  
        endcase  
    end  
endmodule
```

---

# case in Verilog


---

- ❖ Checks if the given expression matches one of the other expressions in the list and branches accordingly
- ❖ **Mostly used in building MUXes (see why later)**

```
case (<expression>)
  case_item1 : <single statement>
  case_item2,
  case_item3 : <single statement>
  case_item4 : begin
                  <multiple statements>
                end
  default    : <statement>
endcase
```


# Circuit of a MUX

- ❖ 4-1 MUX has a decoder inside

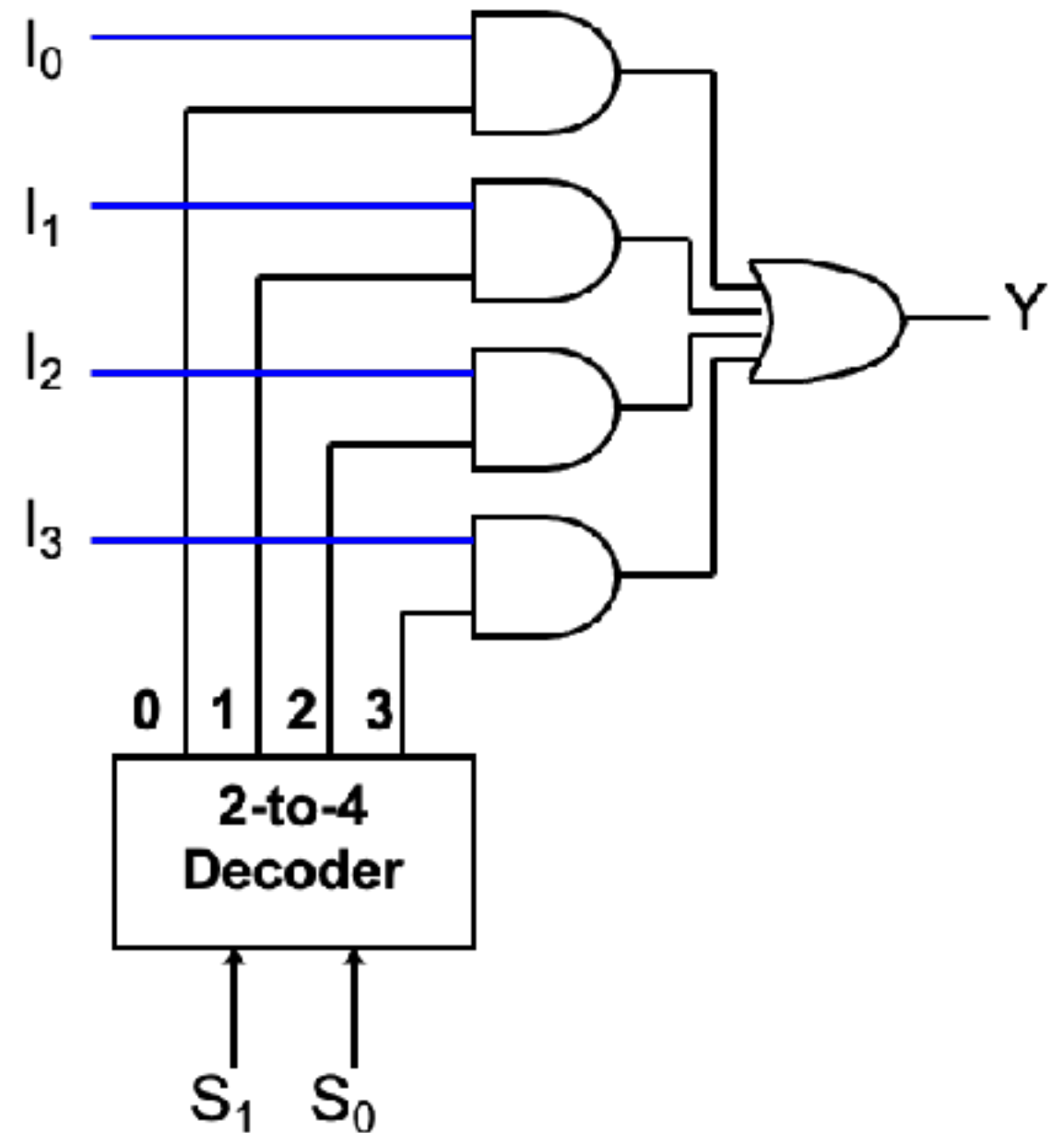

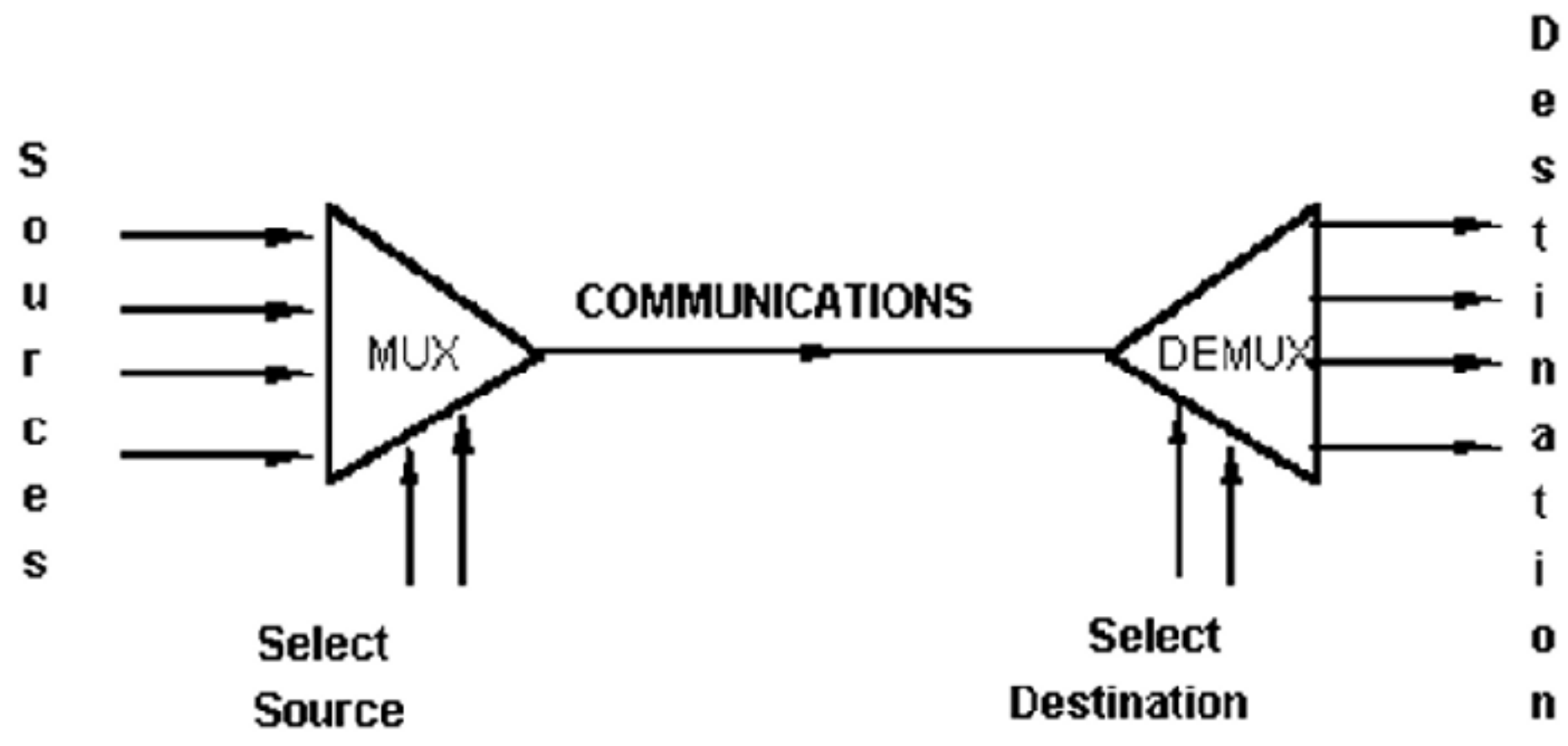
# Real-world Applications of MUX

- ❖ Sharing a single communication line among a number of devices. *At any time, only one source and one destination can use the communication line*


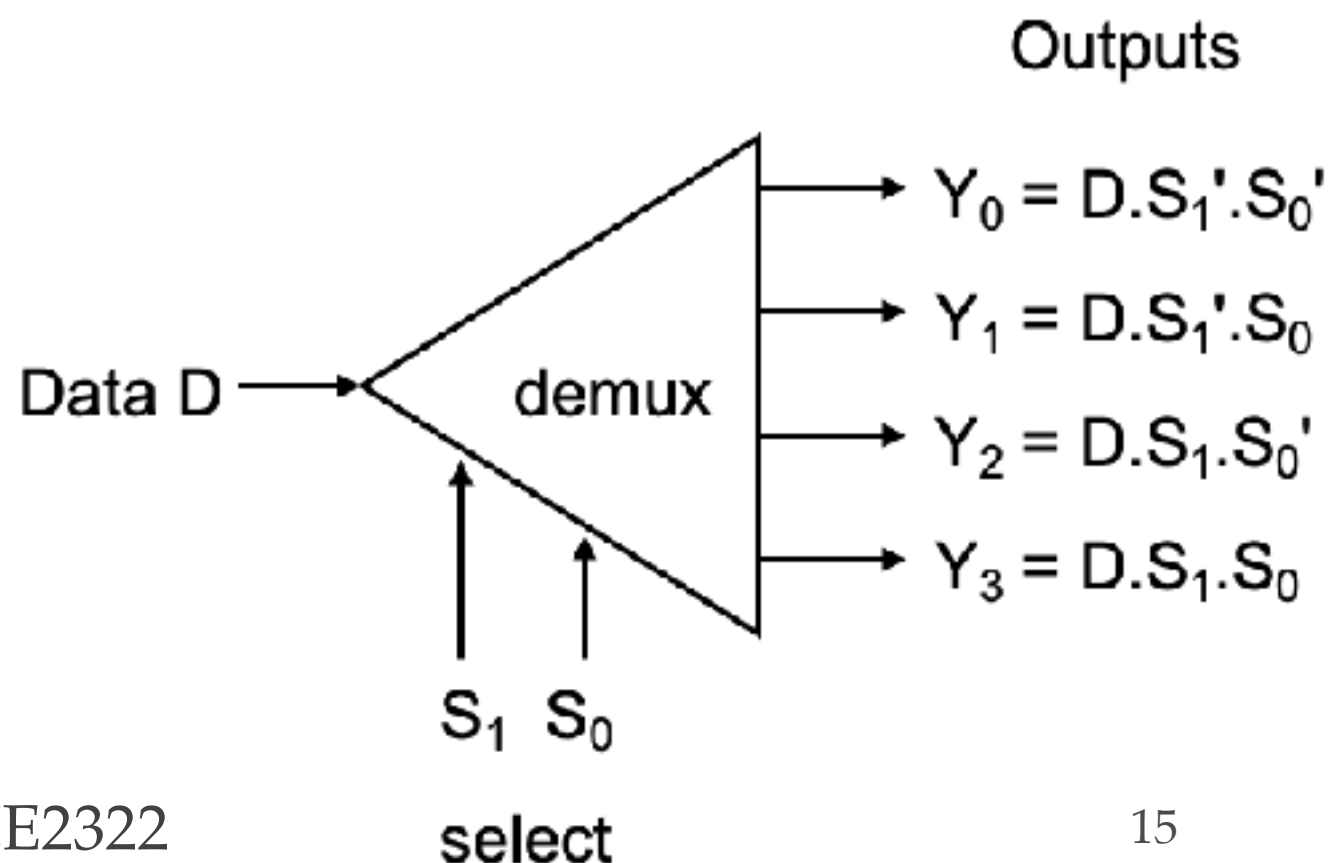
# Demultiplexer

- ❖ Given an input line & a set of selection lines, the demultiplexer will direct data from input to a selected output line.
- ❖ An example of a 1-to-4 demultiplexer:




$S_1$	$S_0$	$Y_0$	$Y_1$	$Y_2$	$Y_3$
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D


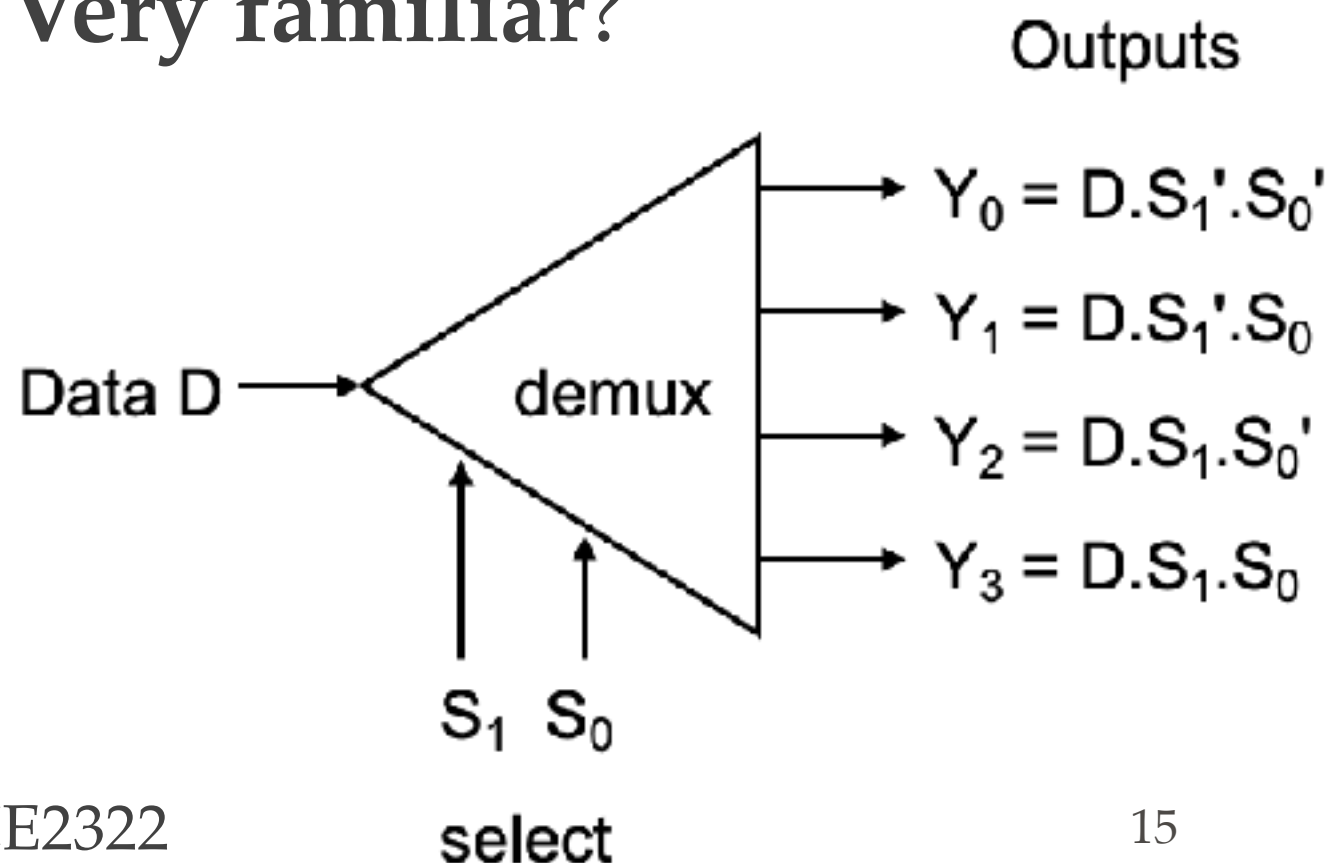
# Demultiplexer


- ❖ Given an input line & a set of selection lines, the demultiplexer will direct data from input to a selected output line.
- ❖ An example of a 1-to-4 demultiplexer:
- ❖ **Very familiar?**



$S_1$	$S_0$	$Y_0$	$Y_1$	$Y_2$	$Y_3$
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D
 
# DeMUX

- ❖ The demultiplexer is actually identical to a decoder with enable:




$S_1$	$S_0$	$Y_0$	$Y_1$	$Y_2$	$Y_3$
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

# DeMUX


- ❖ The demultiplexer is actually identical to a decoder with enable:

❖

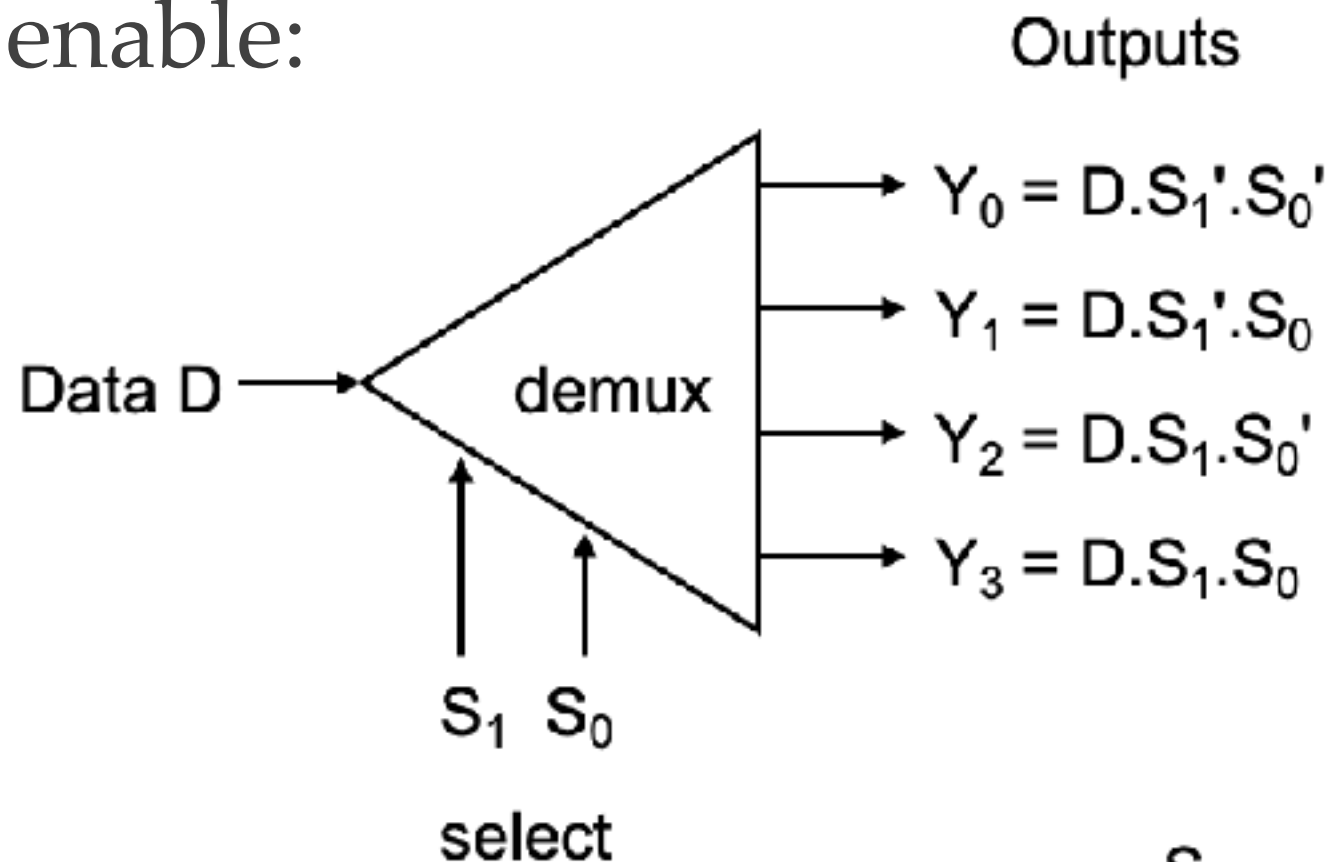


Outputs

$S_1$	$S_0$	$Y_0$	$Y_1$	$Y_2$	$Y_3$
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

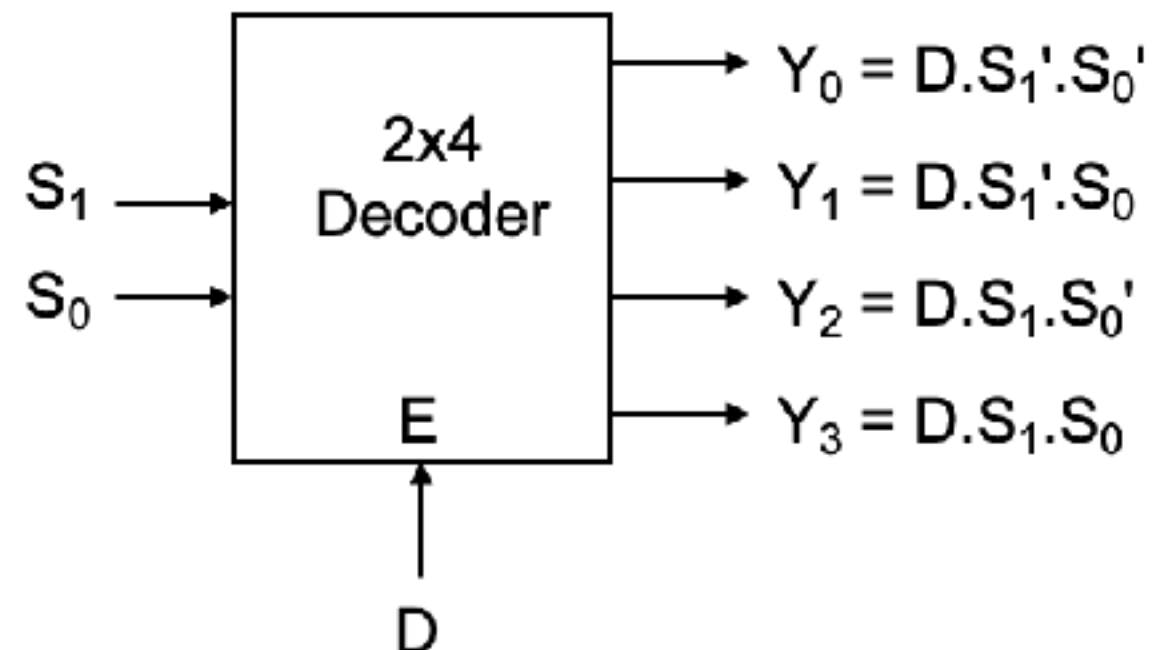
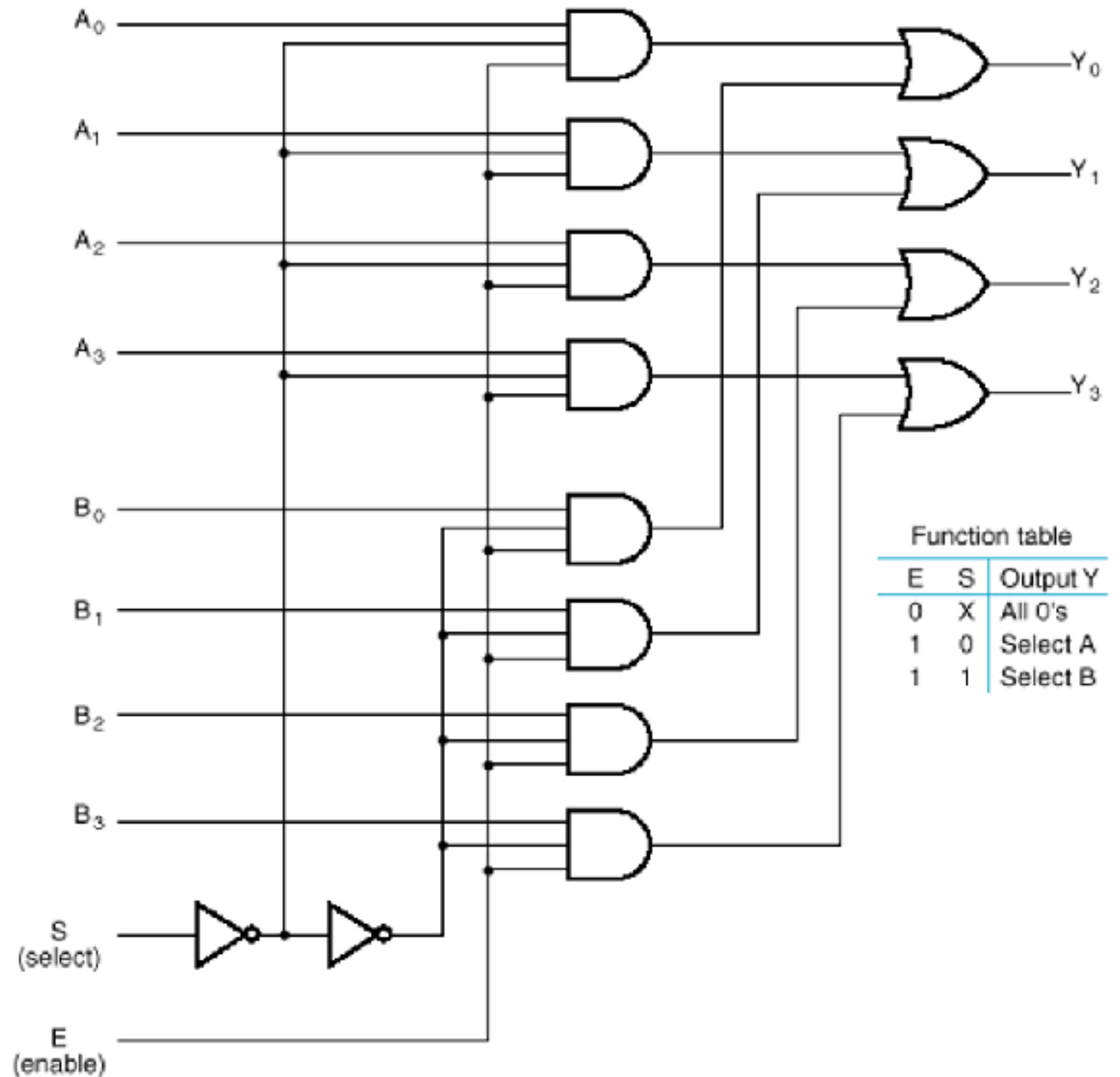
# Quadruple 2-to-1-Line Multiplexer

- ❖ Notice enable bit
- ❖ Notice select bit
- ❖ 4 bit inputs
- ❖ **Data type X**



---

# Verilog Data Types

---

0	represents a logic zero, or a false condition
1	represents a logic one, or a true condition
x	represents an unknown logic value (can be zero or one)
z	represents a high-impedance state

# Verilog Data Types


0	represents a logic zero, or a false condition
1	represents a logic one, or a true condition
x	represents an unknown logic value (can be zero or one)
z	represents a high-impedance state



0



1

 

x



z

---

# Verilog Data Types

---

- ❖ X means that the value is simply unknown at the time, and could be either 0 or 1
- ❖ *Different from the way X is treated in boolean logic, where it means "don't care"*

# Verilog Data Types


- ❖ X means that the value is simply unknown at the time, and could be either 0 or 1
- ❖ *Different from the way X is treated in boolean logic, where it means "don't care"*



0



1

 

X



Z



---

# Verilog Data Types

---

- ❖ In any incomplete electric circuit, the wire not connected to anything will have a high-impedance at that node and is represented by Z or z.
- ❖ *Even in verilog, any unconnected wire will result in a high impedance.*

# Verilog Data Types


- ❖ In any incomplete electric circuit, the wire not connected to anything will have a high-impedance at that node and is represented by Z or z.
- ❖ *Even in verilog, any unconnected wire will result in a high impedance.*



0



1

 

X




Z

# These Data Types in Practical Circuits

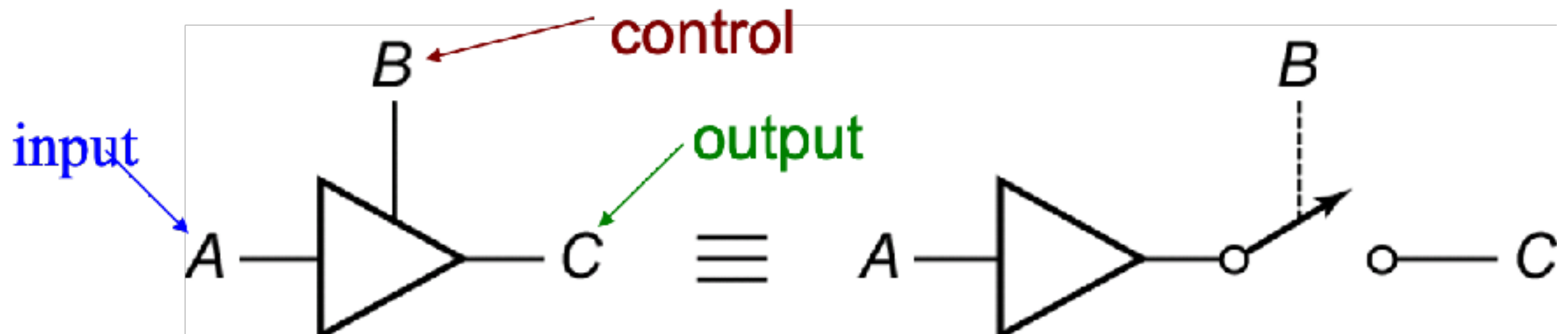
## ❖ Tristate Buffer

- ❖ A tristate buffer can output 3 different values:
- ❖ Logic 1 (high)
- ❖ Logic 0 (low)
- ❖ High-Impedance (Z)



# Tristate Buffer

Enable

 

B	A	C
0	0	$\bar{Z}$
0	1	$\bar{Z}$
1	0	0
1	1	1

B	A	C
0	0	$\bar{Z}$
0	1	$\bar{Z}$
1	0	1
1	1	0

B	A	C
0	0	0
0	1	1
1	0	$\bar{Z}$
1	1	$\bar{Z}$

B	A	C
0	0	1
0	1	0
1	0	$\bar{Z}$
1	1	$\bar{Z}$


---

# Application Scenario (1) of Tristate Buffers: 2-1 MUX

---
 
## ❖ 2x1 MUX Using Tristate Buffers

- ❖ Used in place of a MUX – this is the one case where the output lines can just be “tied together”
- ❖ The control line  $s$  selects which buffer will pass its input




# Application Scenario (2) of Tristate Buffers: Tristate Buses

❖ Floating nodes are used in tristate

❖ Many different drivers

❖ Exactly one is active at once

 

# EECE 2322: Fundamentals of Digital Design and Computer Organization

## Lecture 4\_1: Sequential and Combinational Circuits

Xiaolin Xu  
Department of ECE  
Northeastern University

---

# Difference Between Combinational and Sequential Circuits

---

- ❖ Combinational Circuit

- ❖ Time independent circuits
- ❖ Do not depend on previous inputs to generate any output



Figure: Combinational Circuits



# Difference Between Combinational and Sequential Circuits

## ❖ Sequential Circuit

- ❖ Dependent on
  - ❖ Clock cycles
  - ❖ Present inputs
  - ❖ Past inputs
- ❖ to generate any

 


Figure: Sequential Circuit

---

# Combinational and Sequential Circuits

---

## ❖ Summary

### ❖ Combinational Circuits

- ❖ Output depends on current values of inputs only
- ❖ No feedback
- ❖ No memory

### ❖ Sequential Hardware

- ❖ Feedback
- ❖ Output depends on current inputs and current state
- ❖ Circuit has memory elements
- ❖ Sequential Hardware = Combinational Hardware + memory elements  
( latches, flipflops, memories) ...

# Level-Sensitive and Edge-Sensitive


- ❖ Left: will block until there is a change in the value of a or b
- ❖ Right: will block until clk transitions from 0 to 1.

```
always    @ (a or b or sel)
begin
    y = 0;
    if (sel == 0) begin
        y = a;
    end else begin
        y = b;
    end
end
```

```
always    @ (posedge clk )
if (reset == 0) begin
    y <= 0;
end else if (sel == 0) begin
    y <= a;
end else begin
    y <= b;
end
```


 
# Sequential Logic (1): Memory

- ❖ Fundamental building block of memory
  - ❖ Bi-stable element
  - ❖ Two stable and complementary states



  
# Sequential Logic (1): Memory

- ❖ Fundamental building block of memory
  - ❖ Bi-stable element
  - ❖ Two stable and complementary states



 
# Static Random Access Memory

- ❖ Two possible states: “0” ( $AB=01$ ) or “1” ( $AB=10$ )




# Static-RAM Array

 
 
# Memory Bank Organization and Operation

- ❖ Read access sequence:
  - ❖ 1. Decode row address & drive
  - ❖ 2. Selected bits drive bit-lines
    - ❖ Entire row read
  - ❖ 3. Amplify row data
  - ❖ 4. Decode column address & send
    - ❖ Send to output
  - ❖ 5. Precharge bit-lines
    - ❖ For next access





# SRAM (Static Random Access Memory)

## ❖ Read Sequence

- ❖ 1. address decode
- ❖ 2. drive row select
- ❖ 3. selected bit-cells drive bitlines, (entire row)
- ❖ 4. differential sensing and column select (data is ready)
- ❖ 5. precharge all bitlines
- ❖ Access latency dominated by steps 2 and 3
- ❖ Cycling time dominated by steps 2, 3 and 5
  - ❖ step 2 proportional to  $2^m$
  - ❖ step 3 and 5 proportional to  $2^n$

