

# EECE 2322: Fundamentals of Digital Design and Computer Organization

## Lecture 10\_2: Finite State Machine

Xiaolin Xu  
Department of ECE  
Northeastern University

---

# State of Digital System

---

- ❖ Outputs of sequential logic depend on current *and* prior input values – it has **memory**.
- ❖ Some definitions:
  - ❖ **State:** all the information about a circuit necessary to explain its future behavior
  - ❖ **Latches and flip-flops:** state elements that store one bit of state
  - ❖ **Synchronous sequential circuits:** combinational logic followed by a bank of flip-flops

---

# State Machine Concept

---

❖ Your understanding?

---

# State Machine Concept

---

- ❖ From Wiki:
- ❖ A finite-state machine (FSM) is a mathematical model of computation.
- ❖ It is an **abstract** machine that can be in exactly one of a finite number of states at any given time.

---

# State Machine Concept

---

- ❖ From Wiki:
- ❖ The FSM can change from one state to another in response to some external inputs; the change from one state to another is called a transition.
- ❖ An FSM is defined by a list of its states, its initial state, and the conditions for each transition.

---


# Example1: Controller

---


- ❖ Data components are put together in the data part of an RT level design, and the controller is wired to the data part to control its flow of data.
- ❖ Controllers can be
  - ❖ as easy as one flip-flop, handshaking handlers,
  - ❖ or as complex as several concurrent state machines
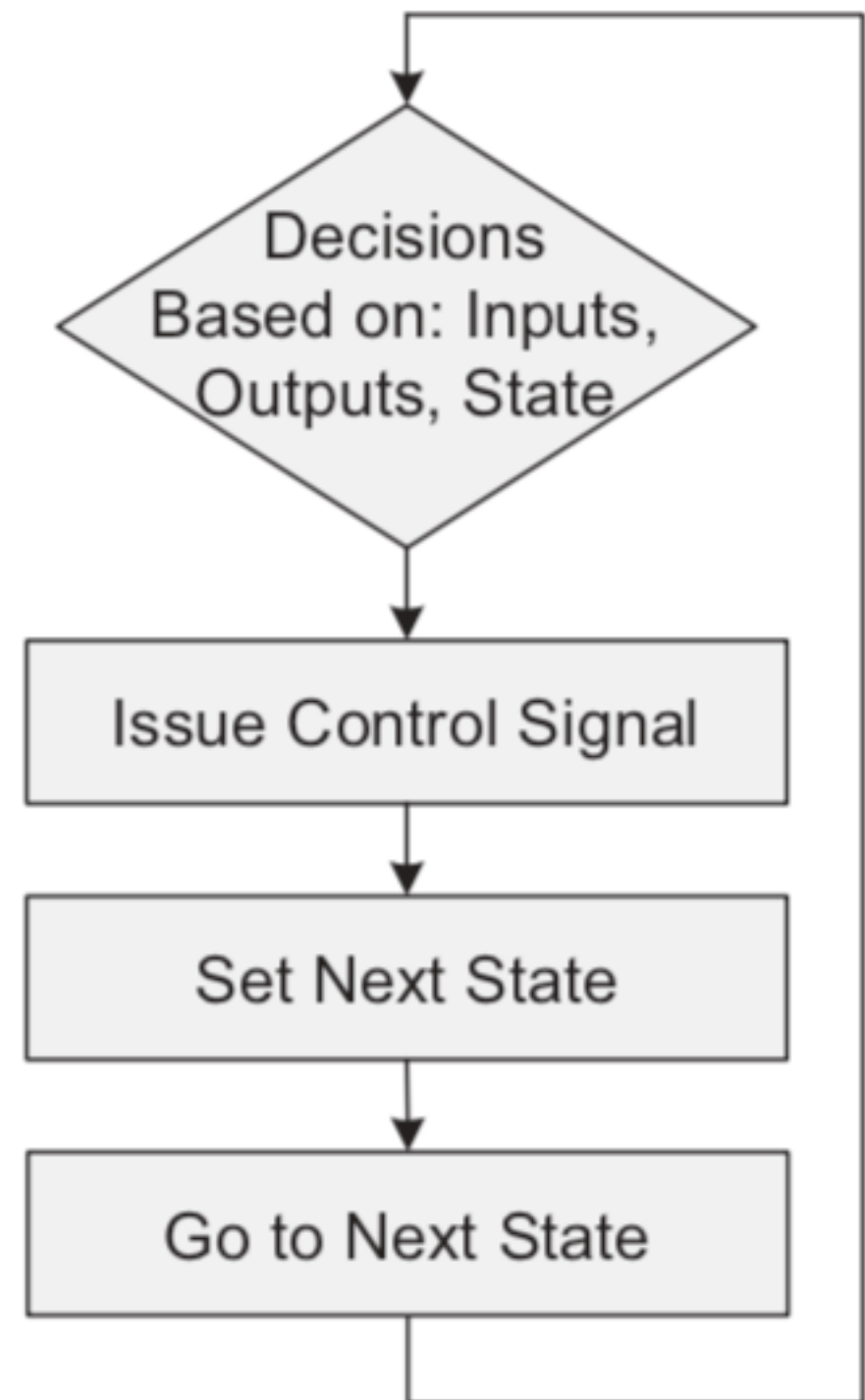
# Example1: Controller

- ❖ A controller circuit. The inputs to the controller determine its next states and its outputs.
- ❖ The controller monitors its inputs and makes decisions as to when and what output signals to assert.
- ❖ Controllers keep past history of circuit data by switching to appropriate states.




# Example1: Controller

 




# Example1: Controller

 

# Example1: Controller

 




# Example1: Controller


Jump button

Reach apex of jump

 
 
# Example1: Controller

- Traffic light controller
  - Traffic sensors:  $T_A$ ,  $T_B$  (TRUE when there's traffic)
  - Lights:  $L_A$ ,  $L_B$



---


# Example2: Sequence Detector

---

- ❖ A sequence detector is a **good representation for the general class of controllers.**
- ❖ Sequence detectors are **simplified controllers**
- ❖ Instead of many inputs / outputs, sequence detectors have **one or two input and output lines, and instead of complex decision makings**
 
# Example2: Sequence Detector


- ❖ A finite state machine-based sequence detector
  - ❖ Searches on input for the 110 sequence
  - ❖ When this sequence is detected in three consecutive clock pulses, the output ( $w$ ) becomes 1 and stays 1 for a complete clock cycle.





 
# Example2: Sequence Detector

- ❖ A sequence detector
  - ❖ Searches on input for the 110 sequence
  - ❖ When this sequence is detected in three consecutive clock pulses, the output (w) becomes 1 and stays 1 for a complete clock cycle.



# State Machine

- ❖ States: s0, s1, s2, and s3

 



---

# We Already Learned FSM

---

# State Machine

- ❖ States: s0, s1, s2, and s3
- ❖ s0 is the reset state and s3 is the state in which the 110 sequence is detected

```
`timescale 1ns/100ps

module Detector110 (input a, clk, reset, output w);
    parameter [1:0] s0=2'b00, s1=2'b01, s2=2'b10, s3=2'b11;
    reg [1:0] current;

    always @ (posedge clk) begin
        if (reset) current = s0;
        else
            case (current)
                s0: if (a) current <= s1; else current <= s0;
                s1: if (a) current <= s2; else current <= s0;
                s2: if (a) current <= s2; else current <= s3;
                s3: if (a) current <= s1; else current <= s0;
            endcase
        end

        assign w = (current == s3) ? 1: 0;

    endmodule
```

---


# Syntax of a Verilog Case Statement

---

- ❖ The case statement compares an expression to a series of cases and executes the statement or statement group associated with the first matching case:
  - ❖ case statement supports single or multiple statements.
  - ❖ Group multiple statements using begin and end keywords.
- ❖ Syntax of a case statement look as shown below.
- ❖ case ()
- ❖ < case1 > : < statement >
- ❖ < case2 > : < statement >
- ❖ .....
- ❖ default : < statement >
- ❖ endcase



# Applications of Case Statement

## ❖ State transition

 

# Applications of Case Statement

## ❖ State transition

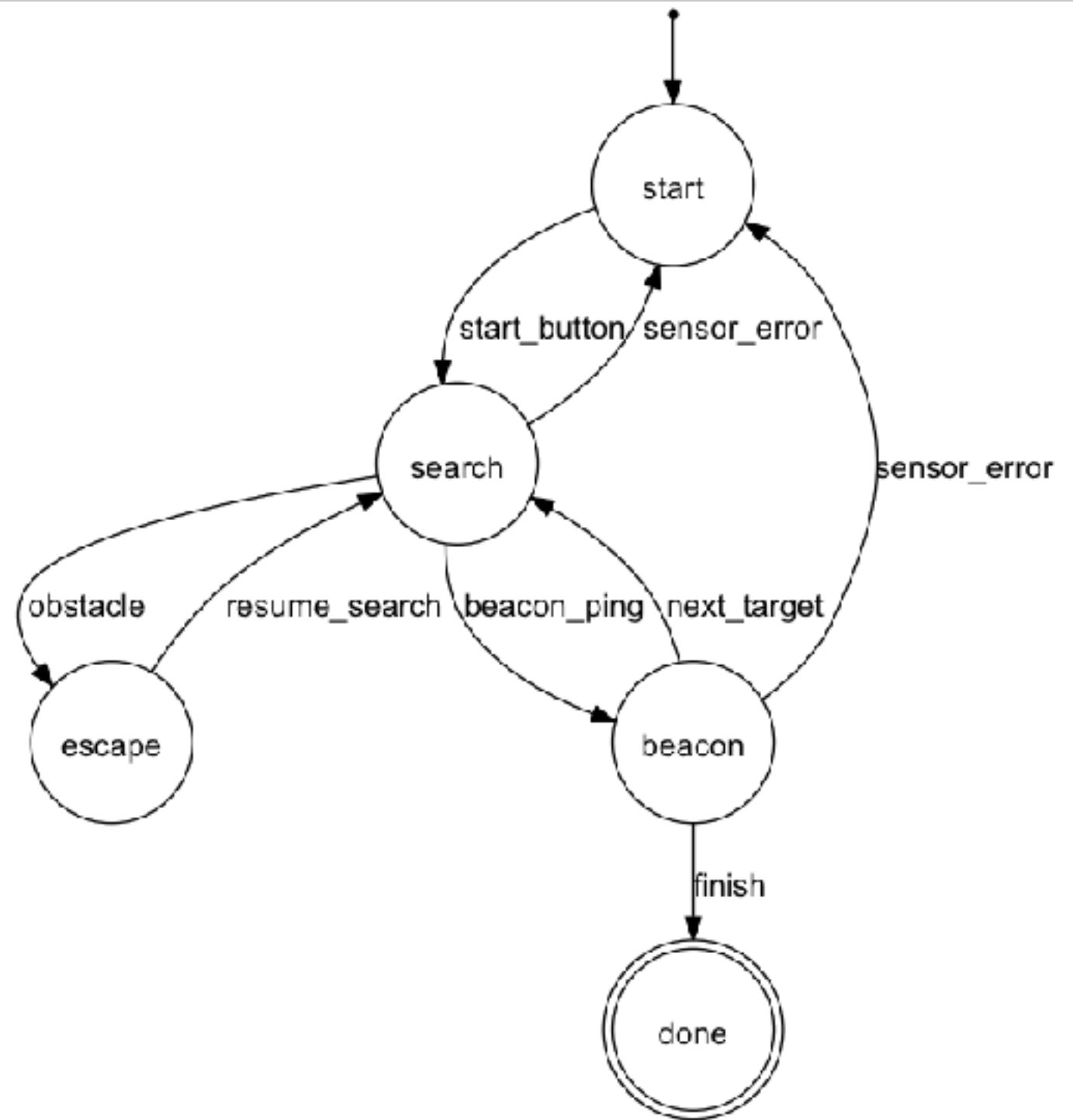 

# Syntax of a Verilog Case Statement

```
module statem(clk, in, reset, out);

input clk, in, reset;
output [3:0] out;

reg [3:0] out;
reg [1:0] state;

parameter zero=0, one=1, two=2, three=3;

always @(state)
begin
    case (state)
        zero:
            out = 4'b0000;
        one:
            out = 4'b0001;
        two:
            out = 4'b0010;
        three:
            out = 4'b0100;
        default:
            out = 4'b0000;
    endcase
end
```


```
always @(posedge clk or posedge reset)
begin
    if (reset)
        state = zero;
    else
        case (state)
            zero:
                state = one;
            one:
                if (in)
                    state = zero;
                else
                    state = two;
            two:
                state = three;
            three:
                state = zero;
        endcase
    end
endmodule
```

# Syntax of a Verilog Case Statement
 
## ❖ Edge detector: Moore Machine


```
localparam A=0, B=1, C=2, D=4, E=5;  
reg [2:0] state,    // Current state  
        nxtState; // Next state
```

```
always @(posedge clk) begin  
    if (reset) begin  
        state <= A;    // Initial state  
    end else begin  
        state <= nxtState;  
    end  
end
```


 
# Verilog case Implementation

```
always @(*) begin
  nxtState = state;
  out = 0;
  case (state)
    A : if (in) nxtState = C;
        else      nxtState = B;
    B : if (in) nxtState = D;
    C : if (~in) nxtState = E;
    D : begin
        out = 1;
        if (in) nxtState = C;
        else    nxtState = E;
      end
    E : begin
        out = 1;
        if (in) nxtState = D;
        else    nxtState = B;
      end
    default : begin
        out = 1'bX;
        nxtState = 3'bX;
      end
  endcase
end
```






# Syntax of a Verilog Case Statement
 
## ❖ Edge detector: Mealy Machine


```
localparam A=0, B=1, C=2;  
reg [1:0] state,    // Current state  
          nxtState; // Next state  
  
always @(posedge clk) begin  
    if (reset) begin  
        state <= A;    // Initial state  
    end else begin  
        state <= nxtState;  
    end  
end
```


 
# Verilog Case Implementation

Output depends on state and input

```
always @(*) begin
  nxtState = state;
  out = 0;
  case (state)
    A : if (in) nxtState = C;
        else    nxtState = B;
    B : if (in) begin
          out = 1;
          nxtState = C;
        end
    C : if (~in) begin
          out = 1;
          nxtState = B;
        end
    default : begin
          out = 1'bX;
          nxtState = 3'bX;
        end
  endcase
end
```



---

# State Elements

---

- ❖ The state of a circuit influences its future behavior
- ❖ State elements store state
- ❖ Bistable circuit
- ❖ SR Latch
- ❖ D Latch
- ❖ D Flip-flop

---



# Sequential Circuits

---

- ❖ Give sequence to events
- ❖ Have memory (short-term)
- ❖ Use feedback from output to input to store information
  
# Bistable Circuit

- ❖ Fundamental building block of other state elements
- ❖ Two outputs:  $Q$ ,  $\bar{Q}$
- ❖ No inputs



# Bistable Circuit Analysis



- Consider the two possible cases:

- $Q = 0$ : –

- then  $Q = 1$ ,  $Q = 0$  (consistent)

- $Q = 1$ : –


- then  $Q = 0$ ,  $Q = 1$  (consistent)

  

- Stores 1 bit of state in the state variable,  $Q$  (or  $\bar{Q}$ )
- But there are **no inputs to control the state**

# SR (Set / Reset) Latch

- SR Latch

 


- Consider the four possible cases:
  - $S = 1, R = 0$
  - $S = 0, R = 1$
  - $S = 0, R = 0$
  - $S = 1, R = 1$

# SR Latch Analysis


–  $S = 1, R = 0$ :

then  $Q = 1$  and  $\bar{Q} = 0$

 

–  $S = 0, R = 1$ :



then  $Q = 0$  and  $\bar{Q} = 1$

 



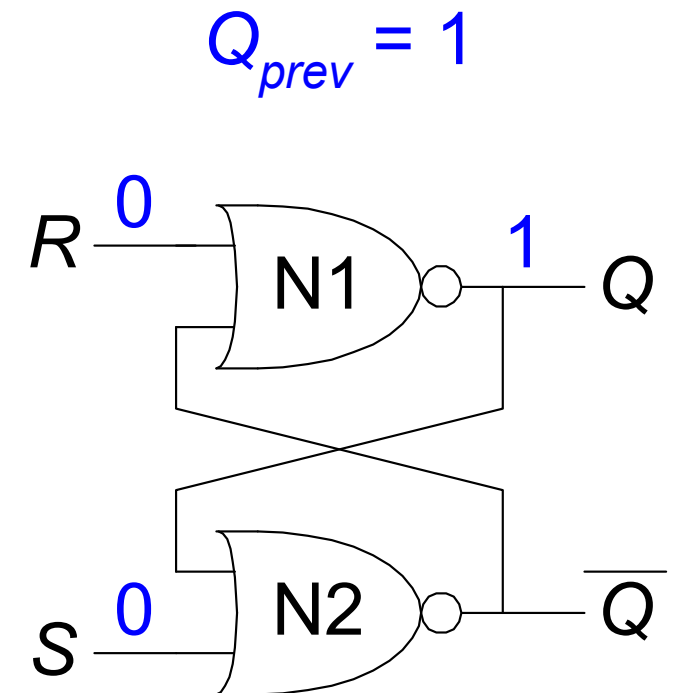 
# SR Latch Analysis

–  $S = 0, R = 0$ :  
then  $Q = Q_{prev}$



 –  $S = 1, R = 1$ :  
then  $Q = 0, \overline{Q} = 0$





# SR Latch Analysis

–  $S = 0, R = 0$ :

then  $Q = Q_{prev}$

– **Memory!**

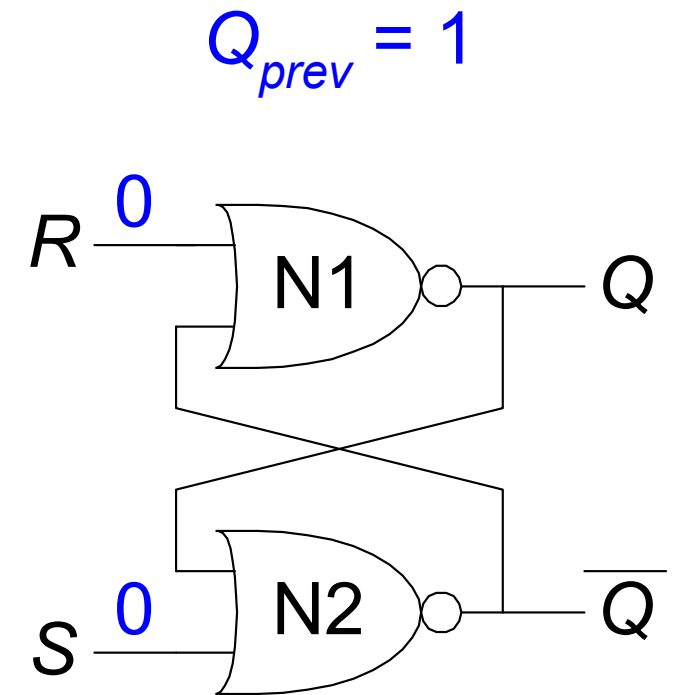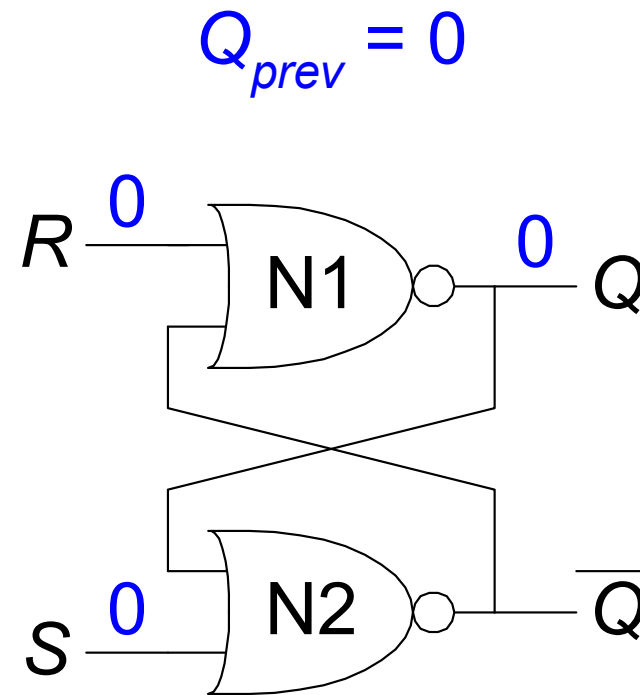


–  $S = 1, R = 1$ :

then  $Q = 0, \bar{Q} = 0$

– **Invalid State**


$\bar{Q} \neq \text{NOT } Q$

 

# SR Latch Symbol

- SR stands for Set/Reset Latch
  - Stores one bit of state ( $Q$ )
- Control what value is being stored with  $S$ ,  $R$  inputs
  - **Set:** Make the output 1  
( $S = 1, R = 0, Q = 1$ )
  - **Reset:** Make the output 0  
( $S = 0, R = 1, Q = 0$ )
- **Must do something to avoid invalid state (when  $S = R = 1$ )**

SR Latch  
Symbol

 

# D Latch

- Two inputs:  $CLK$ ,  $D$ 
  - $CLK$ : controls *when* the output changes
  - $D$  (the data input): controls *what* the output changes to


- Function

- When  $CLK = 1$ ,  
 $D$  passes through to  $Q$  (*transparent*)
- When  $CLK = 0$ ,  
 $Q$  holds its previous value (*opaque*)


- Avoids invalid case when

$$Q \neq \text{NOT } Q$$

D Latch  
Symbol

 


# D Latch Internal Circuit

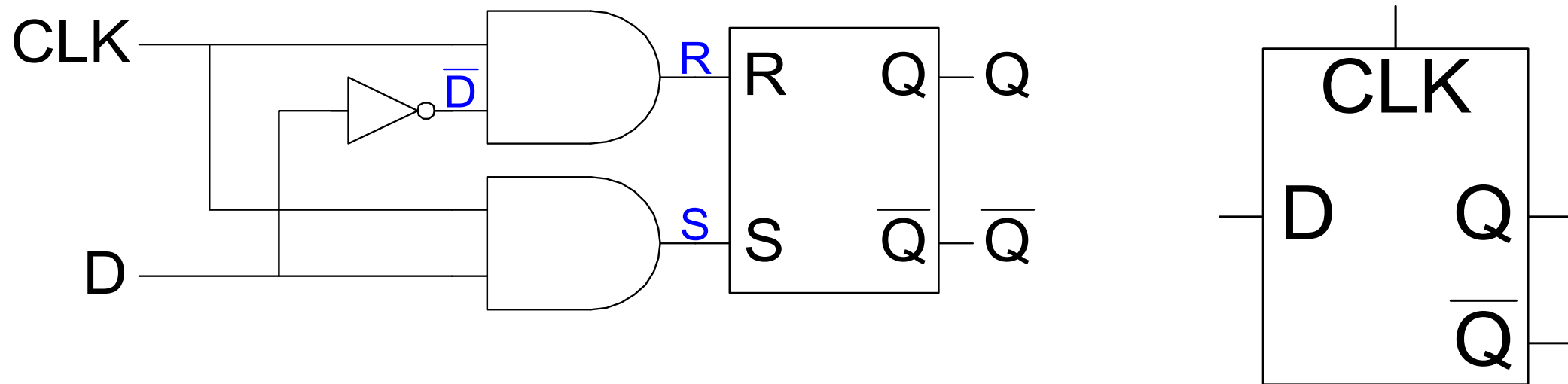

$CLK$	$D$	$\overline{D}$	$S$	$R$	$Q$	$\overline{Q}$
0	X					
1	0					
1	1					

# D Latch Internal Circuit

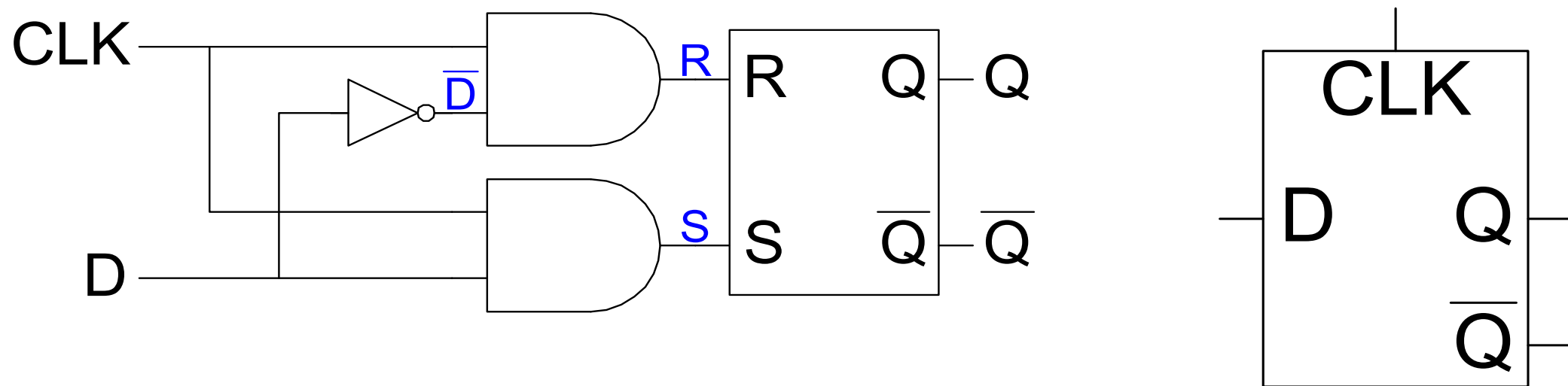


$CLK$	$D$	$\overline{D}$	$S$	$R$	$Q$	$\overline{Q}$
0	X	$\overline{X}$	0	0	$Q_{prev}$	$\overline{Q}_{prev}$
1	0	1	0	1	0	1
1	1	0	1	0	1	0

# D Flip-Flop


- **Inputs:**  $CLK$ ,  $D$
- **Function**
  - Samples  $D$  on rising edge of  $CLK$ 
    - When  $CLK$  rises from 0 to 1,  $D$  passes through to  $Q$
    - Otherwise,  $Q$  holds its previous value
  - $Q$  changes only on rising edge of  $CLK$
- Called *edge-triggered*
- Activated on the clock edge

D Flip-Flop  
Symbols

 


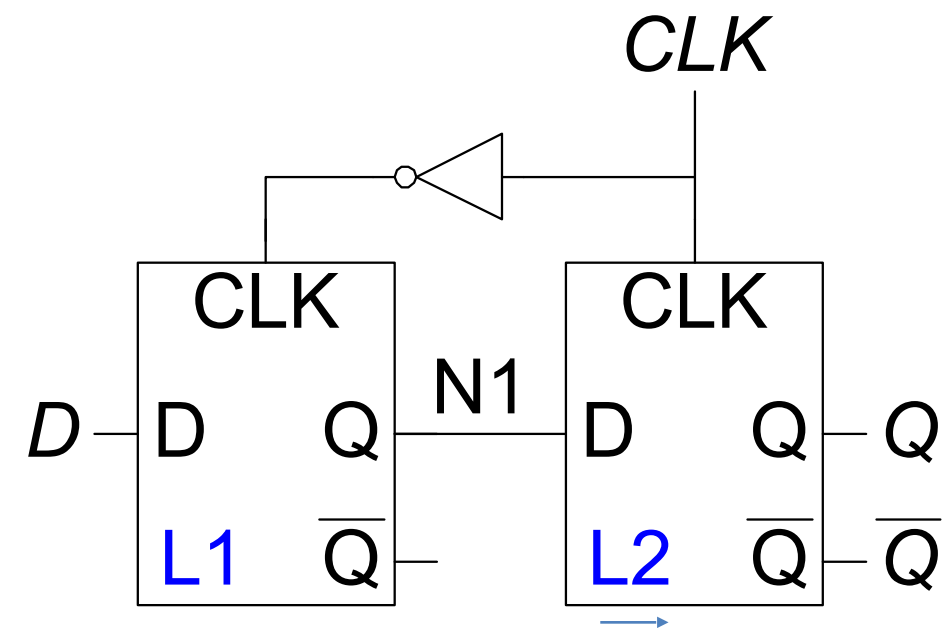
# D Flip-Flop Internal Circuit

- Two back-to-back latches (L1 and L2) controlled by complementary clocks
- When  **$CLK = 0$** 
  - L1 is transparent
  - L2 is opaque
  - $D$  passes through to N1
- When  **$CLK = 1$** 
  - L2 is transparent
  - L1 is opaque
  - N1 passes through to  $Q$
- Thus, on the edge of the clock (when  **$CLK$  rises from 0 to 1**)
  - $D$  passes through to  $Q$









# D Latch vs. D Flip-Flop

  

# D Latch vs. D Flip-Flop

  


# Registers

  


# Enabled Flip-Flops

- **Inputs:**  $CLK$ ,  $D$ ,  $EN$ 
  - The enable input ( $EN$ ) controls when new data ( $D$ ) is stored
- **Function**
  - $EN = 1$ :  $D$  passes through to  $Q$  on the clock edge
  - $EN = 0$ : the flip-flop retains its previous state

Internal  
Circuit

 



Symbol

 

# Resettable Flip-Flops

- **Inputs:**  $CLK$ ,  $D$ ,  $Reset$
- **Function:**
  - $Reset = 1$ :  $Q$  is forced to 0
  - $Reset = 0$ : flip-flop behaves as ordinary D flip-flop

## Symbols

  

---


# Resettable Flip-Flops

---

- Two types:
  - **Synchronous:** resets at the clock edge only
  - **Asynchronous:** resets immediately when  $Reset = 1$
- Asynchronously resettable flip-flop requires changing the internal circuitry of the flip-flop
- Synchronously resettable flip-flop?
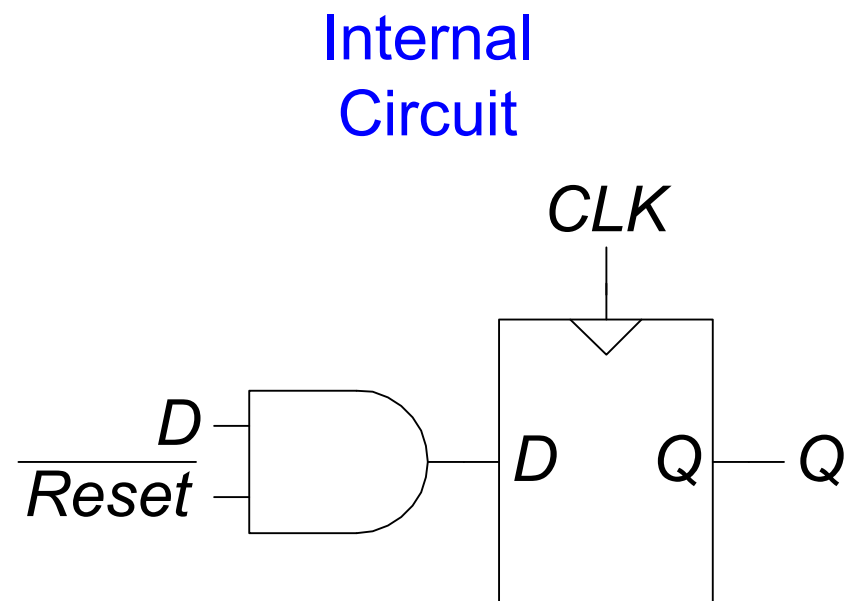
# Resettable Flip-Flops


- Two types:
  - **Synchronous:** resets at the clock edge only
  - **Asynchronous:** resets immediately when  $Reset = 1$
- Asynchronously resettable flip-flop requires changing the internal circuitry of the flip-flop
- Synchronously resettable flip-flop?



# Settable Flip-Flops

- **Inputs:**  $CLK$ ,  $D$ ,  $Set$
- **Function:**
  - $Set = 1$ :  $Q$  is set to 1
  - $Set = 0$ : the flip-flop behaves as ordinary D flip-flop



## Symbols

 



 
 
# Sequential Logic

- Sequential circuits: all circuits that aren't combinational
- A problematic circuit:


  
# Sequential Logic

- Sequential circuits: all circuits that aren't combinational
- A problematic circuit:



- No inputs and 1-3 outputs
- Astable circuit, oscillates
- Period depends on inverter delay
- It has a *cyclic path*: output fed back to input