

EECE 2322: Fundamentals of Digital Design and Computer Organization

Lecture 2_3: Digital Components and Verilog

Xiaolin Xu
Department of ECE
Northeastern University


Karnaugh Map

- ❖ Simplify a logic function
 - ❖ Combine pairs of adjacent 1-cells (minterms) whenever possible
 - ❖ Write a sum of product terms that cover all of the 1-cells

Karnaugh Map for 2-input

❖ What is $f()$?

x_1	x_2	f
0	0	1
0	1	1
1	0	0
1	1	1

 

$$f = \bar{x}_1 + x_2$$

Karnaugh Map for 2-input

❖ What is $F()$?

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1




Truth Table.

		A	
B	0	1	
	0	1	
0	0	1	←
1	1	1	

F .

Karnaugh Map

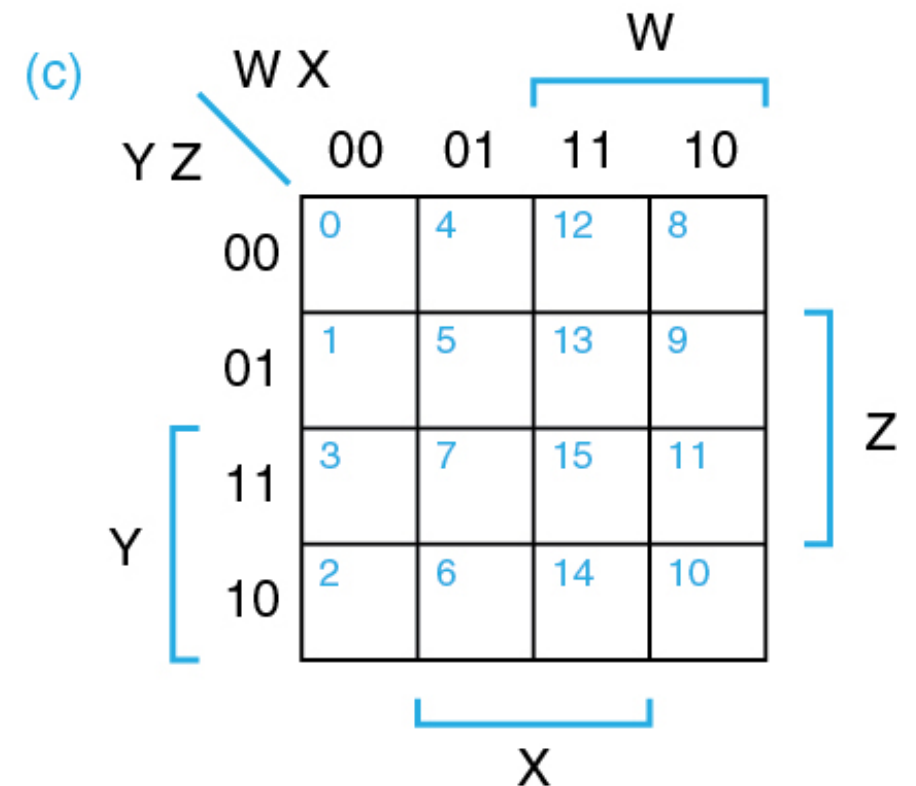  - ❖ (A) 2-Variable; (B) 3-Variable; (C) 4-Variable





Karnaugh Map

❖ $F = \sum_{X,Y,Z}(1,2,5,7)$:

❖ (a) truth table; (b) Karnaugh map; (c) combining adjacent 1-cells.

(a)


X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

  

Karnaugh Map

❖ $F = \Sigma_{X,Y,Z}(1,2,5,7)$:

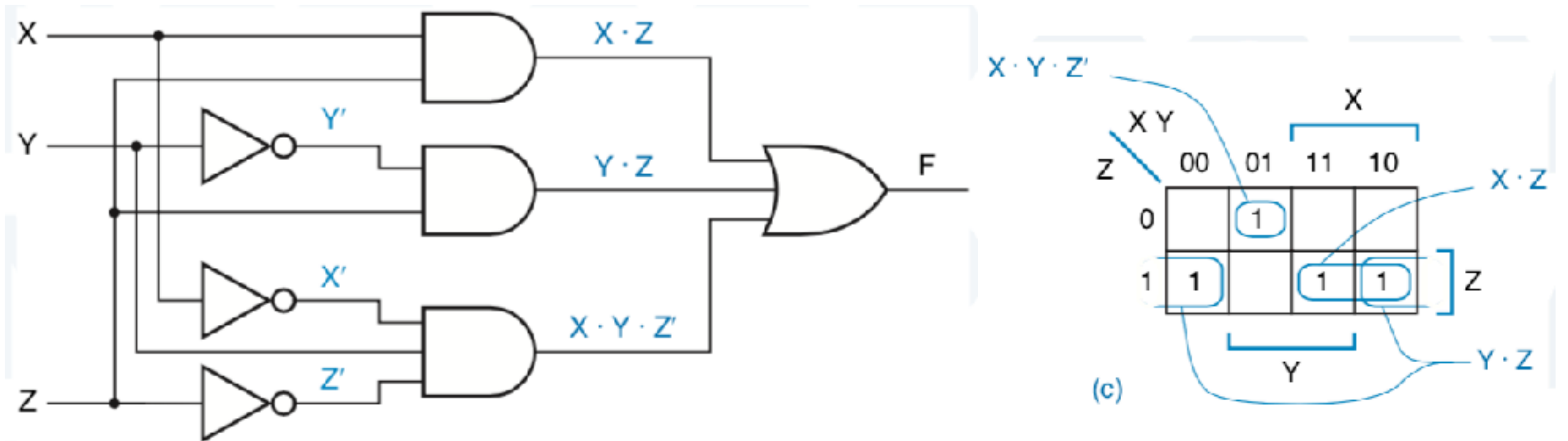❖ (a) truth table; (b) Karnaugh map; (c) combining adjacent 1-cells.





“Don’t-Care” Inputs

- ❖ Sometimes, the specification of a combinational circuit is such that its output doesn’t matter for certain input combinations, called **don’t-cares**.
- ❖ This may be true because the outputs really don’t matter when these input patterns occur, or because these input patterns never occur in practical operation.

“Don’t-Care” Input Combinations

❖ Input: N_0 - N_3

  


Hardware Description Language (HDL)

- ❖ Very-High-Speed Integrated Circuit (VHSIC) Hardware Description Language (VHDL):
 - ❖ Modeling of digital systems
 - ❖ Concurrent and sequential statements
 - ❖ Machine-readable specification
 - ❖ Man- and machine-readable documentation
- ❖ International Standards:
 - ❖ IEEE Std 1076-1987 - IEEE Std 1076-1993

Hardware Description Language (HDL)


- ❖ Review the design schematic

- ❖ Flat

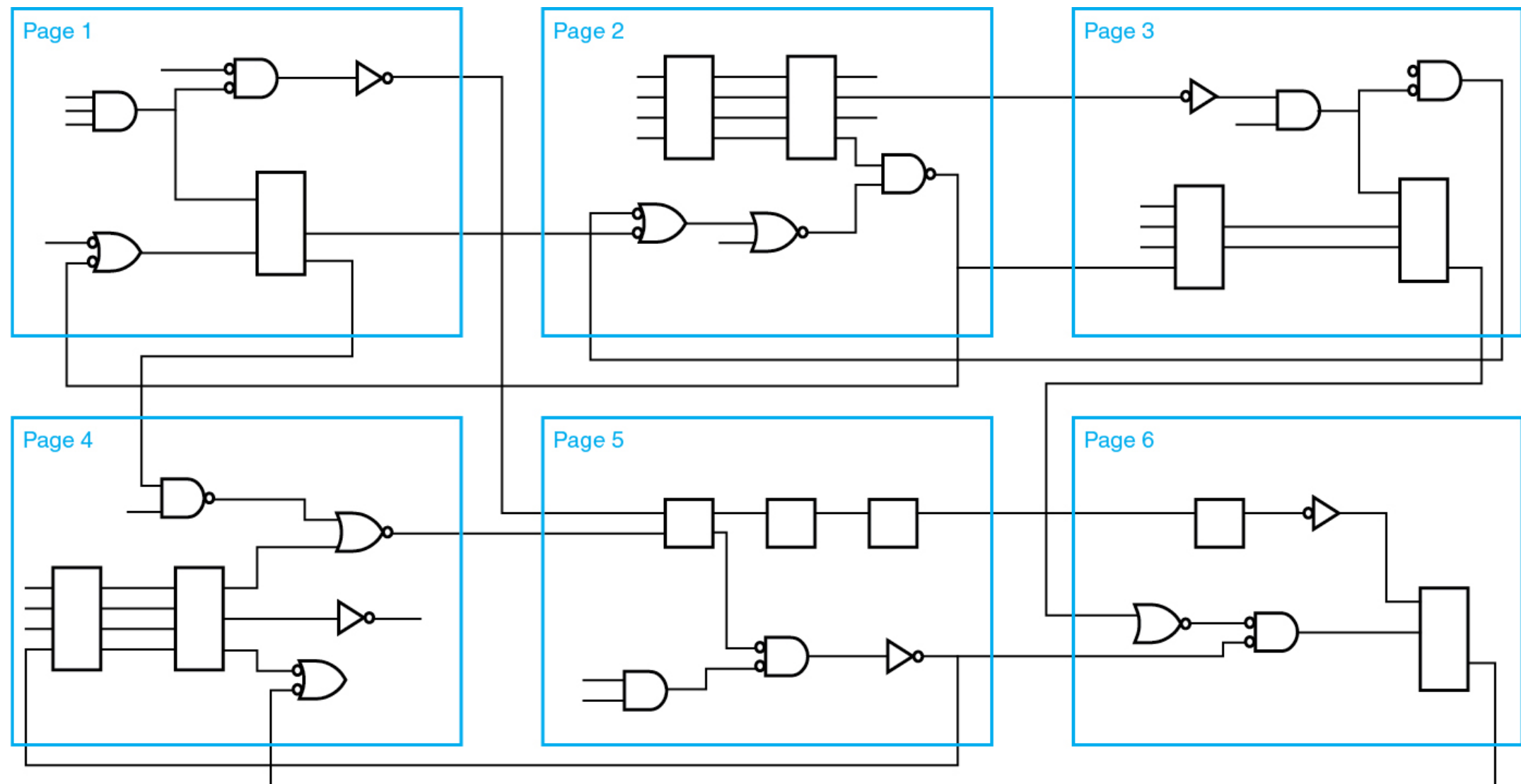


Hardware Description Language (HDL)

 - ❖ Review the design schematic
 - ❖ Hierarchical



Hierarchy Example

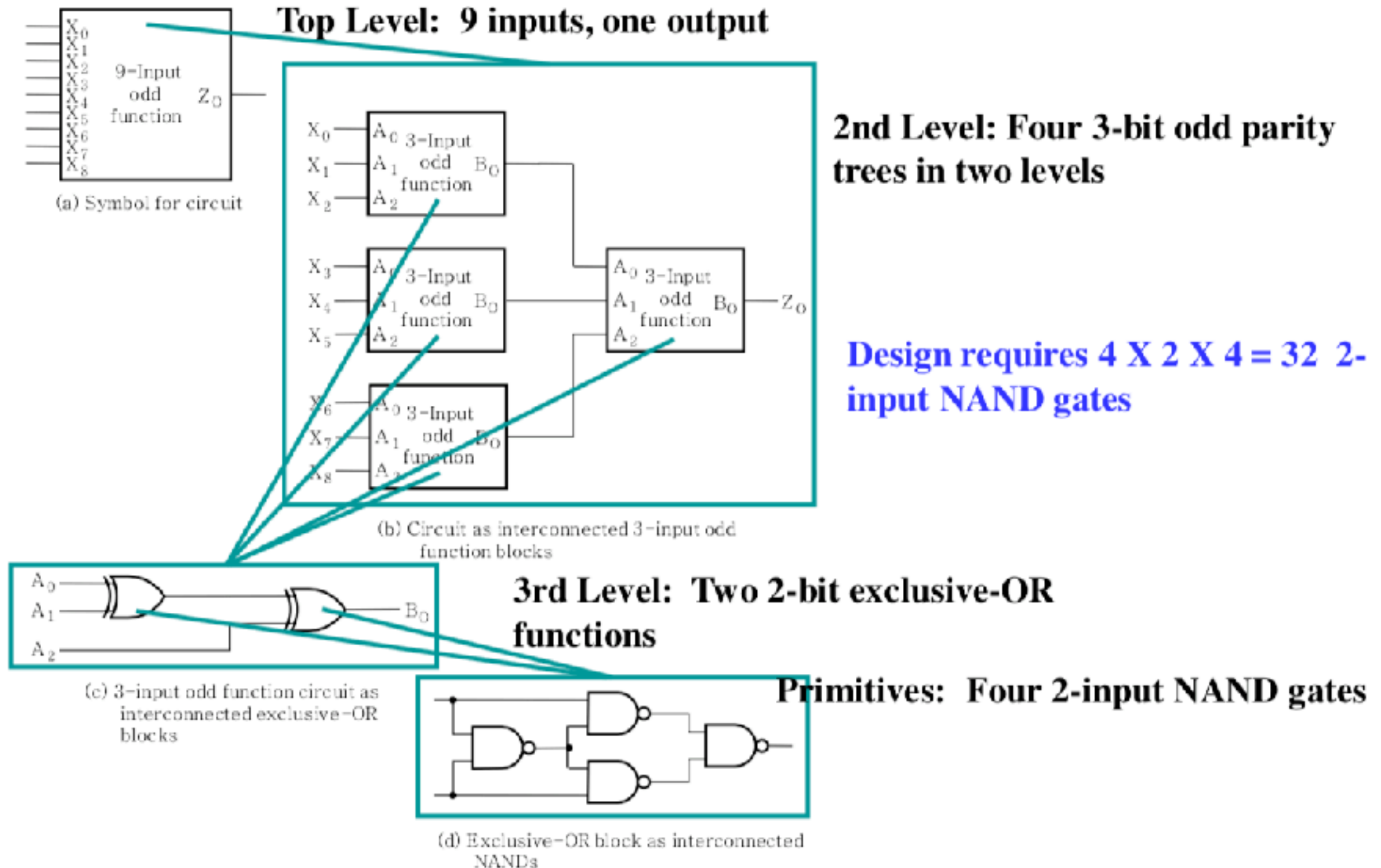

Elements of Verilog: Hardware Modules

- ❖ Verilog hardware description language (HDL) is used to describe hardware modules of a system and complete systems.
- ❖ keyword module, Name of the module, A list of ports of the hardware module, the module functionality specification, and the keyword endmodule.
- ❖ Following a module name and its list of ports, usually variables, wires, and module parameters are declared.
- ❖ After the declarations, statements in a module specify its functionality. This part defines how output ports react to changes on the input ports.

Elements of Verilog: Hardware Modules

- ❖ Verilog hardware description language (HDL) is used to describe hardware modules of a system and complete systems.
- ❖ keyword module, Name of the module, A list of ports of the hardware module, the module functionality specification, and

```
module module-name  
    List of ports;  
    Declarations  
    ...  
    Functional specification of module  
    ...  
endmodule
```

Syntax of Verilog Input / Output Declarations

❖ Ports

- ❖ Ports allow communication between a module and its environment.
- ❖ All but the top-level modules in a hierarchy have ports.
- ❖ Ports can be associated by order or by name.
- ❖ You declare ports to be input, output or inout. The port declaration syntax is :
 - ❖ `input [range_val:range_var] list_of_identifiers;`
 - ❖ `output [range_val:range_var] list_of_identifiers;`
 - ❖ `inout [range_val:range_var] list_of_identifiers;`

Syntax of Verilog Input/Output Declarations

❖ Ports

- ❖ Ports allow communication between a module and its environment.
- ❖ All but the top-level modules in a hierarchy have ports.

▶ Port Declaration: `input [11:0] data_in; output [11:0] data_out;`


✦ Examples : Port Declaration

```
1 input      clk      ; // clock input
2 input [15:0] data_in ; // 16 bit data input bus
3 output [7:0] count   ; // 8 bit counter output
4 inout    data_bi    ; // Bi-Directional data bus
```

- ❖ `inout [range_val:range_var] list_of_identifiers;`

Elements of Verilog: Hardware Modules

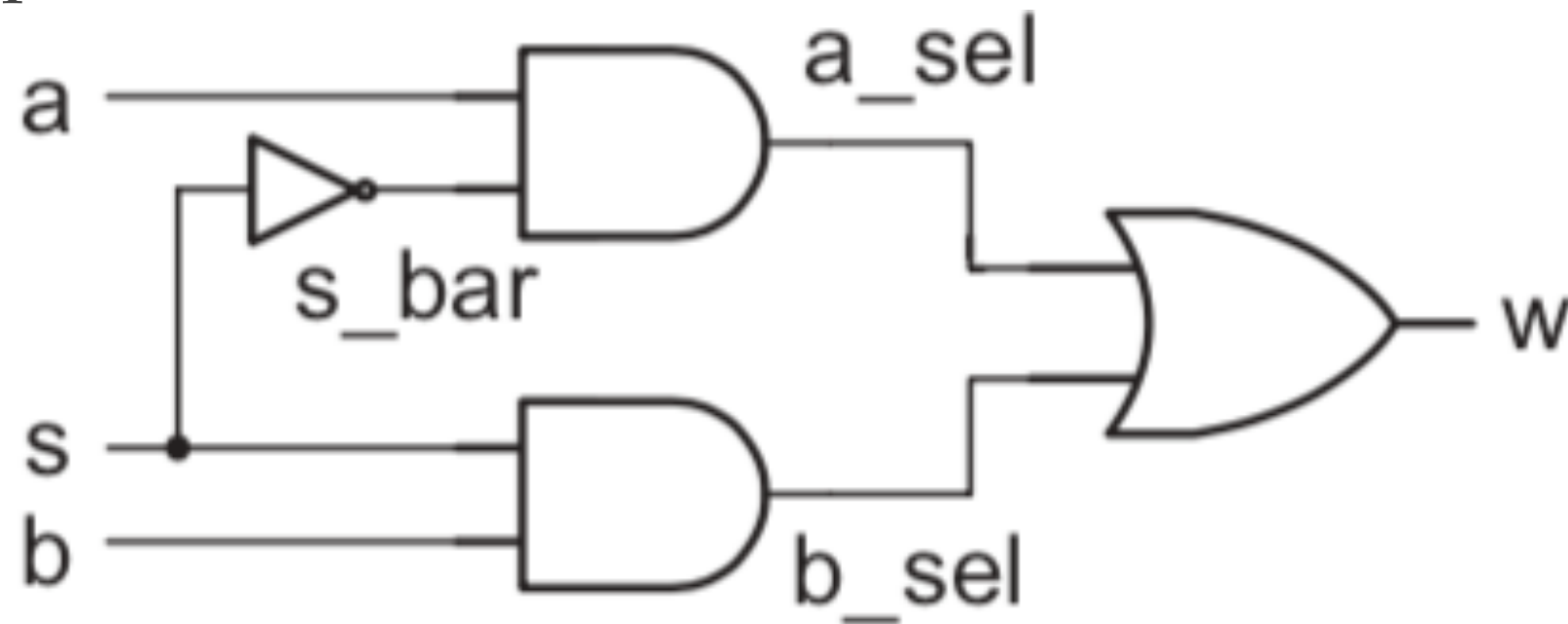
- ❖ A Multiplexer Using Basic Gates
 - ❖ Basic components?



Elements of Verilog: Hardware Modules

❖ A Multiplexer Using Basic Gates

❖ Basic components?

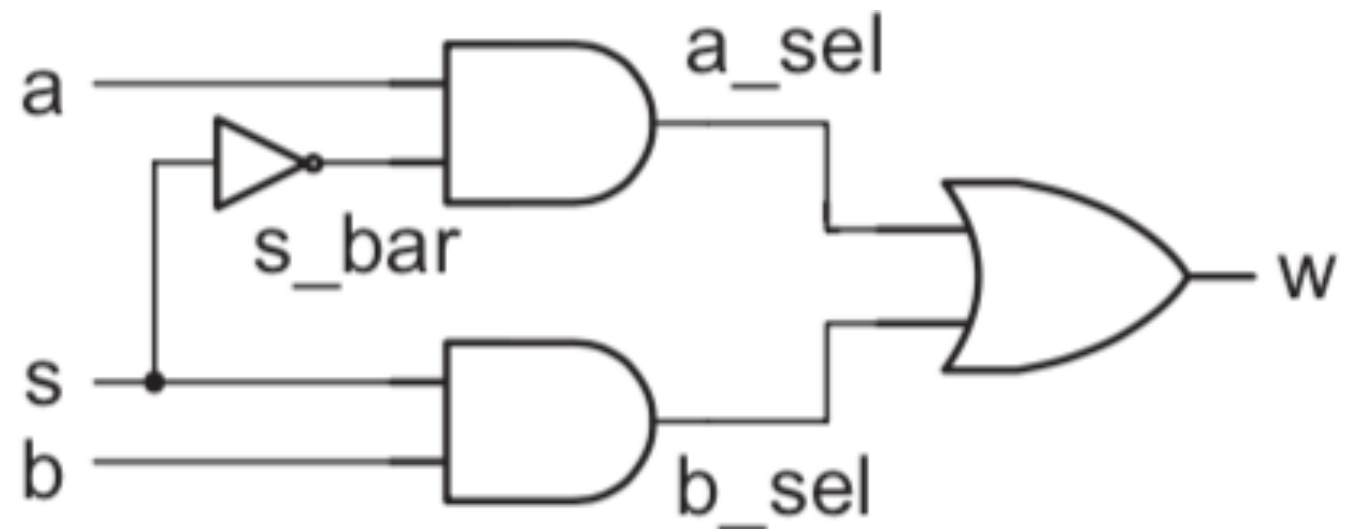


```
module MultiplexerA (input a, b, s, output w);  
    wire a_sel, b_sel, s_bar;  
    not U1 (s_bar, s);  
    and U2 (a_sel, a, s_bar);  
    and U3 (b_sel, b, s);  
    or U4 (w, a_sel, b_sel);  
endmodule
```

Write the Code By Yourself

❖ A Multiplexer Using Basic Gates


❖ Basic components?

 

```
module MultiplexerA (input a, b, s, output w);  
  wire a_sel, b_sel, s_bar;  
  not U1 (s_bar, s);  
  and U2 (a_sel, a, s_bar);  
  and U3 (b_sel, b, s);  
  or U4 (w, a_sel, b_sel);  
endmodule
```

Write the Code By Yourself

 - ❖ A Multiplexer Using Basic Gates
 - ❖ Basic components?



Module name

Module ports

```
module Add_half ( input a, input b, output sum, output c_out );  
wire c_out_bar;  
  
xor (sum, a, b);  
// xor G1 (sum, a, b); ← the label G1 is optional for logic gate primitives  
nand (c_out_bar, a, b);  
not (c_out, c_out_bar);  
  
endmodule
```

Declaration of internal signals

Instantiation of primitive gates

//Verilog keywords in blue

Assign statements

- ❖ Instead of describing a component using primitive gates, boolean expressions can be used to describe the logic
- ❖ Verilog assign statements can be used for assigning results of these expressions to various outputs.
 - ❖ The statement shown in the body of the MultiplexerB module continuously drives w with its right-hand side expression.


Verilog: Operator

Operator	Description
&	AND
~&	NAND
	OR
~	NOR
^	XOR
~^ or ^~	XNOR

```
module MultiplexerB (input a, b, s, output w);  
    assign w = (a & ~s) | (b & s);  
endmodule
```

Elements of Verilog: assign

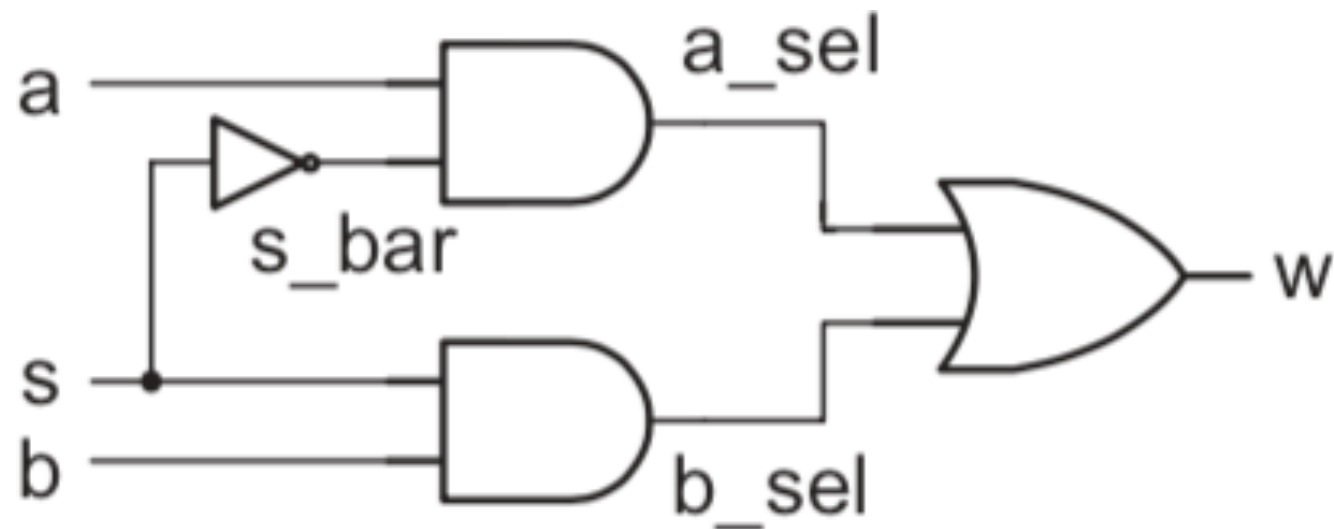
- ❖ Assign statement and Boolean expression



```
module MultiplexerB (input a, b, s, output w);  
    assign w = (a & ~s) | (b & s);  
endmodule
```


Elements of Verilog: assign

 
- ❖ Assign statement and Boolean expression
- ❖ Write the code by yourself



```
module MultiplexerB (input a, b, s, output w);  
    assign w = (a & ~s) | (b & s);  
endmodule
```

Elements of Verilog: assign

 - ❖ Assign statement and Boolean expression
- ❖ Write the code by yourself




```
module combo (input a, b, c, d, output o);  
  assign o = ~((a & b) | c ^ d);  
endmodule
```

Conditional Operator in Verilog

- ❖ The conditional operator has the following C-like format:
- ❖ `cond_expr ? true_expr : false_expr`
- ❖ The `true_expr` or the `false_expr` is evaluated and used as a result depending on what `cond_expr` evaluates to (true or false).

Conditional Operator in Verilog

 - ❖ The conditional operator has the following C-like format:
- ❖ `cond_expr ? true_expr : false_expr`
- ❖ `module Mux2_1(z, c, x, y);`
 - ❖ `input c, x, y;`
 - ❖ `output z;`
 - ❖ `assign z = c ? x : y;`
- ❖ `endmodule`



Procedural Blocks

- ❖ What if the operation of a unit is too complex to be described? by assignment of boolean or conditional expressions?

```
module MultiplexerD (input a, b, s, output w);  
    reg w;  
    always @ (a, b, s) begin  
        if (s) w = b;  
        else w = a;  
    end  
endmodule
```

Procedural Blocks


- ❖ What if the operation of a unit is too complex to be described? by assignment of boolean or conditional expressions?
- ❖ higher-level procedural constructs should be used.

```
module MultiplexerD (input a, b, s, output w);  
    reg w;  
    always @ (a, b, s) begin  
        if (s) w = b;  
        else w = a;  
    end  
endmodule
```

Procedural Blocks

- ❖ What if the operation of a unit is too complex to be described? by assignment of boolean or conditional expressions?
- ❖ higher-level procedural constructs should be used.
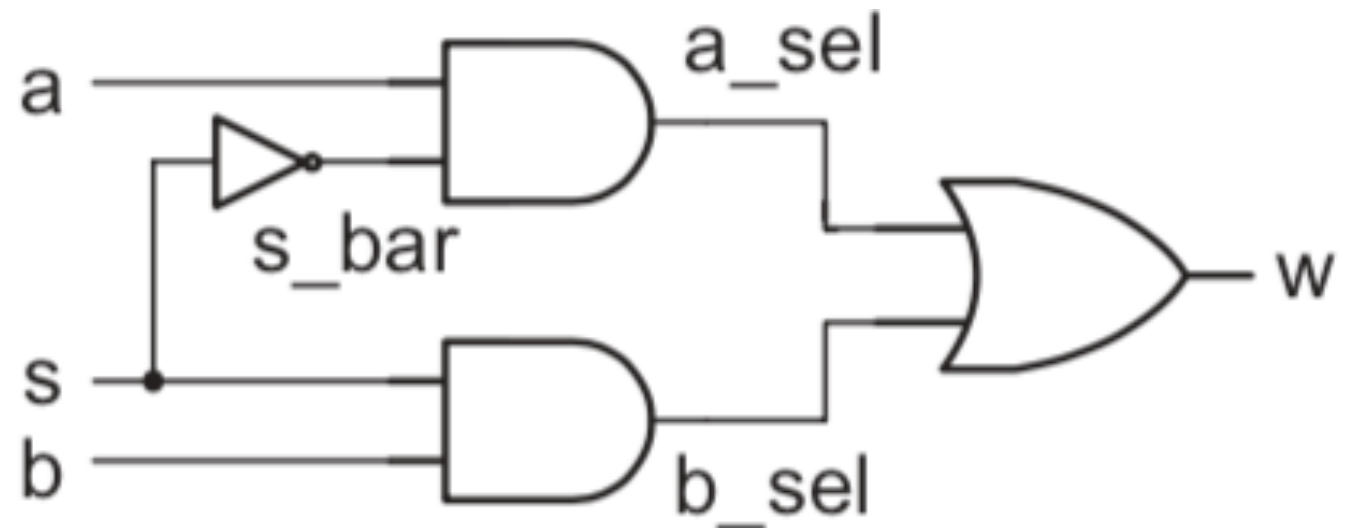
```
module MultiplexerD (input a, b, s, output w);  
  reg w;  
  always @ (a, b, s) begin  
    if (s) w = b;  
    else w = a;  
  end  
endmodule
```



Data Representation in Verilog

<i>Literal</i>	<i>Meaning</i>
1'b0	A single 0 bit
1'b1	A single 1 bit
1'bx	A single unknown bit
8'b00000000	An 8-bit vector of all 0 bits
8'h07	An 8-bit vector of five 0 and three 1 bits
8'b111	The same 8-bit vector (0-padded on left)
16'hF00D	A 16-bit vector that makes me hungry
16'd61453	The same 16-bit vector, with less hunger
2'b1011	Tricky or an error, leftmost "10" ignored
4'b1?zz	A 4-bit vector with three high-Z bits
8'b01x11xx0	An 8-bit vector with some unknown bits

Testbench and Simulation

- ❖ **A NAND gate**

- ❖ `// Data-flow modeling of a nand gate`
- ❖ `module nand_gate(c,a,b);`
- ❖ `input a,b;`
- ❖ `output c;`
- ❖ `assign c =~(a&b);`
- ❖ `endmodule`

Xilinx Vivado or Online Simulator

- ❖ Use the Xilinx tools to simulate your Verilog
- ❖ OR you can use online tools:
- ❖ Icarus Verilog <http://iverilog.icarus.com>
- ❖

Testbench and Simulation: NAND Gate

- ❖ // high level module to test nand, test_nand1.v
- ❖ module nand_test;
- ❖ reg a,b;
- ❖ wire c;
- ❖ nand_gate nand_test(c,a,b);
- ❖ initial begin // apply the stimulus, test data
- ❖ a=0; b=0; // initial value
- ❖ #1 a=1; // delay one simulation cycle, then change a=1.
- ❖ #1 b=1;
- ❖ #1 a=0;
- ❖ #1;
- ❖ end
- ❖ initial begin
- ❖ \$monitor(\$time," a=%b, b=%b, c=%b",a,b,c);
- ❖ end
- ❖ endmodule

More Example: 2-1 MUX


❖ 2-1 Multiplexer

2-to-1 Multiplexer Behavior

when sel = 0 choose A to send to output Y
sel = 1 choose B

$$Y = \overline{\text{Sel}} \bullet A + \text{Sel} \bullet B$$

sel	Y
0	A
1	B

 

Design Code of 2-1 MUX

❖ Structural Model: 2-1 mux

❖

```
module mux2 (in0, in1, select, out);  
    input in0,in1,select;  
    output out;  
    wire s0,w0,w1;  
  
    not (s0, select);  
    and (w0, s0, in0),  
        (w1, select, in1);  
    or  (out, w0, w1);  
  
endmodule // mux2
```

Testbench of 2-1 MUX

```
module testmux;
  reg a, b, s;
  wire f;
  reg expected;
mux2 myMux (.select(s), .in0(a), .in1(b), .out(f));
  initial
    begin
      #0 s=0; a=0; b=1; expected=0;
      #10 a=1; b=0; expected=1;
      #10 s=1; a=0; b=1; expected=1;
      #10 $stop;
    end
  initial
    $monitor("select=%b in0=%b in1=%b out=%b, expected out=%b time=%d",
             s, a, b, f, expected, $time);
endmodule // testmux
```

Testing Results

- ❖ Result of running testbench:
 - ❖ select=0 in0=0 in1=1 out=0, expected out=0 time=0
 - ❖ select=0 in0=1 in1=0 out=1, expected out=1 time=10
 - ❖ select=1 in0=0 in1=1 out=1, expected out=1 time=20

Testing Results

- ❖ Testbench:
 - ❖ Provides inputs, checks on outputs
 - ❖ Design is instantiated inside testbench
 - ❖ Verilog code in testbench does not describe circuits
 - ❖ Behaves like an ordinary programming language
- ❖ *Does this testbench cover all possible input combinations?*

Modeling Circuit Delay

```
module mux2 (in0, in1, select, out);  
    input in0,in1,select;  
    output out;  
    wire s0,w0,w1;  
    not #1 (s0, select);  
    and #1 (w0, s0, in0),  
          (w1, select, in1);  
    or #1 (out, w0, w1);  
endmodule // mux2
```

❖ *#1 represents delay from inputs to output*